

1. (10 points) FoEE 7.27

7.27 For the circuit shown in Fig. P7.27, suppose that $R_B = 230 \text{ k}\Omega$, $R_{E1} = 400 \Omega$, $R_{E2} = 0 \Omega$, $R_C = 100 \Omega$, and $V_{CC} = 6 \text{ V}$. Given that the BJTs have $\beta = 100$, verify that the transistors are in the active region by finding i_{C1} , v_{CE1} , i_{C2} , and v_{CE2} .


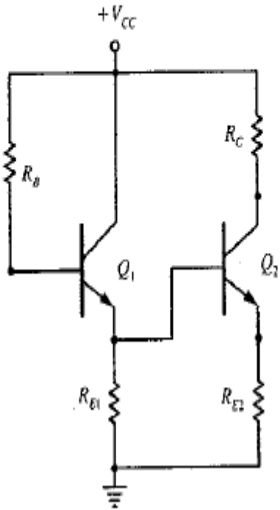


Fig. P7.27

$$\beta = 100$$

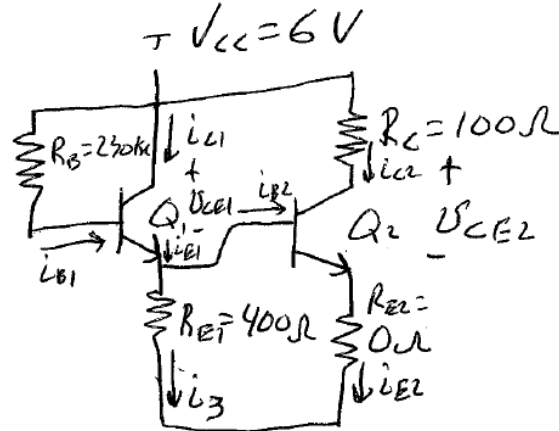

If we are asked to verify that the transistors are on, then we can assume on and confirm that there are no contradictions.

If Q_1 & Q_2 are on: $V_{BE1} = 0.7 \text{ V}$, $V_{BE2} = 0.7 \text{ V}$

$$i_{C1} \approx i_{B1} = 100 i_{B1} \text{ and } i_{C2} = 100 i_{B2}$$

so, KVL: $6 = 230 \text{ k} (i_{B1}) + V_{BE1} + V_{BE2} + i_{E2} R_{E2}$

$$6 = 230,000 i_{B1} + 1.4$$

$$\therefore i_{B1} = 20 \mu\text{A}$$

$$i_{C1} = 100 i_{B1} \therefore i_{C1} = 2 \text{ mA}$$

$$i_{B2} = i_{E1} - i_{C1}$$

$$i_{C1} = \frac{V_{BE2}}{400 \Omega} = \frac{0.7}{400} \text{ A}$$

$$i_{E1} = i_{B1} + i_{C1} = 2.02 \text{ mA}$$

$$\therefore i_{B2} = 2.02 \text{ mA} - 1.75 \text{ mA} = 270 \mu\text{A}$$

$$\therefore i_{C2} = 100 \cdot 270 \mu\text{A} = 27 \text{ mA}$$

By KVL: $V_{CE1} = 6 - V_{BE2} = 5.3 \text{ V}$

By KVL: $V_{E2} = 6 - i_{C2} (R_C) = 3.3 \text{ V}$

2. (10 points) FoEE 7.91

7.91 The RTL circuit shown in Fig. P7.91 is a NAND gate. The low voltage is 0.4 V and the high voltage is 1.2 V. Determine whether each transistor is OFF or ON, and find the minimum values of h_{FE} for (a) $v_1 = v_2 = 0.4$ V; (b) $v_1 = 0.4$ V, $v_2 = 1.2$ V; (c) $v_1 = 1.2$ V, $v_2 = 0.4$ V; and (d) $v_1 = v_2 = 1.2$ V.


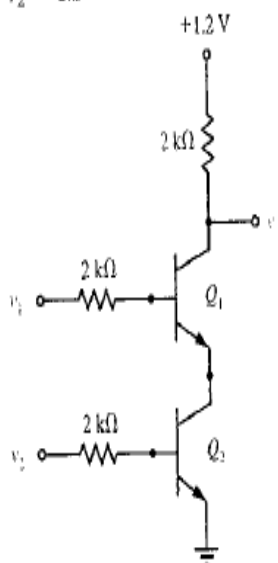


Fig. P7.91

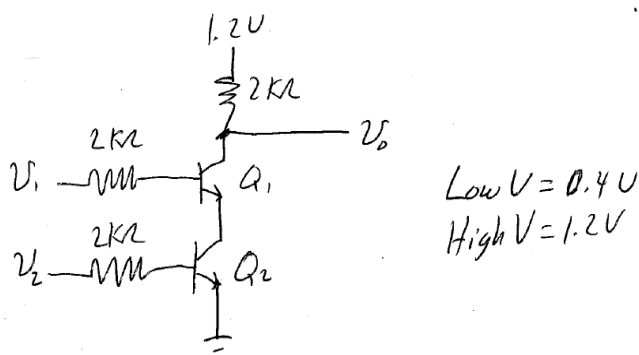

a) By looking at v_1, v_2 we know Q_2 is off.
 $v_1 = v_2 = 0.4$ V. V_{BE2} isn't high enough to turn it on.

$$\therefore i_{B2} = 0, i_{C2} = 0.$$

$$\text{If } i_{C2} = 0 \text{ then } i_{E1} = 0.$$

$V_{BE1} < 0.5$ V so Q_1 is off.

No current flows, so $V_o = 1.2$ V.

b) $v_1 = 0.4$ V, $v_2 = 1.2$ V

Here, Q_2 is on since $v_2 > 0.5$ V.

$$i_{B2} = \frac{v_2 - V_{BE2}}{2K} = 0.2 \text{ mA}$$

Since $v_1 < 0.5$, Q_1 is off ... so, $i_{B1} = 0, i_{C1} = 0$

$$i_{C1} = i_{E1} = i_{C2} = 0 \text{ A.}$$

$$\text{Since } h_{FE1} = \frac{i_{C2}}{i_{B2}} = \frac{0}{0.2 \text{ mA}} = 0.$$

$$V_o = 1.2 \text{ V}$$

c) $v_1 = 1.2$ V, $v_2 = 0.4$ V. $V_{BE2} < 0.5 \dots Q_2$ is off

$$\text{So, } i_{B2} = i_{C2} = 0$$

If Q_1 is ON, so $i_{B1} > 0$ A. $i_{C2} = i_{E2} = i_{B2} + i_{C2}$
this is > 0 A.

So, Q_1 is off.

$$\therefore V_o = 1.2 \text{ V}$$

d) $v_1 = v_2 = 1.2$ V. So, assume both Q_1 & Q_2 are on.

$$i_{B2} = \frac{v_2 - V_{BE2}}{2K} = 0.2 \text{ mA}$$

$$i_{B1} = \frac{v_1 - (V_{BE1} + V_{CE2})}{2K} = 0.1 \text{ mA}$$

$$V_o = V_{CE1} + V_{CE2} = 0.4 \text{ V.}$$

$$i_{C1} = \frac{1.2 - 0.4}{2K} = 0.4 \text{ mA.}$$

$$\text{Also, } i_{C2} = i_{B1} + i_{C1} = 0.1 \text{ mA} + 0.4 \text{ mA} = 0.5 \text{ mA}$$

$$h_{FE1} \geq \frac{i_{C1}}{i_{B1}} = 4 \quad h_{FE2} \geq \frac{i_{C2}}{i_{B2}} = 2.5$$

3. (10 points) FoEE 8.11


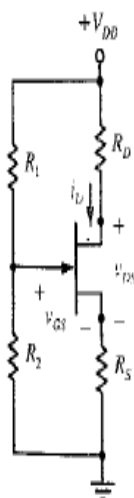


Fig. P8.10

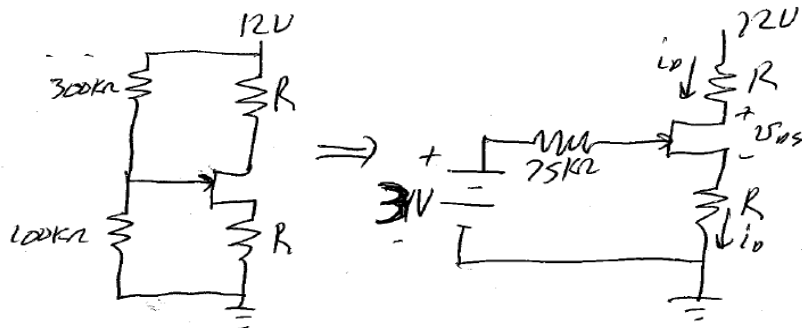8.11 For the circuit shown in Fig. P8.10, the JFET has $I_{DSS} = 12 \text{ mA}$ and $V_p = -4 \text{ V}$. Given that $R_1 = 300 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_D = R_S = R$, $V_{DD} = 12 \text{ V}$, and $v_{DS} = 6 \text{ V}$, determine (a) v_{GS} , (b) i_D , and (c) R . (Hint: Use Thévenin's theorem.)



$$\begin{aligned} \text{a) } V_{DS} = 6 \text{ V} \quad \text{By KVL, } 12 &= R i_D + V_{DS} + R i_D \\ &= 2 R i_D + 6 \\ \therefore R i_D &= 3 \end{aligned}$$


$$\begin{aligned} \text{By KVL: } 3 &= 75 \text{ k} (i_G) + V_{GS} + R i_D \\ &= 0 + V_{GS} + R i_D \end{aligned}$$

$$\therefore V_{GS} = 0 \text{ V}$$

$$\begin{aligned} \text{b) } V_{DS} = 6 \text{ V} > V_{GS} - V_p = 4 \text{ V} \quad \text{JFET is active.} \\ \text{So } i_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = I_{DSS} = 12 \text{ mA.} \\ \text{c) From (c) } R i_D &= 3 \quad \text{so, } \frac{3}{12} = R = 250 \Omega \end{aligned}$$


4. (0 points) FoEE 7.13

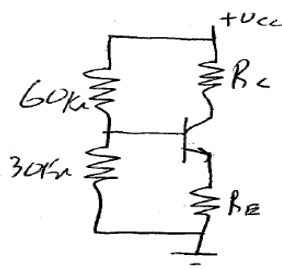7.13 The BJT in the circuit shown in Fig. P7.10 has $\beta = 100$. Suppose that $R_1 = 60 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$, and $V_{CC} = 6 \text{ V}$. Find R_E and R_C such that the transistor is biased in the active region at $i_C = 2 \text{ mA}$ and $v_{CE} = 2.1 \text{ V}$.



$$\begin{aligned} i_C &= 2 \text{ mA} \quad v_{CE} = 2.1 \text{ V} \\ \beta &= 100 \end{aligned}$$

Redrawing this we get:

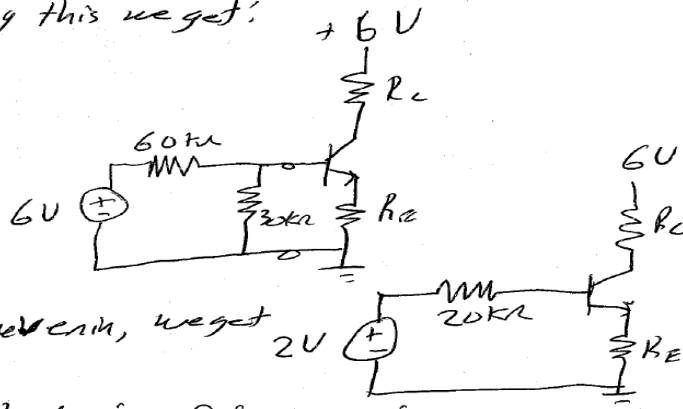

Using Thevenin, we get

$$\begin{aligned} \text{if } i_C &= 2 \text{ mA} \quad i_C = \beta i_B = 100 i_B \\ \text{So, } i_B &= 20 \mu\text{A} \end{aligned}$$

$$\begin{aligned} \text{By KVL: } 2 &= 20 \text{ k} (i_B) + V_{BE} + R_E (i_B + i_C) \\ 2 &= 20,000 (20 \mu\text{A}) + 0.7 + R_E (101 \cdot 20 \mu\text{A}) \\ R_E &= 446 \Omega \end{aligned}$$

$$\text{KVL again } \Rightarrow i_C R_C + v_{CE} + i_E R_E = 6 \Rightarrow R_C = 1.5 \text{ k}\Omega$$

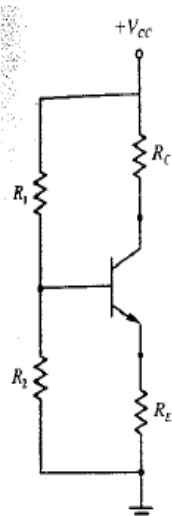


Fig. P7.10

5. (0 points) FoEE 8.33


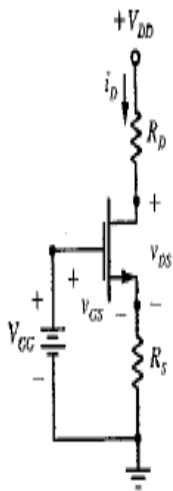


Fig. P8.32

8.33 For the circuit given in Fig. P8.32, the enhancement MOSFET has $K = 0.25 \text{ mA/V}^2$ and $V_t = 2 \text{ V}$. Given that $R_S = 0 \Omega$ and $V_{DD} = 16 \text{ V}$, determine the value of R_D for which the enhancement MOSFET will operate on the border between the active and the ohmic regions when V_{GG} is (a) 4 V and (b) 10 V.

S) FoEE 8.33

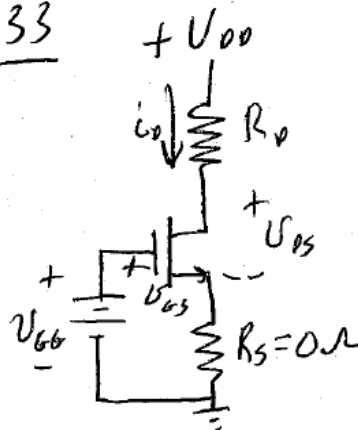

Given: $K = 0.25 \text{ mA/V}^2$
 $V_t = 2 \text{ V}$
 $V_{DD} = 16 \text{ V}$

At the border $V_{DS} = V_{GS} - V_t$

In (a) $V_{GG} = 4 \text{ V}$, so $V_{GS} = 4 \text{ V}$, so $V_{DS} = 2 \text{ V}$

using $i_D = K(V_{GS} - V_t)^2 = 1 \text{ mA}$

By KVL: $16 = R_D i_D + V_{DS} = R_D (1 \text{ mA}) + 2$

$\therefore R_D = 14 \text{ k}\Omega$

In (b) $V_{GG} = 10 \text{ V}$, so $V_{GS} = 10 \text{ V}$, so $V_{DS} = 8 \text{ V}$

Again $i_D = K(V_{GS} - V_t)^2 = 16 \text{ mA}$ By KVL we find $R_D = 500 \Omega$