

①
4.8 Connect a $5\text{-}\Omega$ resistor in parallel with the inductor in the circuit shown in Fig. P4.6. Suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ) \text{ V}$. Find the voltage $v_o(t)$ across the inductor by using nodal analysis. Draw a phasor diagram. Is this circuit a lag network or a lead network?


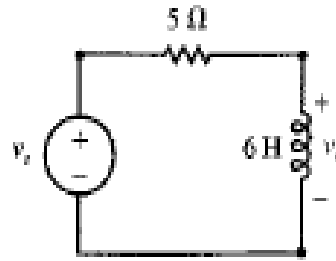


Fig. P4.6

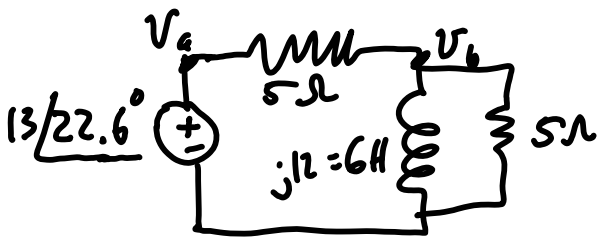

$$V_s = 13 \angle -22.6^\circ =$$


$$\frac{V_s - V_o}{5} = \frac{V_o}{5} + \frac{V_o}{j12}$$

$$12V_s - 12V_o = 12V_o - 5jV_o$$

$$(24 - j5)V_o = 12V_s = 12 \cdot 13 \angle -22.6^\circ$$


$$V_s(t) = 13 \cos(2t - 22.6^\circ)$$
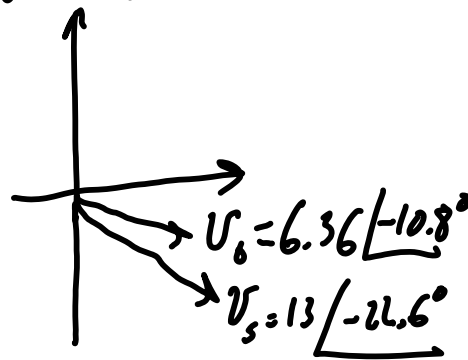
$$V_o = \frac{156 \angle -22.6^\circ}{\sqrt{601} \angle -11.8^\circ} = 6.36 \angle -10.8^\circ = 6.36 \cos(2t - 10.8^\circ)$$



Output leads source so this is a lead network.

② F0 EE 4.13

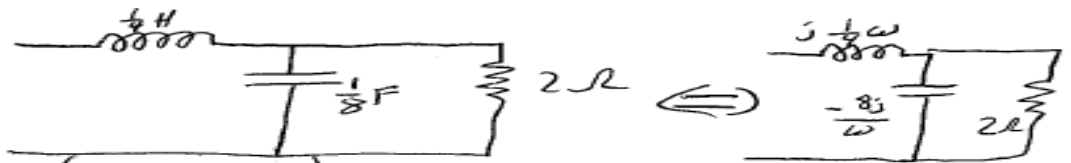

$$So, Z = \left(\frac{1}{\left(\frac{1}{(-j\frac{8}{\omega})} + \frac{1}{2} \right)} \right) + \frac{j\omega}{4}$$

Cap and resistor in series with inductor in parallel

$$Z = \frac{1}{\frac{1}{2} + \frac{j\omega}{8}} + \frac{j\omega}{4} = \frac{8}{4 + j\omega} + \frac{j\omega}{4}$$

$$= \frac{8(4 - j\omega)}{(4 + j\omega)(4 - j\omega)} + \frac{j\omega}{4} = \frac{32 - j\omega}{16 + \omega^2} + \frac{j\omega}{4}$$

$$= \frac{32 - 8j\omega}{16 + \omega^2} + \frac{j\omega(16 + \omega^2)}{4(16 + \omega^2)}$$

$$= \frac{32}{16 + \omega^2} + \frac{j\omega[\omega^2 + 16 - 32]}{4(16 + \omega^2)}$$

$$= \frac{32}{16 + \omega^2} + j \frac{\omega[\omega^2 - 16]}{4(\omega^2 + 16)}$$

$$a) \omega = 2 \frac{\text{rad}}{\text{s}} \quad Z = \frac{32}{20} + j \frac{-24}{80} = (1.6 - j0.3) \Omega = 1.63 \angle -10.62^\circ \Omega$$

$$b) \omega = 4 \frac{\text{rad}}{\text{s}} \quad Z = \frac{32}{32} + j \frac{0}{128} = (1 + j0) \Omega = 1 \angle 0^\circ \Omega$$

$$c) \omega = 8 \frac{\text{rad}}{\text{s}} \quad Z = \frac{32}{80} + j \frac{384}{320} = (0.4 + j1.2) \Omega = 1.26 \angle 71.57^\circ \Omega$$

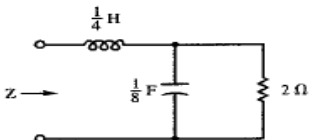


Fig. P4.13

3

4.18 For the circuit shown in Fig. P4.17, find the Thévenin equivalent of the circuit in the shaded box when $v_s(t) = 4 \cos(2t - 60^\circ)$ V. Use this to determine $v_o(t)$.

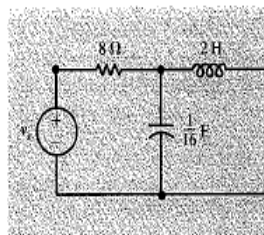


Fig. P4.17

$v_s = 4 \cos(2t - 60^\circ)$ V
 $\omega = 2$ rad/s

$S_o, V_{oc} \rightarrow$

$$V_{oc} = \frac{-j8}{8-j8} 4 \angle -60^\circ = \frac{8 \angle -90^\circ 4 \angle -60^\circ}{8\sqrt{2} \angle -45^\circ}$$

$$V_{oc} = 2\sqrt{2} \angle -105^\circ = 2\sqrt{2} \cos(2t - 105^\circ)$$
 V

$$Z_o = \frac{8 \angle -90^\circ \cdot j4}{8-j8} = j4 + \left(\frac{-64j}{8-j8} \right)$$

$$= j4 + \left(\frac{-8j}{1-j} \right) = j4 - \frac{8j(1+j)}{(1-j)(1+j)}$$

$$= j4 - \frac{8j-8}{1-j^2} = j4 - \frac{j8-8}{2}$$

$$Z_o = j4 - j4 + 4 = 4 \Omega$$

$$S_o, V_o(t) = \sqrt{2} \cos(2t - 105^\circ)$$
 V

4) 4.21

4.21 For the op-amp circuit shown in Fig. P4.21, find $v_o(t)$ when $v_s(t) = 6 \sin 2t$ V.

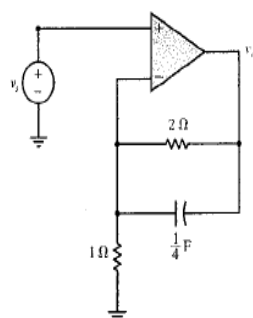


Fig. P4.21

$v_s = 6 \sin 2t$ Volts

Ideal op-amp: so $v_+ = v_-$
 $v_+ = 6 \sin 2t$

Let's write a KCL equation at v_- :

$$i_{R1} + i_C + i_{R2} = 0$$

$$\frac{v_+ - v_o}{2} + \frac{v_+ - v_o}{Z_C} + \frac{v_+}{1} = 0$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 2 \cdot \frac{1}{4}} = -j2 \Omega$$

$$v_+ = 6 \angle 0^\circ$$

$$S_o, \frac{v_+}{2} - \frac{v_o}{2} + \frac{v_+}{-j2} + \frac{v_o}{j2} + v_+ = 0$$

$$v_+ \left(\frac{1}{2} - \frac{1}{j2} + 1 \right) = v_o \left(\frac{1}{2} - \frac{1}{j2} \right)$$

$$v_o = \frac{v_+ \left(\frac{3}{2} + \frac{1}{2}j \right)}{\left(\frac{1}{2} + \frac{1}{2}j \right)} = \frac{6 \angle 0^\circ 1.58 \angle 18.43^\circ}{0.707 \angle 45^\circ}$$

$$= 13.4 \angle -26.57^\circ$$

$$v_o(t) = 13.4 \sin(2t - 26.57^\circ)$$
 Volts

5

4.25 Use mesh analysis to find I_1 and I_2 for the circuit given in Fig. P4.25 when $V_{s1} = 250\sqrt{2}\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}\angle -90^\circ$ V, and $Z = 26 - j15 \Omega$.

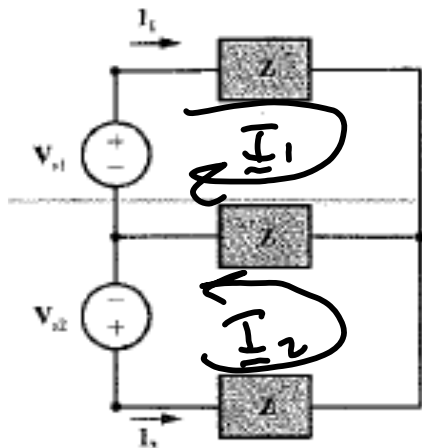


Fig. P4.25

KVL around 1st (top) loop:

$$V_{s1} = I_1 Z + (I_2 + I_1) Z$$

$$V_{s1} = 2I_1 Z + I_2 Z$$

$$2V_{s1} = 4I_1 Z + I_2 Z$$

$$-V_{s2} = -I_1 Z + I_2 Z$$

$$2V_{s1} - V_{s2} = 3I_1 Z \quad I_1 = \frac{500\sqrt{2}\left(\frac{\sqrt{3}}{2} - \frac{j}{2}\right) + 250\sqrt{2}j}{3 - 30\angle -30^\circ}$$

$$So, I_1 = \frac{250\sqrt{2}(\sqrt{3})}{90\angle -30^\circ} = 6.8\angle 30^\circ \text{ A}$$

From mesh analysis:

$$Z I_2 = V_{s1} - 2I_1 Z$$

$$I_2 = \frac{V_{s1} - 2I_1 Z}{Z} = \frac{V_{s1}}{Z} - \frac{2I_1}{1} = \frac{250\sqrt{2}\angle -30^\circ}{30\angle -30^\circ} - 2(6.8)\angle 30^\circ$$

$$= \frac{25\sqrt{2}}{\sqrt{3}} - 13.6\angle 30 = 11.8 - (11.8 + j6.8) = -j6.8$$

$$I_2 = 6.8\angle -90^\circ \text{ A}$$

4.32 For the op-amp circuit given in Fig. P4.22, when $v_s(t) = 3 \cos 2t$ V, then the output voltage $v_o(t) = 10.6 \cos(2t + 135^\circ)$ V. Find the average power absorbed by each element.


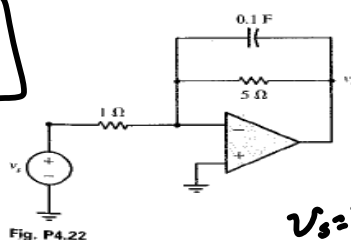


Fig. P4.22

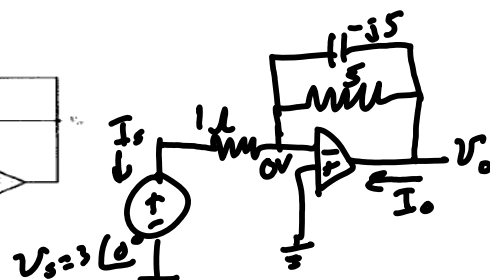

$$V_o = 10.6 \cos(2t + 135^\circ) \quad \omega = 2$$

$$V_s = 3\angle 0^\circ$$

6

$$1\Omega: P_1 = \frac{1}{2} \frac{|V_s|^2}{R_1} = \frac{1}{2} \cdot \frac{9}{1} = \frac{9}{2} = 4.5 \text{ W}$$

$$5\Omega: P_2 = P_{5\Omega} = \frac{1}{2} \frac{|V_{oc}|^2}{R_s} = \frac{1}{2} \frac{(10-6)^2}{5} = 11.2 \text{ W}$$

$$\text{Capacitor: } P_{avg} = 0 \text{ W (by inspection)}$$

$$I_o = \frac{0 - \underline{V}_o}{5} + \frac{0 - \underline{V}_o}{-j5} = -\frac{1}{5} \left[\underline{V}_o + \frac{-\underline{V}_o}{j} \right] = -\frac{1}{5} [\underline{V}_o + j \underline{V}_o]$$

$$\begin{aligned} I_o &= -\frac{1}{5} [10.6 \angle 135^\circ] (1+j) \\ &= \frac{10.6}{5} \angle -45^\circ \sqrt{2} \angle 45^\circ = 3 \angle 0^\circ \end{aligned}$$

$$\begin{aligned} \text{Op amp: } P_o &= \frac{1}{2} |V_o| |I_o| \cos(\text{ang}(V_o) - \text{ang}(I_o)) \\ &= \frac{1}{2} (10.6)(3) \cos(135^\circ) = -11.2 \text{ W} \end{aligned}$$

$$I_s = \frac{0 - \underline{V}_s}{1} = -3 \angle 0^\circ = 3 \angle 180^\circ$$

$$\text{For the voltage source: } P_s = \frac{1}{2} |V_s| |I_s| \cos[\text{ang}(V_s) - \text{ang}(I_s)]$$

$$P_s = \frac{1}{2} (3)(3) \cos(0 - 180^\circ)$$

$$P_s = -\frac{9}{2} = -4.5 \text{ W}$$

⑦

4.42 A 115-V rms, 60-Hz electric hair dryer absorbs 500 W at a lagging pf of 0.95. What is the rms value of the current drawn by this dryer?

$$P = V_e I_e \cos \theta = 115(I_e) \cos \theta$$

$$500 = 115(I_e) 0.95$$

$$\therefore I_e = 4.58 \text{ A rms}$$

Optional Problems

8. (0 points) FoEE 4.6

4.6 For the ac circuit shown in Fig. P4.6, suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ)$ V. Find $v_o(t)$ by using voltage division. Draw a phasor diagram. Is this circuit a lag network or a lead network?

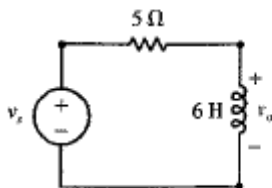


Fig. P4.6

FoEE 4.6

$v_s(t) = 13 \cos(2t - 22.6^\circ)$ Volts

$Z_L = j\omega L = j \cdot 2 \cdot 6 = j12$

$$v_o(t) = \frac{Z_L}{Z_R + Z_L} v_s(t)$$

$$V_o = \frac{j12}{5 + j12} 13 \angle -22.6^\circ$$

$$= \frac{12 \angle 90^\circ}{\sqrt{5^2 + 12^2} \angle \tan^{-1}(\frac{12}{5})} 13 \angle -22.6^\circ$$

$$= \frac{12 \cdot 13}{13} \angle 90^\circ - 22.6^\circ - 62.4^\circ$$

$$= 12 \angle 0^\circ$$

$v_o(t) = 12 \cos(2t)$ Volts

Phasor Diagram

Phase of $v_s = -22.6^\circ$
Phase of $v_o = 0^\circ$

\therefore Lead Network

9. (0 points) FoEE 4.17

4.17 For the circuit shown in Fig. P4.17, find the Thévenin equivalent of the circuit in the shaded box when $v_s(t) = 4 \cos(4t - 60^\circ)$ V. Use this to determine $v_o(t)$.


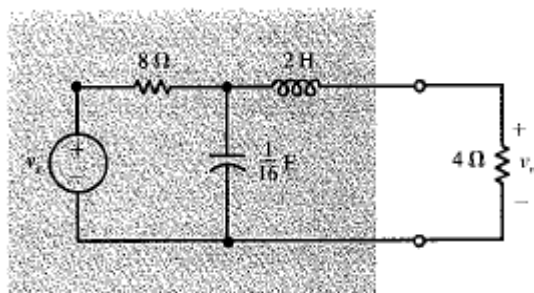



Fig. P4.17

$$v_{oc} = \frac{-j4}{8 - j4} 4 \angle -60^\circ = \frac{-j 4 \angle 60^\circ}{2 - j} = \frac{1 \angle -90^\circ 4 \angle -60^\circ}{\sqrt{5} \angle -26.6^\circ}$$

$$v_{oc} = 1.79 \angle -123^\circ \text{ Volts}$$

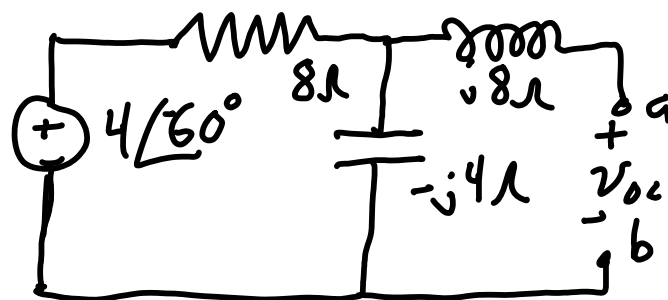First, we should find the freq. domain circuit



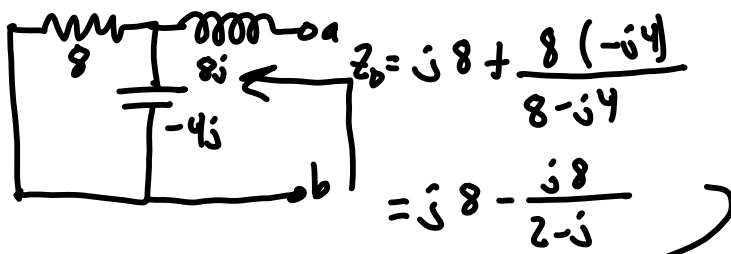


$$Z_0 = j8 + \frac{8(-j4)}{8-j4}$$

$$= j8 - \frac{j8}{2-j}$$

$$= \frac{j8(2-j) - j8}{2-j} = \frac{16j + 8 - j8}{2-j} = \frac{8j + 8}{2-j} = \frac{8(j+1)}{2-j} = \frac{8\sqrt{2} \angle 45^\circ}{\sqrt{5} \angle -26.6^\circ}$$
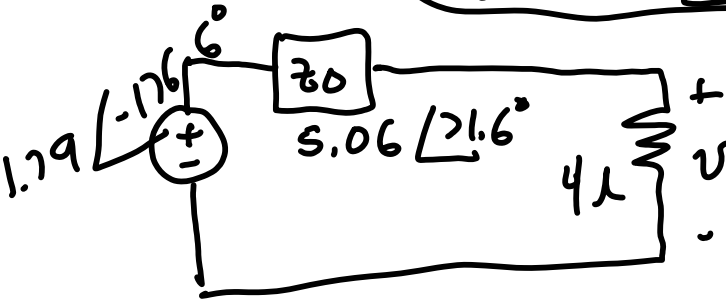
$$Z_0 = 5.06 \angle 71.6^\circ = 1.6 + j4.8$$




$$V_0 = \frac{4}{4 + (1.6 + j4.8)} \cdot 1.79 \angle -123^\circ = 0.97 \angle -164^\circ$$

$$V_0(t) = 0.97 \cos(4t - 164^\circ)$$

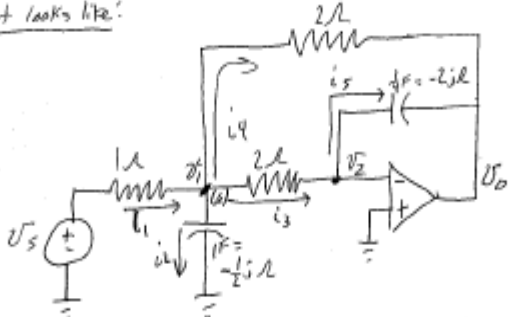10. (0 points) FoEE 4.23 **4.23** For the op-amp circuit shown in Fig. P4.23, find $v_o(t)$ when $v_s(t) = 4 \cos(2t - 30^\circ)$ V. (See p. 258.)

FoEE 4.23 Find power absorbed by 1 ohm resistor, each capacitor and for the op-amp.
 $V_s(t) = 4 \cos(2t - 30^\circ)$ So $V_s = 4 \angle -30^\circ$
 Circuit looks like:



KCL at node (a): $i_1 = i_2 + i_3 + i_4$ (1)
 KCL at node (b): $i_3 = i_5$ (2)

Using Ohm's Law (2) becomes: $\frac{V_1 - V_0}{2} = \frac{V_0 - V_0}{-2j}$

Since op-amp is ideal $V_1 = 0V$ So, $\frac{V_1 - V_0}{2} = \frac{-V_0}{-2j} \Rightarrow V_1 =$

Now, expanding (1) with Ohm's Law:

$$\frac{V_s - V_1}{1} = \frac{V_1}{-2j} + \frac{V_1 - V_0}{2} + \frac{V_1 - V_0}{2}$$

$$V_s + jV_0 = 2V_0 + \frac{-jV_0}{2} - \frac{jV_0}{2} - \frac{V_0}{2}$$

$$V_s = V_0 \left[\frac{3}{2} - 2j \right] \Rightarrow V_0 = \frac{4 \angle -30^\circ}{2.5 \angle -53.13^\circ}$$

So, $V_0 = 1.6 \angle 23.13^\circ$

$\therefore V_0(t) = 1.6 \cos(2t + 23.13^\circ)$ Volts

Avg. Power absorbed by 1 ohm resistor:

$P_R = \frac{1}{2} \frac{V^2}{R} = \frac{1}{2} V^2$ Here, V is the amplitude of the voltage across the resistor.

So $V_R = V_s - V_1$

$V_s = 4 \angle -30^\circ$ $V_1 = -jV_0 = 1.6 \angle -66.87^\circ$

When adding or subtracting phasors, we should have them in rectangular form.

So, $V_R = (3.46 - 2j) - (0.6285 - 1.47j)$
 $= 2.83 - 0.53j$

$V_R = 2.88 \angle -10.61^\circ$

So $P_R = \frac{1}{2} (2.88)^2 = 4.15$ W absorbed

Avg. Power absorbed by each capacitor = 0 W

Avg. Power is ALWAYS 0 across a capacitor or inductor.

$P_{1F} = 0W, P_{\frac{1}{2}F} = 0W$

Avg. Power absorbed by op-amp:

Direction depends on I_o

For power: $P_A = \frac{1}{2} |V_o| |I_o| \cos(\angle V_o - \angle I_o)$

$I_o = \frac{V_0}{-2j} + \frac{V_0 - V_1}{2} = \frac{V_0 j}{2} + \frac{V_0}{2} + \frac{jV_0}{2} = V_0 \left(\frac{1}{2} + j \right)$

So, $I_o = 1.6 \angle 23.13^\circ$ $1.12 \angle 63.43^\circ$
 $= 1.79 \angle 86.56^\circ$ Ams.


So $P_A = \frac{1}{2} |1.6| |1.79| \cos(23.13^\circ - 86.56^\circ) = 1.43 \cos(-63.43^\circ)$

$P_A = -0.6383$ W

This is negative power absorbed because the current is delivered by the op-amp!

FoEE 4.28

$$V_s = 10 \cos 3t$$

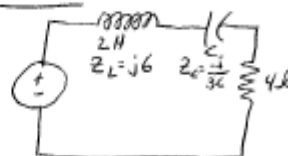

$$P_{\text{avg of resistor}} = \frac{1}{2} I_a^2 R$$

$$I_a = \frac{V_a}{Z_a} \quad \& \quad Z_T = j6 + 4 - \frac{j}{3}$$

$$= 4 + j\left(6 - \frac{1}{3}\right)$$

$$Z_a = \sqrt{16 + \left(6 - \frac{1}{3}\right)^2}$$

$$\text{So, } P_{\text{avg of resistor}} = \frac{1}{2} \frac{V_a^2}{Z_a^2} R = \frac{1}{2} \frac{100}{\left(16 + \left(6 - \frac{1}{3}\right)^2\right)} \cdot 4$$

$$= \frac{200}{\left(16 + \left(6 - \frac{1}{3}\right)^2\right)}$$

$$\text{So, (a) } C = \frac{1}{6} F \quad P = \frac{200}{16 + \left(6 - \frac{1}{3 \cdot 2}\right)^2} = \frac{200}{32} = 6.25 W$$

$$(b) C = \frac{1}{18} F \quad P = \frac{200}{16 + \left(6 - \frac{1}{3 \cdot 3}\right)^2} = \frac{200}{16} = 12.5 W$$

$$(c) C = \frac{1}{30} F \quad P = \frac{200}{16 + \left(6 - \frac{1}{3 \cdot 30}\right)^2} = \frac{200}{32} = 6.25 W.$$