

Chapter 11: Field effect Transistors: Operation, Circuit, Models, and Applications – Instructor Notes

Chapter 11 introduces field-effect transistors. **Should the instructor choose to only teach field-effect devices (or to cover FETs before BJTs), Section 10.1 can be used as an introductory section prior to starting Chapter 11.**

Section 11.1 briefly reviews the classification and symbols for the major families of field-effect devices. Section 11.2 introduces the fundamental ideas behind the operation of N-channel field-effect enhancement-mode transistors. A brief explanation of P-channel devices is also presented in this section. Section 11.3 , illustrates the calculation of the state and operating point of basic field-effect transistor circuits. Section 11.4 outlines the operation of MOSFET large-signal amplifiers, and presents two practical examples (11.6 and 11.7), related to a battery charging circuit and a DC motor drive circuit. These examples are analogous to those presented in Chapter 10 for BJT large-signal amplifiers, giving the instructor the opportunity to make a comparison of the two technologies, if so desired. Finally, Section 11.5 introduces the analysis of MOSFET switches and presents CMOS gates. The box *Focus on Measurements: MOSFET bidirectional analog gate* (pp. 572-573) presents an analog application of CMOS technology.

The end-of-chapter problems are straightforward applications of the concepts illustrated in the chapter. The 5th Edition of this book includes 13 new problems; some of the 4th Edition problems were removed, increasing the end-of-chapter problem count from 23 to 35.

Learning Objectives

1. Understand the classification of field-effect transistors. *Section 11.1.*
2. Learn the basic operation of enhancement-mode MOSFETs by understanding their i - v curves and defining equations. *Section 11.2.*
3. Learn how enhancement-mode MOSFET circuits are biased. *Section 11.3.*
4. Understand the concept and operation of FET large-signal amplifiers. *Section 11.4*
5. Understand the concept and operation of FET switches. *Section 11.5.*
6. Analyze FET switches and digital gates. *Section 11.5.*

Section 11.2: n-channel MOSFET Operation

Problem 11.1

Solution:

Known quantities:

For the transistors shown in Figure P11.1, $|V_T| = 3 \text{ V}$.

Find:

The operating state of each transistor.

Analysis:

- a) This is an n-channel enhancement MOSFET, with $V_T = -3 \text{ V}$. To operate in the triode region, the condition is: $v_{DS} < v_{GS} - V_T$. To operate in the saturation region, the condition is: $v_{DS} \geq v_{GS} - V_T$. To turn the transistor on, the condition is: $v_{GS} > V_T$.

$$\begin{aligned} \text{We can compute: } v_{GS} &= -2.5 \text{ V} & v_{DS} &= 2.5 \text{ V} & v_{GS} - V_T &= -2.5 + 3 = 0.5 \text{ V} \\ v_{DS} &= 2.5 \text{ V} > v_{GS} - V_T & & & & = 0.5 \text{ V}. \end{aligned}$$

Therefore, the transistor is in the saturation region.

- b) This is a p-channel enhancement MOSFET, with $V_T = 3 \text{ V}$. To operate in the triode region, the condition is: $v_{DS} > v_{GS} - V_T$. To operate in the saturation region, the condition is: $v_{DS} \leq v_{GS} - V_T$. To turn the transistor on, the condition is: $v_{GS} < V_T$.

$$\begin{aligned} \text{We can compute: } v_{GS} &= 2 \text{ V} & v_{DS} &= -1 \text{ V} & v_{GS} - V_T &= 2 - 3 = -1 \text{ V} \\ v_{DS} &= -1 \text{ V} > v_{GS} - V_T & & & & = -1 \text{ V}. \end{aligned}$$

Therefore, the transistor is in the saturation region.

- c) This is a p-channel enhancement MOSFET, with $V_T = -3 \text{ V}$. To operate in the triode region, the condition is: $v_{DS} > v_{GS} - V_T$. To operate in the saturation region, the condition is: $v_{DS} \leq v_{GS} - V_T$. To turn the transistor on, the condition is: $v_{GS} < V_T$.

$$\begin{aligned} \text{We can compute: } v_{GS} &= -5 \text{ V} & v_{DS} &= -1 \text{ V} & v_{GS} - V_T &= -5 + 3 = -2 \text{ V} \\ v_{DS} &= -1 \text{ V} > v_{GS} - V_T & & & & = -2 \text{ V}. \end{aligned}$$


Therefore, the transistor is in the triode region.

- d) This is an n-channel enhancement MOSFET, with $V_T = -3 \text{ V}$. To operate in the triode region, the condition is: $v_{DS} < v_{GS} - V_T$. To operate in the saturation region, the condition is: $v_{DS} \geq v_{GS} - V_T$. To turn the transistor on, the condition is: $v_{GS} > V_T$.

$$\begin{aligned} \text{We have: } v_{GS} &= -2 \text{ V} > V_T. \\ v_{GS} - V_T &= -2 + 3 = 1 \text{ V} \\ v_{DS} &= 6 \text{ V} > v_{GS} - V_T = 1 \text{ V} \end{aligned}$$

Therefore, the transistor is in the saturation region.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

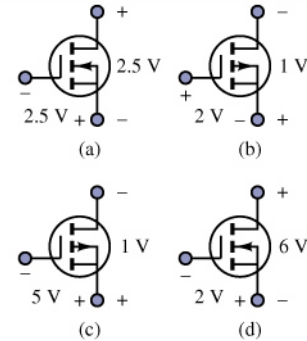

Problem 11.2

Solution:

Known quantities:

The potentials of an n-channel enhancement-mode MOSFET (4, 5, and 10 V respectively).

Find:


The circuit symbol, if the device is operating:

- In the ohmic state.
- In the active region.

Analysis:


- To operate in the ohmic region, the condition is: $v_{DS} < v_{GS} - V_T$ and $V_T > 0$, $v_{DS} > 0$.

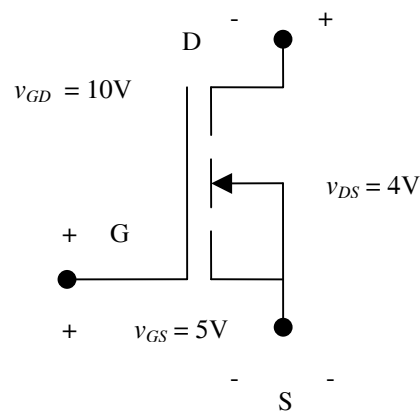The circuit for operation in the ohmic region is shown below.



- To operate in the active region, the condition is: $v_{DS} \geq v_{GS} - V_T$ and $V_T > 0$, $v_{DS} > 0$.

The circuit for operation in the active region is shown below.

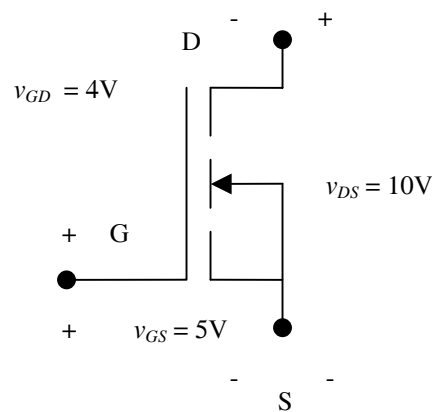

Problem 11.3

Solution:

Known quantities:

The threshold voltage, $V_T = 2$ V, of an enhancement-type NMOS that has its source grounded and a 3 V DC source connected to the gate.

Find:

The operating state if:

- a) $v_D = 0.5$ V .
- b) $v_D = 1$ V .
- c) $v_D = 5$ V

Analysis:

$$v_{DS} = v_D = 0.5 \text{ V}$$

a) $v_{GS} - V_T = 3 - 2 = 1 \text{ V}$

$$v_{DS} < v_{GS} - V_T$$

The transistor is in the triode region.

$$v_{DS} = v_D = 1 \text{ V}$$

b) $v_{GS} - V_T = 3 - 2 = 1 \text{ V}$

$$v_{DS} = v_{GS} - V_T$$

The transistor is either in the triode or in the saturation region.

$$v_{DS} = v_D = 5 \text{ V}$$

c) $v_{GS} - V_T = 3 - 2 = 1 \text{ V}$

$$v_{DS} > v_{GS} - V_T$$

The transistor is in the saturation region.

Problem 11.4

Solution:

Known quantities:

The threshold voltage, $V_T = 2$ V, of the p-channel transistor shown in Figure P11.4. $k = 10$ mA/V².

Find:

R and v_D for $i_d = 0.4$ mA.


Analysis:

The device shown is a p-channel enhancement mode MOSFET, with $V_T = 2$ V and $V_{DG} = 0$ V. To operate in the saturation region we require: $v_{DS} \geq v_{GS} - V_T$.

Since $v_{DG} = v_{DS} - v_{GS} = 0 > -V_T = -2$ V, the transistor is in the saturation region. Knowing $k = 10$ mA/V², we can write: $0.4 = 10(v_{GS} - 2)^2$ and determine $v_D = v_{DS} = v_{GS} = 2.2$ V. R can be found as follows:

$$R = \frac{20 - v_D}{i_D} = \frac{20 - 2.2}{0.4 \cdot 10^{-3}} = 44.5 \text{ k}\Omega$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

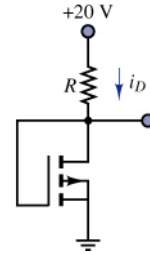

Problem 11.5

Solution:

Known quantities:

The threshold voltage, $V_T = 2$ V, of an enhancement-type NMOS transistor. $i_D = 1$ mA when $v_{GS} = v_{DS} = 3$ V.

Find:

The value of i_D for $v_{GS} = 4$ V.

Analysis:

Because $v_{DS} > v_{GS} - V_T$, the transistor is in the saturation region:

$$i_D = k \cdot (v_{GS} - V_T)^2 = k \cdot (3 - 2)^2 = 0.001 \text{ A}$$

$$\Rightarrow k = 0.001.$$

For $v_{GS} = 4$ V we have:

$$i_D = 0.001 \cdot (4 - 2)^2 = 4 \text{ mA}.$$

Problem 11.6

Solution:

Known quantities:

Characteristics of an n-channel enhancement-mode MOSFET operated in the ohmic region:

$$v_{DS} = 0.4 \text{ V}, V_T = 3.2 \text{ V}. \text{ Effective resistance of the channel, given by: } R_{DS} = \frac{500}{(v_{GS} - 3.2)} \Omega.$$

Find:

The value of i_D when $v_{GS} = 5 \text{ V}$, $R_{DS} = 500 \Omega$, and $v_{GD} = 4 \text{ V}$.

Analysis:

Since $V_{DS} = 0.4 < v_{GS} - V_T = 5 - 3.2 = 1.8 \text{ V}$, the transistor is operating in the ohmic region. The effective resistance is: $R_{DS} = \frac{500}{(5 - 3.2)} = 277.78 \Omega$. Since $R_{DS} = \frac{V_{DS}}{i_D}$, we have: $i_D = \frac{V_{DS}}{R_{DS}} = 1.44 \text{ mA}$.

Problem 11.7

Solution:

Known quantities:

The threshold voltage, $V_T = 2.5 \text{ V}$, of an enhancement-type NMOS that has its source grounded and a 4 V DC source connected to the gate.

Find:

The operating state if:

- a) $v_D = 0.5 \text{ V}$
- b) $v_D = 1.5 \text{ V}$

Analysis:

- a) $v_{DS} = 0.5 < v_{GS} - V_T = 4 - 2.5 = 1.5 \text{ V}$, therefore the transistor is in the triode region.
 - b) $v_D = 1.5 \text{ V} = v_{DS}$, therefore the transistor is at the border of the saturation and triode regions.
-

Problem 11.8

Solution:

Known quantities:

The threshold voltage, $V_T = 4$ V, of an enhancement-type NMOS. $i_D = 1$ mA when $v_{GS} = v_{DS} = 6$ V.

Find:

The value of i_D when $v_{GS} = 5$ V.

Analysis:

From $0.001 = k(6 - 4)^2$, we have $k = 0.25 \times 10^{-3}$

For $v_{GS} = 5$ V, and assuming active operation: $i_D = 0.25 \times 10^{-3}(5 - 4)^2 = 0.25$ mA.

Problem 11.9

Solution:

Known quantities:

The threshold voltage, $V_T = 1.5$ V, of the NMOS transistor shown in Figure P11.9. $k = 0.4$ mA/V².

Find:

The voltage levels of the pulse signal at the drain output, if v_G is a pulse with 0 V to 5 V.


Analysis:

Since $V_T = 1.5$ V, with $v_G = 0$ V, $v_{GS} < V_T$, the transistor is cut off. Therefore, $v_D = 5$ V.

When $v_G = 5$ V, and assuming that the transistor is in the active region:

$i_D = k(v_{GS} - V_T)^2 = 0.4(5 - 1.5)^2 = 4.9$ mA. Therefore, $v_D = 5 - 4.9 \times 1 = 0.1$ V.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

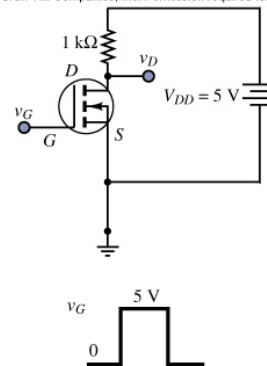

Problem 11.10**Solution:****Known quantities:**

Circuit shown in Figure 11.10.

Find:Find the current i_D .**Analysis:**


In the circuit of Figure P11.10,

$$v_{DS} = 0.1 < v_{GS} - V_T = 14 \text{ V},$$

therefore the transistor is in the ohmic region. We can compute the drain current to be:

$$\begin{aligned} i_D &= K \left[2(v_{GS} - V_T)v_{DS} - v_{DS}^2 \right] \\ &= 0.5 \times 10^{-3} \left[2(15 - 1) \times 0.1 - (0.1)^2 \right] = 1.395 \text{ mA} \end{aligned}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

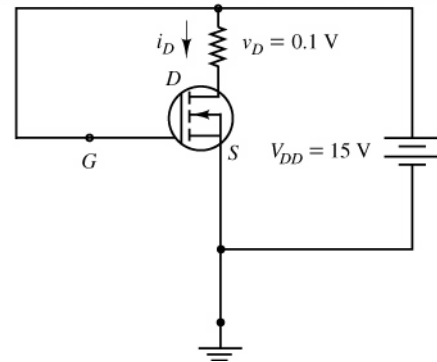**Problem 11.11****Solution:****Known quantities:**

In the circuit shown in Figure P11.11, the MOSFET operates in the active region.

Find:

- R_D
- The largest allowable value of R_D for the MOSFET to remain in the saturation region.

Analysis:Since the transistor is in the saturation region and $i_D = 0.5 \text{ mA}$, we have

$$\begin{aligned} i_D &= K(v_{GS} - V_T)^2 \\ 0.5 &= 0.5(v_{GS} + 1)^2 \end{aligned}$$

and $v_{GS} = -2 \text{ V}$; $v_{GS} < V_T = -1$. Since the source is at 10 V , the gate voltage must be 8 V . Thus, we can select $R_1 = 1 \text{ M}\Omega$ and $R_2 = 4 \text{ M}\Omega$ to obtain this operating condition.

(a) R_D can be found to be

$$R_D = \frac{V_D}{i_D} = \frac{8 \text{ V}}{0.5 \text{ mA}} = 16 \text{ k}\Omega$$


(b) Saturation region operation would be maintained when V_D exceeds V_G by $|V_T|$,

$$V_{D_{\max}} = 8 + 1 = 9 \text{ V}$$

Therefore,

$$R_{D_{\max}} = \frac{V_{D_{\max}}}{0.5} = 18 \text{ k}\Omega$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

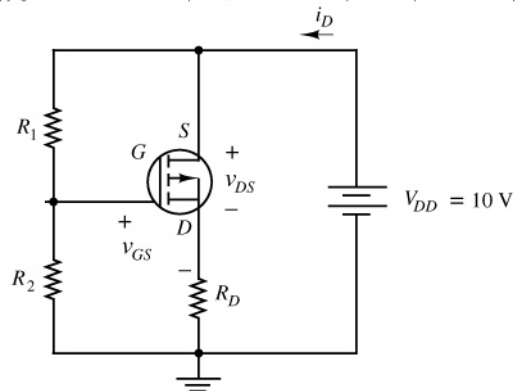

Problem 11.12

Solution:

Known quantities:

An enhancement-type MOSFET has the parameters $K = 0.5 \text{ mA/V}^2$ and $V_T = 1.5 \text{ V}$, and the transistor is operated at $v_{GS} = 3.5 \text{ V}$.

Find:

- a) The drain current obtained at $v_{DS} = 3 \text{ V}$.
- b) The drain current obtained at $v_{DS} = 10 \text{ V}$.

Analysis:

(a) $V_{DS} = 3 > V_{GS} - V_T = 3.5 - 1.5 = 2 \text{ V}$

$$i_D = K(V_{GS} - V_T)^2 = 0.5 \times 10^{-3} \times 4 = 2 \text{ mA}$$

(b) $V_{DS} = 10 > V_{GS} - V_T = 2 \text{ V}$

$$i_D = K(V_{GS} - V_T)^2 = 0.5 \times 10^{-3} \times 4 = 2 \text{ mA}$$

Section 11.3: MOSFET Amplifiers

Problem 11.13

Solution:

Known quantities:

The i - v characteristic of Figure P11.13(a), and the circuit in Figure P11.13(b): $V_{GG} = 7\text{ V}$, $V_{DD} = 10\text{ V}$, $R_D = 5\Omega$

Find:

The current i_{DQ} the voltage v_{DSQ} , and the region of operation of the MOSFET.

Analysis:

The operating point can be determined using the load line method.



$$i_D = \frac{V_{DD}}{R_D} - \frac{v_{DS}}{R_D} = 2 - 0.2 v_{DS}$$

By superimposing the load line on Figure P11.13(a), and by noticing that $V_{GS} = V_{GG} = 7\text{ V}$, we obtain

$$i_{DQ} = 0.8\text{ A}, v_{DSQ} = 6\text{ V}$$

The MOSFET is in the saturation region.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

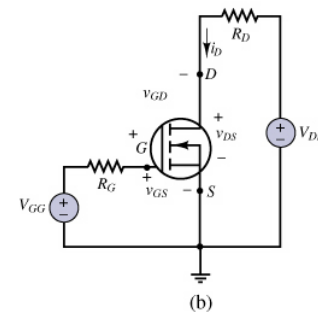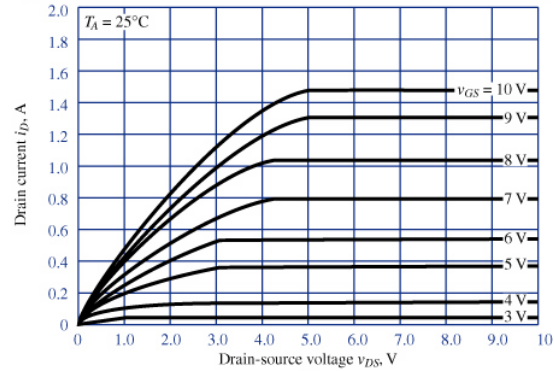

Problem 11.14

Solution:

Known quantities:

The circuit in Figure P11.13(b):

$$V_{GG} = 7\text{ V}, V_{DD} = 20\text{ V}, V_T = 3\text{ V}, R_D = 5\Omega, K = 50\text{ mA/V}^2$$

Find:

The current i_{DQ} the voltage v_{DSQ} , and the region of operation of the MOSFET.

Analysis:

Assuming that the MOSFET is in the saturation region, the quiescent drain current is

$$i_{DQ} = K(v_{GSQ} - V_T)^2 = 0.05(7 - 3)^2 = 0.8\text{ A}$$

The drain-to-source voltage is

$$v_{DSQ} = V_{DD} - R_D i_{DQ} = 20 - 5 \cdot 0.8 = 16\text{ V}$$

Since $v_{DG} = v_{DS} - v_{GS} = 9\text{ V} > V_T \Rightarrow$ hypothesis was correct

Problem 11.15

Solution:

Known quantities:

The circuit in Figure 11.9 in the text:

$$V_{DD} = 36 \text{ V}, V_T = 4 \text{ V}, R_D = 10 \text{ k}\Omega, R_1 = R_2 = 2 \text{ M}\Omega, K = 0.1 \text{ mA/V}^2$$

Find:

The current i_{DQ} , the voltage v_{DSQ} , the resistance R_S , and the operating region of the MOSFET.

Analysis:

Using Thevenin equivalent,

$$V_{GG} = \frac{R_2}{R_1 + R_2} V_{DD} = 18 \text{ V}$$

We can write the equations

$$V_{GG} = v_{GSQ} + R_S i_{DQ} = 18,$$

$$V_{DD} = (R_D + R_S) i_{DQ} + v_{DSQ} = R_D i_{DQ} + 18 - v_{GSQ} + v_{DSQ} = 36 \Rightarrow R_D i_{DQ} + v_{DSQ} = 18 + v_{GSQ}$$

Assuming saturation conditions, the current i_D can be written as

$$i_{DQ} = K(v_{GSQ} - V_T)^2 \Rightarrow v_{GSQ} + R_S K(v_{GSQ} - V_T)^2 = 18$$

and

$$R_D K(v_{GSQ} - V_T)^2 + v_{DSQ} = 18 + v_{GSQ}$$

Notice that the problem has more unknown than equations; we can impose the v_{DSQ} to ensure saturation conditions as

$$v_{DSQ} = V_{DD} / 2 = 18 \text{ V} \Rightarrow$$

$$(v_{GSQ} - V_T)^2 = v_{GSQ} \Rightarrow v_{GSQ}^2 - 9v_{GSQ} + 16 = 0 \Rightarrow v_{GSQ} = 6.56 \text{ V}$$

Remark: The other solution of the algebraic equation is not acceptable because $< V_T$.

The resistance R_S is given by

$$R_S = \frac{18 - v_{GSQ}}{K(v_{GSQ} - V_T)^2} = \frac{18 - 6.56}{0.1 \cdot 10^{-3} (6.56 - 4)^2} = 17.45 \text{ k}\Omega$$

and the drain current

$$i_{DQ} = K(v_{GSQ} - V_T)^2 = 0.655 \text{ mA}$$

Problem 11.16

Solution:

Known quantities:

The circuit in Figure P11.16:

$$V_{DD} = 12 \text{ V}, V_T = 1 \text{ V}, R_S = R_D = 10 \text{ k}\Omega, R_1 = R_2 = 2 \text{ M}\Omega, K = 1 \text{ mA/V}^2$$

Find:

The current i_{DQ} , the voltage v_{DSQ} , and the voltage v_{GSQ} .

Analysis:

Using Thevenin,

$$V_{GG} = \frac{R_2}{R_1 + R_2} V_{DD} = 6 \text{ V}$$

We can write the equations

$$V_{GG} = v_{GSQ} + R_S i_{DQ} = 6,$$

$$V_{DD} = (R_D + R_S) i_{DQ} + v_{DSQ} = 2R_D i_{DQ} + v_{DSQ} = 12$$

Assuming saturation conditions, the current i_D can be written as

$$i_{DQ} = K(v_{GSQ} - V_T)^2 \Rightarrow v_{GSQ} + R_S K(v_{GSQ} - V_T)^2 = 6 \Rightarrow 10v_{GSQ}^2 - 19v_{GSQ} + 4 = 0 \Rightarrow$$

$$v_{GSQ} = 1.66 \text{ V}$$

The other solution is not acceptable because less than V_T .

It follows

$$i_{DQ} = \frac{6 - v_{GSQ}}{R_S} = 0.434 \text{ mA},$$

$$v_{DSQ} = 12 - 2R_D i_{DQ} = 3.32 \text{ V}$$

Problem 11.17

Solution:


Known quantities:

The power MOSFET circuit shown in Figure P11.17.

Find:

- If $V_G = 5 \text{ V}$, find the range of R_L for which the VCCS will operate.
- If $R_L = 1 \Omega$, determine the range of V_G for which the VCCS will operate.

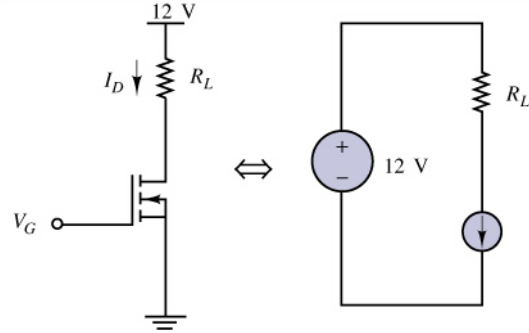Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Analysis:

The MOSFET should be working in the saturation region, so $v_{GD} < 3 \Rightarrow V_D > V_G - 3$

$$\text{a) } V_G = 5 \text{ V, } I_D = K(v_{GS} - V_T)^2 = 1.5(5 - 3)^2 = 6 \text{ A so}$$

$$V_D = 12 - R_L I_D > V_G - 3 = 2 \Rightarrow R_L < \frac{10}{6} \Omega$$

$$\text{b) } V_D = 12 - R_L I_D > V_G - 3 \Rightarrow V_G < 9 - R_L I_D = 9 - I_D$$

$$I_D = K(v_{GS} - V_T)^2 = K(V_G - V_T)^2$$

Solve the above two equations, we can have

$$I_D = 8.36 \text{ A or } I_D = 4.31 \text{ A}$$

Obviously, the second one is reasonable, so

$$V_G < 9 - I_D = 4.69 \text{ V}$$

Problem 11.18

Solution:


Known quantities:

The circuit in Figure P11.18:

Find:

- Determine I_L if $V_{DD} = 12 \text{ V}$, $V_G = 10 \text{ V}$, $V_T = 4 \text{ V}$, $R_L = 2 \Omega$, $K = 0.5 \text{ A/V}^2$
- If the power rating of the MOSFET is 50 W, how small can R_L be.

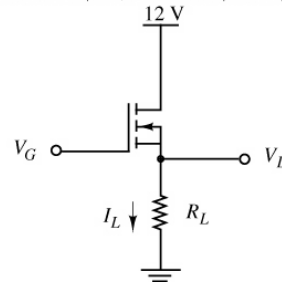Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Analysis:

a) Since $v_{GD} = 10 - 12 < V_T = 4 \text{ V}$, MOSFET is working in the saturation region

$$V_L = V_G - V_T = 10 - 4 = 6 \text{ V}$$

$$\text{So } I_L = \frac{V_L}{R_L} = \frac{6}{2} = 3 \text{ A}$$

$$\text{b) } P_{\max} = v_{DS} I_D = 50 \text{ W} \Rightarrow I_{L\max} = I_D = \frac{P_{\max}}{v_{DS}} = \frac{50}{12 - 6} = 8.33 \text{ A}$$

$$\text{So, } R_{L\min} = \frac{V_L}{I_{L\max}} = \frac{6}{8.33} = 0.72 \Omega$$

Problem 11.19


Solution:

Known quantities:

The Class A amplifier shown in Figure P11.19

Find:

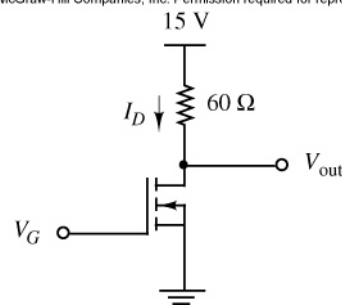- Determine the output current for the given biased audio tone input, $V_G = 10 + 0.1 \cos(500t)$ V. Let $K = 2 \text{ mA/V}^2$ and $V_T = 3 \text{ V}$.
- Determine the output voltage.
- Determine the voltage gain of the $\cos(500t)$ signal.
- Determine the DC power consumption of the resistor and the MOSFET.



Analysis:

- The MOSFET should be working at the saturation region

$$\text{So } i_D = K(v_{GS} - V_T)^2 = 0.002(10 + 0.1 \cos(500t) - 3)^2 = 0.002(49 + 1.4 \cos(500t) + 0.01 \cos^2(500t)) \\ = 0.002(49 + 1.4 \cos(500t) + 0.005 \cos(1000t) + 0.005) \text{ A}$$

$$\text{b) } V_{out} = V_{DD} - i_D R = 15 - 60 \times 0.002(49 + 1.4 \cos(500t) + 0.005 \cos(1000t) + 0.005) \text{ V}$$

$$\text{c) } \text{gain} = \left. \frac{V_{out}}{V_G} \right|_{\omega=500} = \frac{-60 \times 0.002 \times 1.4}{0.1} = -1.68$$

- We can ignore the cosine part signal when calculating the DC power consumption.

$$i_{D_DC} = 0.002(49 + 0.005) = 0.098 \text{ A}$$

$$P_R = i_{D_DC}^2 \times R = 0.576 \text{ W}$$

$$P_{MOSFET} = i_{D_DC} \times v_{DS} = i_{D_DC} \times (V_{DD} - i_{D_DC} \times R) = 0.098 \times (15 - 0.098 \times 60) = 0.894 \text{ W}$$

Problem 11.20

Solution:


Known quantities:

The source-follower amplifier shown in Figure P11.20.

$$V_G = 9 + 0.1 \cos(500t) \text{ V}, K = 30 \text{ mA/V}^2 \text{ and } V_T = 4 \text{ V}$$

Find:

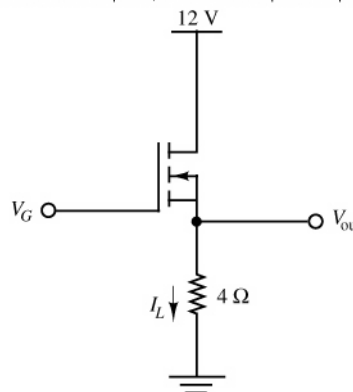- Determine the load current I_L .
- Determine the output voltage.
- Determine the voltage gain of the $\cos(500t)$ signal.
- Determine the DC power consumption of the resistor and the MOSFET.



Analysis:

The MOSFET should be working at the saturation region, So the $V_{out} = V_S = v_{GS} - V_T = 5 + 0.1 \cos(500t)$

$$\text{a) } I_L = \frac{V_{out}}{R} = \frac{5 + 0.1 \cos(500t)}{4} = 1.25 + 0.025 \cos(500t)$$

$$c) \text{ gain} = \frac{V_{out}}{V_G} \bigg|_{\omega=500} = \frac{0.1}{0.1} = 1$$

d) We can ignore the cosine part signal when calculating the DC power consumption.

$$i_{D_DC} = 1.25 \text{ A}$$

$$P_R = i_{D_DC}^2 \times R = 6.25 \text{ W}$$

$$P_{MOSFET} = i_{D_DC} \times v_{DS} = i_{D_DC} \times (V_{DD} - i_{D_DC} \times R) = 1.25 \times (12 - 5) = 8.75 \text{ W}$$

Problem 11.21

Solution:

Known quantities:

The circuit shown in Figure P11.21.

$$V_G = 8 \text{ V}, K = 4 \text{ A/V}^2 \text{ and } V_T = 3 \text{ V}$$

Find:

The discharging current I_D and the required MOSFET power rating.


Analysis:

Obviously, the MOSFET should be working in the saturation region.

$$i_D = K(v_{GS} - V_T)^2 = 4(8 - 3)^2 = 100 \text{ A}$$

$$P = v_{DS} \times i_D = (12.7 - R \times i_D) \times i_D = (12.7 - 0.002 \times 100) \times 100 = 1250 \text{ W}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

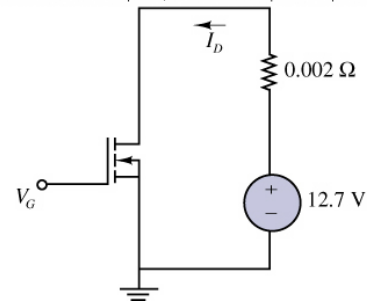

Problem 11.22

Note: the value of K should be 0.006 A/V^2 , not mA/V^2 .

Solution:

Known quantities:

The circuit shown in Figure P11.22.

Find:

Determine the output V_G .


Analysis:

Obviously, the MOSFET should be working in the saturation region.

$$i_D = K(v_{GS} - V_T)^2$$

$$V_G = V_T + \sqrt{\frac{i_D}{K}} = 1.5 + \sqrt{\frac{0.01}{0.006 \times 10^{-3}}} = 1.5 + 1.29 = 2.79 \text{ V}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

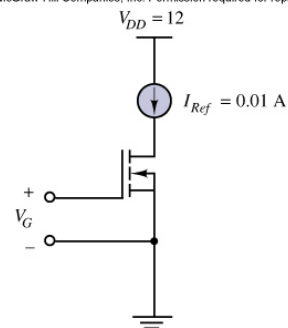

Problem 11.23

Solution:

Known quantities:

The circuit shown in Figure P11.23.

Find:

Determine the load current in each of the circuits.

Analysis:

- a) In the figure of left hand side, resistance is connected to the drain

Assume that the drain current in each MOSFET is i_D , then the current through the resistance is $2i_D$

Obviously, the MOSFET is working at the saturation region, so

$$i_D = K(v_{GS} - V_T)^2 = K(V_G - V_T)^2$$

$$\text{And } v_{GD} = V_G - V_D = V_G - V_{DD} + I_L R_L < V_T$$

Solve the equations above, we can get the current

- b) In the figure of right hand side, resistance is connected to the source


Assume that the drain current in each MOSFET is i_D , then the current through the resistance is $2i_D$

Obviously, the MOSFET is working in the saturation region, so

$$i_D = K(v_{GS} - V_T)^2 = K(V_G - I_L R_L - V_T)^2$$

$$\text{And } v_{GD} = V_G - V_D = V_G - V_{DD} < V_T, \text{ and } v_{GS} = V_G - V_S = V_G - I_L R_L > V_T$$

Solving the equations above, we can get the current

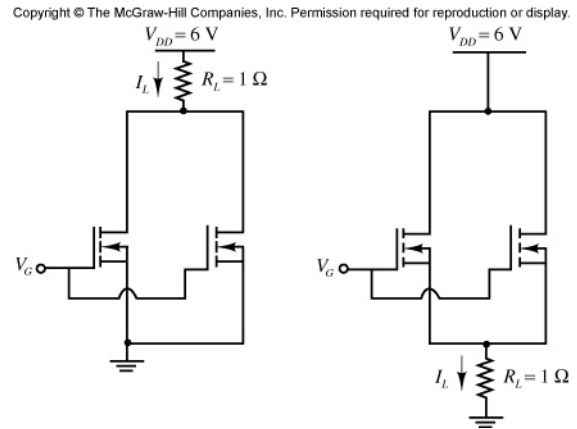

Problem 11.24

Solution:

Known quantities:

A “push-pull amplifier” can be constructed from matched n-and-p-channel MOSFETs, shown in Figure P11.24.

Find:


Determine V_L and I_L .

Analysis:

If $V_L < V_{in}$, the output of the operational amplifier is positive infinity, so both MOSFETs will work in the triode region and the V_L will increase, until it reaches $V_L = V_{in}$;

If $V_L > V_{in}$, the output of the operational amplifier is negative infinity, so both two MOSFET will work in cutoff region, and the V_L will increase, until it reaches $V_L = V_{in}$; So $V_L = V_{in}$ is the only equilibrium in the system, so

$$V_L = V_{in}. \text{ Correspondingly, } I_L = \frac{V_L}{R_L} = 2V_L$$

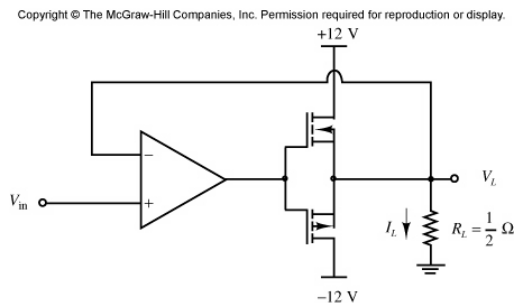

Problem 11.25**Solution:****Known quantities:**

The circuit shown in Figure 11.25.

Find:


Determine the $V - I$ characteristics of the voltage controlled resistance.

Analysis:

Since the gate is connected to the drain, the MOSFET can either work in the saturation region or cutoff region, dependant on whether $V_G \geq V_S$

$$\text{So, } I = \begin{cases} K(V - V_T)^2, & V \geq V_T \\ 0, & V < V_T \end{cases}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

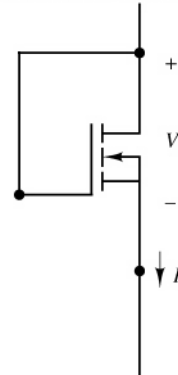**Problem 11.26****Solution:****Known quantities:**

The two-stage amplifier shown in the circuit of Figure P11.26.

Find:

- Determine the V_L and I_L for $V_G = 4$ V
- Determine the V_L and I_L for $V_G = 5$ V
- Determine the V_L and I_L for $V_G = 4 + 0.1\cos(750t)$ V

Analysis:

Assume the drain current in the MOSFET in the left hand side is i_{D1} and in the right hand side i_{D2} . Obviously, both MOSFET are working in saturation region.

$$\text{a) } i_{D1} = K(v_{GS1} - V_T)^2 = K(V_{G1} - V_T)^2 = 1 \text{ A}$$

$$V_{G2} = V_{D1} = V_{DD} - R \times i_{D1} = 12 - 2 \times 1 = 10 \text{ V}$$

$$i_{D2} = K(v_{GS2} - V_T)^2 = K(V_{G2} - R \times i_{D2} - V_T)^2$$

$$\text{Solve it and we can have } i_{D2} = 2.68 \text{ or } 4.57 \text{ A}$$

Obviously, the first solution is reasonable, so $I_L = i_{D2} = 2.68$ A and $V_L = R \times I_L = 5.36$ V

$$\text{b) } i_{D1} = K(v_{GS1} - V_T)^2 = K(V_{G1} - V_T)^2 = 4 \text{ A} \quad V_{G2} = V_{D1} = V_{DD} - R \times i_{D1} = 12 - 2 \times 4 = 4 \text{ V}$$

$$i_{D2} = K(v_{GS2} - V_T)^2 = K(V_{G2} - R \times i_{D2} - V_T)^2 \text{ Solve it and we can have } i_{D2} = 0.25 \text{ or } 1 \text{ A}$$


Obviously, the first solution is reasonable, so $I_L = i_{D2} = 0.25$ A and $V_L = R \times I_L = 0.5$ V

c) Basically, the signal in c) part is a comparably small cosine signal superposed by the signal the in a) part. If we ignore the harmonics larger than 1st order, we can approximately have the following solution

$$i_{D1} = 1 - 0.2\cos(750t) \text{ A} \quad V_{G2} = 10 + 0.4\cos(750t) \text{ V}$$

$$I_L = i_{D2} = 2.68 - 1.31\cos(750t) \text{ A} \quad V_L = 5.36 - 2.62\cos(750t) \text{ V}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

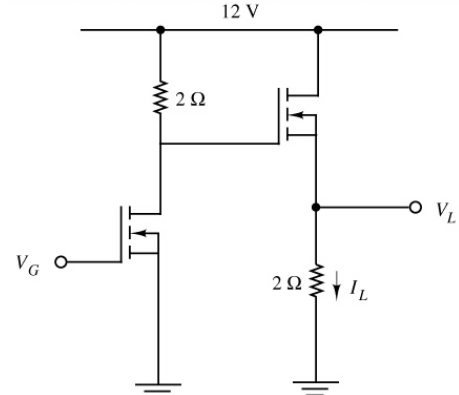

Section 11.4: MOSFET Switches

Problem 11.27

Solution:

Known quantities:

The CMOS NAND gate of Figure 11.23 in the text.

Find:

Identify the state of each transistor for $v_1 = v_2 = 5\text{ V}$.

Analysis:

The two transistors at the top are cut off and the two at the bottom are on.

Problem 11.28

Solution:

Known quantities:

The CMOS NAND gate of Figure 11.23 in the text.

Find:

Identify the state of each transistor for $v_1=5\text{V}$, $v_2=0\text{V}$.

Analysis:

The transistor at the bottom and the first on the top are off, the other two are on.

Problem 11.29

Solution:

Find:

Draw the schematic diagram of a two-input CMOS OR gate.

Analysis:

The output of the circuit of Figure 11.18 is connected as an input to the circuit of Figure 11.14.

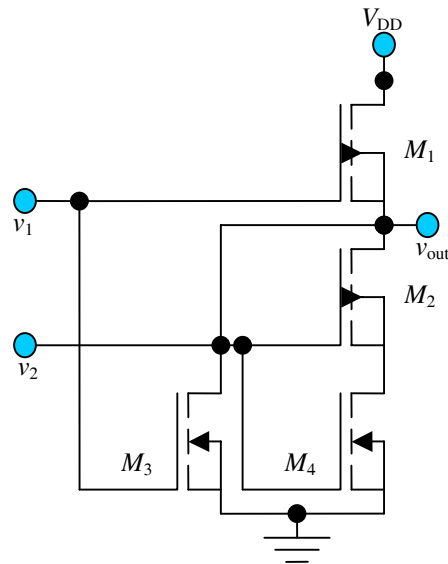


Figure 11.18

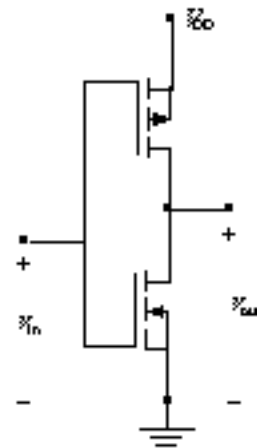


Figure 11.14

Problem 11.30

Solution:

Find:

Draw the schematic diagram of a two-input CMOS AND gate.

Analysis:

The output of the circuit of Figure 11.21 in the text is connected as an input to the circuit of Figure 11.14.

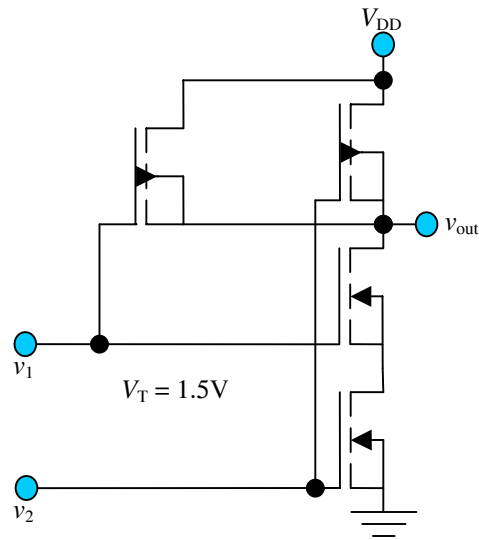


Figure 11.21

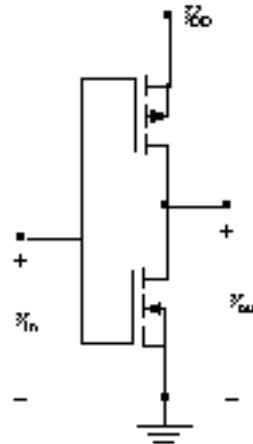


Figure 11.14

Problem 11.31


Solution:

Find:

Draw the schematic diagram of a two-input CMOS NOR gate.

Known quantities:

The circuit of Figure 11.18

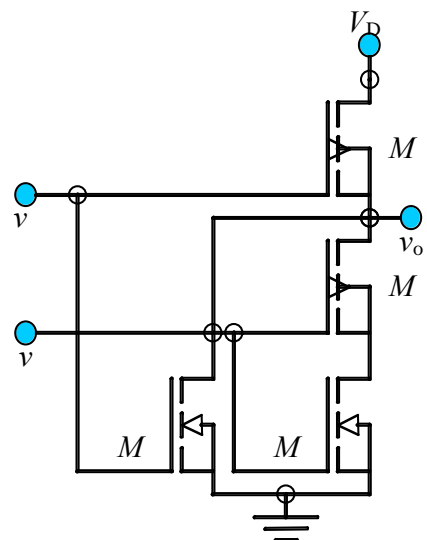

Figure

Problem 11.32


Solution:

Find:

Draw the schematic diagram of a two-input CMOS NAND gate.

Known quantities:

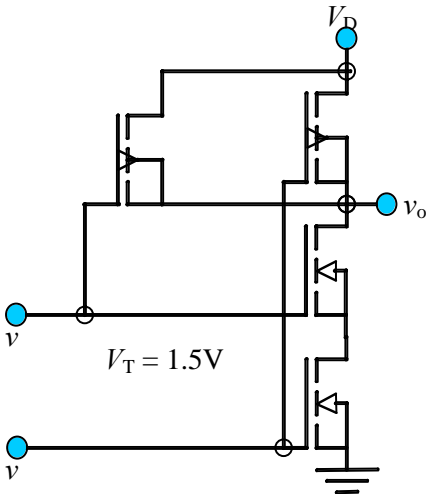The circuit of Figure 11.21, in the text.



Figure

Problem 11.33

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Solution:

Known quantities:


The circuit of Figure P11.33.

Find:

Show that the given circuit functions as a logic inverter.

Analysis:

Construct a state table:

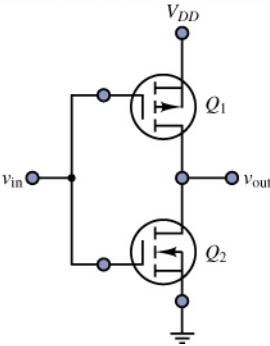

v_{in}	Q_1	Q_2	v_{out}
low	resistive	open	high
high	open	resistive	low

This table clearly describes an inverter.

Problem 11.34

Solution:

Known quantities:


The circuit of Figure P11.34.

Find:

Show that the given circuit functions as a NOR gate.

Analysis:

Construct a state table:

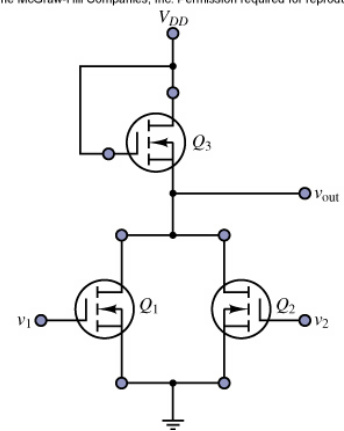

v_1	v_2	Q_1	Q_2	v_{out}
0	0	off	off	high
0	high	off	on	low
high	0	on	off	low
high	high	on	on	low

This table clearly describes a NOR gate.

Problem 11.35

Solution:

Known quantities:

The circuit of Figure P11.35.


Find:

Show that the given circuit functions as a NAND gate.

Analysis:

Construct a state table:

v_1	v_2	Q_1	Q_2	v_{out}
0	0	off	off	high
0	high	off	on	high
high	0	on	off	high
high	high	on	on	low

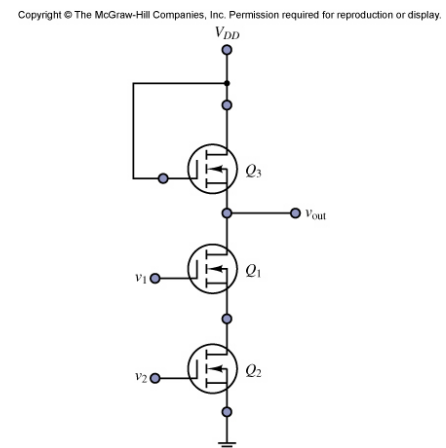

This table clearly describes a NAND gate.