




Next: [About this document ...](#) Up: [final16s](#) Previous: [Instruction \(read this before](#)

The Final Exam (don't click until you are ready to take the exam)

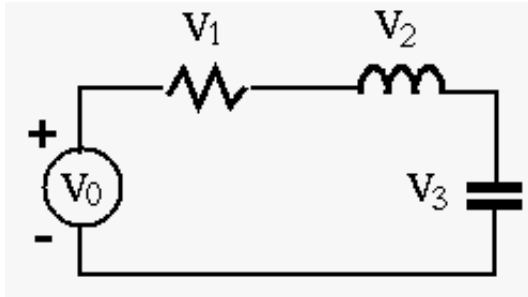
1. Answer the following questions:

- (10 pts) The RMS values of the three AC voltages across R, L, and C are known to be $V_1 = 4\text{ V}$, $V_2 = 5\text{ V}$, and $V_3 = 2\text{ V}$, respectively. Find the RMS voltage V_0 of the source. If the AC voltage source is replaced by a DC voltage source $V_0 = 10\text{ V}$, find the three voltages V_1 , V_2 , and V_3 .




- (10 pts) In the figure above, it is known that $R = 10\Omega$, $L = 100\text{ mH}$, and $C = 500\mu\text{F}$, and the current through the loop is known to be $i(t) = \cos(100t)\text{ A}$, find all four voltages $v_0(t)$, $v_1(t)$, $v_2(t)$, and $v_3(t)$.

- (10 pts) The RMS values of the three AC currents through R, L, and C measured by the three ammeters A_1 , A_2 , and A_3 are $I_1 = 4\text{ A}$, $I_2 = 5\text{ A}$, and $I_3 = 2\text{ A}$, respectively. Find the RMS value of the source current I_0 . If the AC voltage source is replaced by a DC current source $I_0 = 1\text{ A}$, find the three currents I_1 , I_2 , and I_3 measured respectively by ammeters A_1 , A_2 , and A_3 .

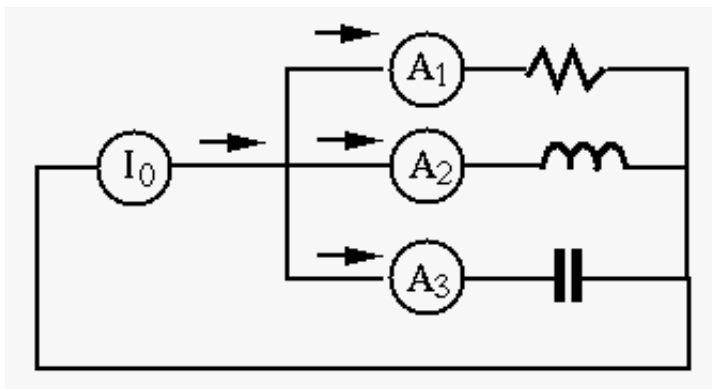


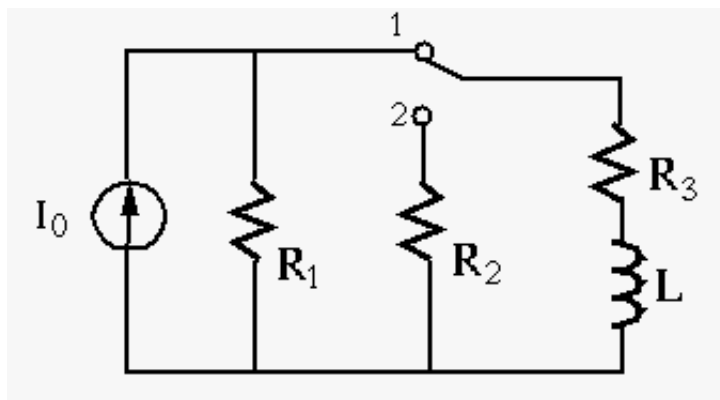2. (23 pts) In the circuit below, $R_1 = 20\Omega$, $R_2 = 10\Omega$, $R_3 = 30\Omega$, $L = 10\text{ mH}$, $I_0 = 5\text{ A}$.

The circuit is at steady state before the switch is turned from position 1 to position 2 at $t = 0$. Find the three voltages $v_1(t)$, $v_2(t)$ and $v_L(t)$ across R_1 , R_2 and L , respectively, for $t > 0$ (the bottom wire is treated as ground).



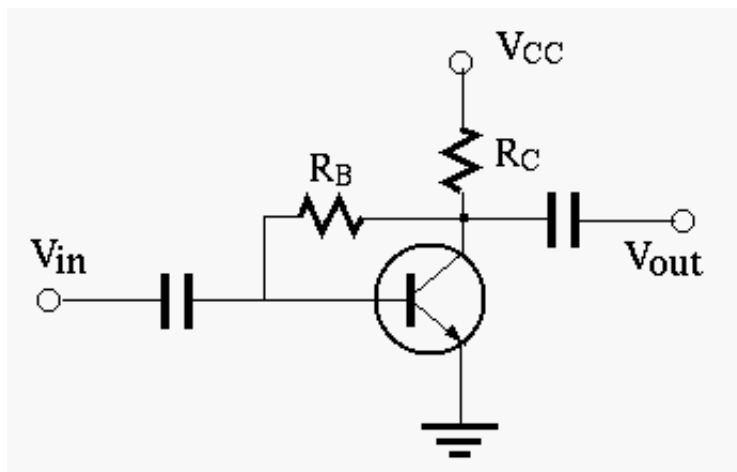3. (23 pts) The circuit below shows a simple means for obtaining improved bias stability of the DC operating point of the transistor. As always, assume $V_{BE} = 0.7\text{ V}$ when answering the following questions.



- Complete the event chain below (in terms of V_C , V_B , I_B , etc.) to show qualitatively that R_B connected to the collector C (instead of V_{CC}) introduces a negative feedback by

which the DC operating point tends to be stabilized:


$$I_C \uparrow \Rightarrow \dots \Rightarrow I_C \downarrow$$

- Derive an expression for I_C in terms of R_B , R_C , V_{CC} and β .
- Assuming $\beta = 100$, $V_{BE} = 0.7$, and $V_{CC} = 10V$, find $\overline{R_C}$ and R_B so that $V_{CE} = 5V$ and $I_C = 2mA$.
- Confirm your design does put the DC operating point in the middle of the linear region.

4. (24 pts) Determine qualitatively what kind of filter the following op-amp circuit is. Is it a first or second order? a low-pass, high-pass, or band-pass?

Find the frequency response function (FRF) of the circuit, and find the cut-off frequency ω_c of the filter in terms of the given circuit parameters R_1 , R_2 , R and C , so that

$$|H(j\omega_c)| = |H(j\omega_p)|/\sqrt{2}, \text{ where } \omega_p \text{ is the frequency at which } |H(j\omega_p)| \text{ reaches maximum.}$$

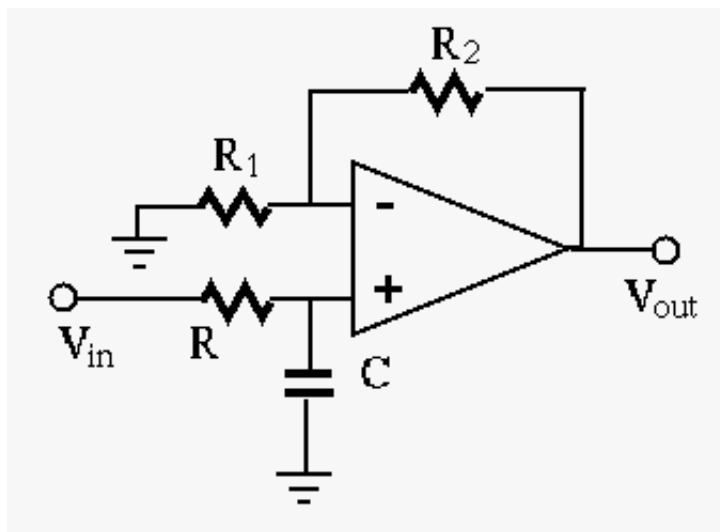

Next: [About this document ...](#) Up: [final16s](#) Previous: [Instruction \(read this before Ruye Wang 2016-05-09\)](#)