

1) 3.57 For the circuit shown in Fig. P3.57, the switch opens at time $t = 0$ s. Find $v(t)$ and $i(t)$ for all time.

2) 3.58 For the circuit shown in Fig. P3.57, change the value of the capacitor to $\frac{2}{3}$ F. For the resulting circuit, the switch opens at time $t = 0$ s. Find $v(t)$ and $i(t)$ for all time.

3) 3.59 For the circuit shown in Fig. P3.57, change the value of the capacitor to 3 F. For the resulting circuit, the switch opens at time $t = 0$ s. Find $v(t)$ and $i(t)$ for all time.



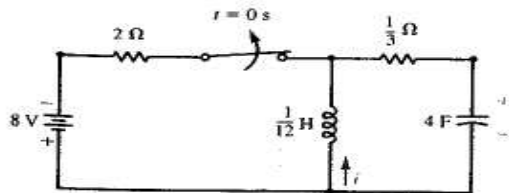


Fig. P3.57

① FEE 3.57
15 pts

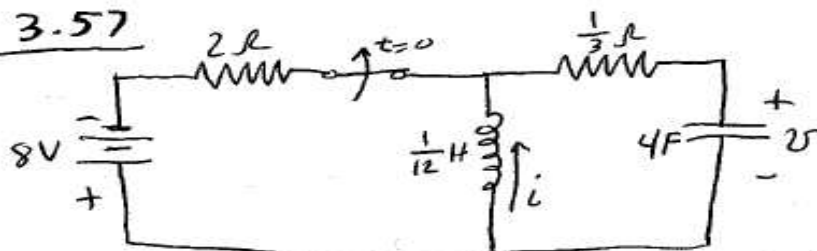


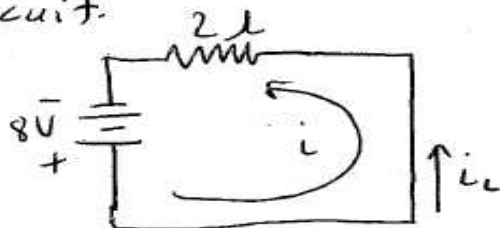At $t < 0$, it's a DC circuit where the inductor acts as a short circuit and the capacitor is an open circuit.



$$\text{So } i_L = i = 4 \text{ A}$$

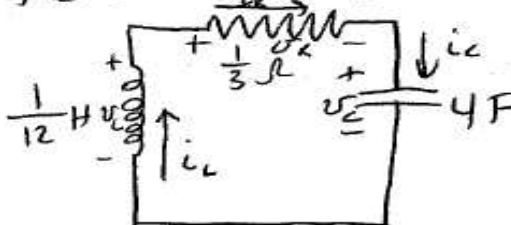As soon as the switch opens, we are left with this circuit.



$$\text{Here, } i_L = i_R = i_C \\ v_L = v_R + v_C$$

We also know:

$$i_L(0^+) = 4 \text{ A (instant. change)}$$

$$v_C(0^+) = 0 \text{ V (inst. change)}$$

$$v_R(0^+) = \frac{1}{3} \cdot 4 = \frac{4}{3} \text{ V (Ohm's Law)}$$

$$v_L(0^+) = \frac{4}{3} \text{ V (KVL)}$$

$$i_C(0^+) = 4 \text{ A (KCL)}$$

$$i_R(0^+) = 4 \text{ A (KCL)}$$

Now, what happens after 0^+ :

We need to determine if this is overdamped, under-damped or critically damped.

Remember, the 2nd order differential equation that satisfies the series RLC circuit is:

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\alpha = \frac{1}{2} \cdot \frac{1}{12} = 2$$

$$\omega_n = \frac{1}{\sqrt{LC}} = 3$$

So, since $\alpha^2 = 4 > \omega_n^2$ this is the "overdamped" case.

$$s_1 = -\alpha - \sqrt{\alpha^2 - \omega_n^2} = -2 - \sqrt{4-3} = -3$$

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega_n^2} = -2 + \sqrt{4-3} = -1$$

And, our expression for $v_c(t)$ is:

$$v_c(t) = A_1 e^{-3t} + A_2 e^{-t}$$

Now, to solve for A_1 & A_2 we need initial conditions

$$v_c(0) = A_1 + A_2 = 0 \quad (1)$$

$$\frac{dv_c(t)}{dt} = -3A_1 e^{-3t} - A_2 e^{-t}$$

$$i_c(t) = C \frac{dv_c(t)}{dt} = 4 \cdot [-3A_1 e^{-3t} - A_2 e^{-t}]$$

$$i_c(0) = -12A_1 - 4A_2 = 4A \quad (2)$$

$$(1) \& (2) \text{ combine to yield: } -8A_1 = 4 \Rightarrow A_1 = -\frac{1}{2}$$

$$\therefore A_2 = \frac{1}{2}$$

$$\text{So, } v_c(t) = -\frac{1}{2} e^{-3t} + \frac{1}{2} e^{-t} \text{ Volts}$$

$$i_c(t) = 4 \cdot \frac{3}{2} e^{-3t} - 4 \cdot \frac{1}{2} e^{-t} = 6e^{-3t} - 2e^{-t} \text{ Amps}$$


for $t \geq 0$

$$\begin{aligned} v_c(t) &= 0V \\ i_c(t) &= 4A \end{aligned} \quad \text{for } t < 0$$

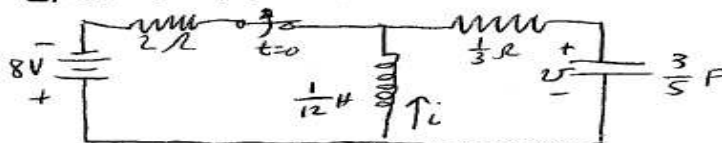2) F0EE 3.50

10
pts.


Here we revisit the circuit from the last HW except the capacitor is now $\frac{3}{5} F$.



Note, the value of the capacitor has no impact on its behavior at DC, so, the values at $t=0^-$ are the same as in HW 4: #5.

$$\text{So, } i(0^-) = 4A \text{ and } v(0) = 0V \cdot \frac{1}{3} \Omega$$

For $t \geq 0$ we have

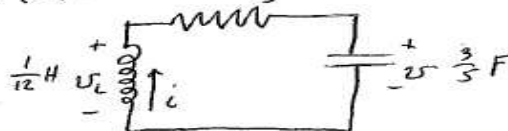

$$\alpha = \frac{R}{2L} = \frac{1/3}{2 \cdot 1/12} = 2$$

$$\omega_n^2 = \frac{1}{LC} = \frac{1}{1/12 \cdot 3/5} = 20$$

Since $\alpha^2 < \omega_n^2$ we have an underdamped case

$$\text{So, } \omega_d = \sqrt{\omega_n^2 - \alpha^2} = 4 \text{ rad/s}$$

$$\text{So, } v(t) = e^{-2t} (B_1 \cos 4t + B_2 \sin 4t)$$

Using boundary conditions: $v(0) = B_1 = 0$.

$$\therefore v(t) = e^{-2t} (B_2 \sin 4t)$$

$$i(t) = C \frac{dv}{dt} = \frac{3}{5} B_2 [e^{-2t} 4 \cos 4t - 2e^{-2t} \sin 4t]$$

$$i(0) = \frac{3}{5} B_2 [4 - 0] = 4A \quad \therefore B_2 = 5/3$$

$$\text{So, } v(t) = \frac{5}{3} e^{-2t} \sin 4t \text{ u(t) V}$$

$$i(t) = \begin{cases} 4A & t < 0 \\ e^{-2t} (4 \cos 4t - 2 \sin 4t) A & t \geq 0 \end{cases}$$

3 10 pts.

FoEE 3.59

Here we have the same circuit as in #2, except

$$C = 3 \text{ F. So, } v(0^-) = 0, i(0^-) = 4 \text{ A.}$$

$$\alpha = 2 \text{ and } \omega_n^2 = \frac{1}{\frac{1}{12} \cdot 3} = 4.$$

So $\alpha^2 = \omega_n^2$ \therefore This is a critically damped case.

$$\text{So, } v(t) = A_1 t e^{-2t} + A_2 e^{-2t}$$

Using boundary conditions:

$$v(0) = A_1(0) e^{-2 \cdot 0} + A_2 e^{-2 \cdot 0} = A_2 = 0.$$

$$\therefore v(t) = A_1 t e^{-2t}$$


$$i(t) = 3 \frac{dv}{dt} = 3 \cdot A_1 t (-2e^{-2t}) + 3 A_1 e^{-2t}$$

$$i(0) = 3 A_1 = 4 \quad \therefore A_1 = 4/3$$


$$\text{So, } v(t) = \frac{4}{3} t e^{-2t} u(t)$$

$$i(t) = \begin{cases} -8 t e^{-2t} + 4 e^{-2t} \text{ A} & \text{for } t \geq 0 \\ 4 \text{ A} & \text{for } t < 0 \end{cases}$$

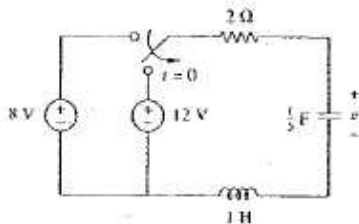4. (15 points) Determine $v(t)$ for $t > 0$ for the following circuit:




Initial condition:

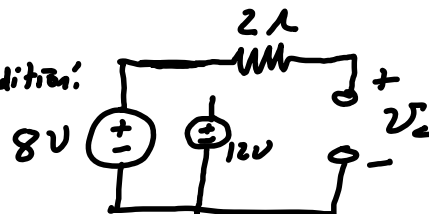

Since no current can flow $v_c = 8 \text{ V}$
So $v(0^-) = v(0^+) = 8 \text{ V}$

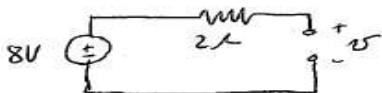First, we find $v(0)$ by looking at the DC circuit:




$$\therefore v(0) = 8 \text{ V}$$

$$i(0) = 0 \text{ A}$$

No current flows through an open circuit.

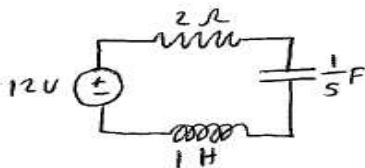After the switch closes we have the charging case:



$$\frac{d^2 v}{dt^2} + \frac{1}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{V}{LC}$$

$$2\alpha = 2 \quad \omega_n^2 = 5 \quad 60$$

$$\therefore \alpha = 1$$

Since $\alpha^2 < \omega_n^2$ this is underdamped.

Using the charging solution, we have:

$$v(t) = 12 + e^{-t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$v(0) = 12 + A_1 = 8 \text{ V} \quad \therefore A_1 = -4$$

$$i(t) = C \frac{dv}{dt} = \frac{1}{5} \left[e^{-t} (-2A_1 \sin 2t + 2A_2 \cos 2t) + -e^{-t} (A_1 \cos 2t + A_2 \sin 2t) \right]$$

$$\text{So, } i(0) = \frac{1}{5} (2A_2 - A_1) = 0 \text{ A}$$


$$= \frac{1}{5} (2A_2 + 4) = 0 \quad \therefore A_2 = -2$$

$$\therefore v(t) = 12 + e^{-t} (-4 \cos 2t - 2 \sin 2t) \text{ V for } t > 0$$

⑤ FEE 3.82

15 pts

$$2u(t) = v_s$$

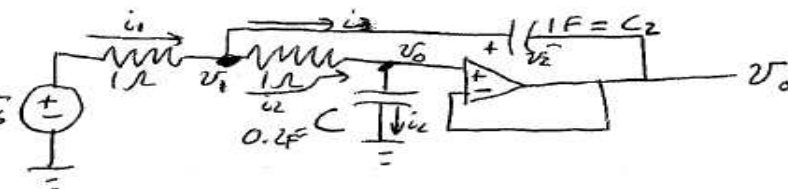

After $t=0$:

$$i_2 = i_C \Rightarrow \frac{v_1 - v_o}{1\Omega} = C \frac{dv_o}{dt} \Rightarrow v_1 = v_o + C \frac{dv_o}{dt}$$

$$i_1 = \frac{2 - v_1}{1\Omega}$$

$$2 - v_1 = 2 - v_o - C \frac{dv_o}{dt}$$

$$i_3 = C_2 \frac{dv_o}{dt} = (1F) \frac{d(v_1 - v_o)}{dt}$$

Combining: $i_1 = i_3 + i_2$

$$2 - v_1 = \frac{d(v_1 - v_o)}{dt} + v_1 - v_o$$

$$2 - v_o - C \frac{dv_o}{dt} = \frac{d(C \frac{dv_o}{dt})}{dt} + C \frac{dv_o}{dt}$$

$$2 - v_o - C \frac{dv_o}{dt} = C \frac{d^2 v_o}{dt^2} + C \frac{dv_o}{dt}$$

$$\therefore \frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + \frac{v_o}{C} = \frac{2}{C}$$

$$C = 0.2F \quad \boxed{\text{So, } \frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + 5 v_o = 10}$$

6. (5 points) 4.5 b

4.5 Find the rectangular form of the sum $A_1 + A_2$ for A_1 and A_2 given in Problem 4.3.

4.3 Find the rectangular form of the product $A_1 A_2$

given that: (a) $A_1 = 3e^{j30^\circ}$, $A_2 = 4e^{j60^\circ}$; (b) $A_1 = 3e^{j30^\circ}$, $A_2 = 4e^{-j30^\circ}$; (c) $A_1 = 5e^{-j60^\circ}$, $A_2 = 2e^{j120^\circ}$; (d) $A_1 = 4e^{j45^\circ}$, $A_2 = 2e^{-j90^\circ}$.

$$A_1 = 3e^{j30^\circ} = 3\cos 30^\circ + j3\sin 30^\circ = 3\frac{\sqrt{3}}{2} + j\frac{3}{2}$$

$$A_2 = 4e^{-j30^\circ} = 4\frac{\sqrt{3}}{2} - j\frac{4}{2}$$

$$\boxed{A = \frac{7\sqrt{3}}{2} - j\frac{1}{2}}$$

Optional Problems

1. (20 points) EE 3.60

3.60 For the circuit shown in Fig. P3.60, the switch opens at time $t = 0$ s. Find $i(t)$ and $v(t)$ for all time. (See p. 184.)


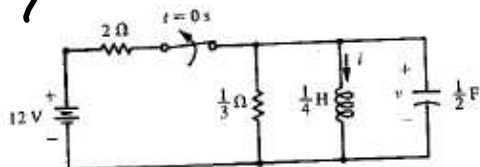


Fig. P3.60

At $t=0^-$ we use DC substitutions and replace the inductor with a short and the capacitor with an open.

These initial conditions are independent of the R, L, C values on the right hand side of the circuit and will hold for 3.60, 61 and 62.

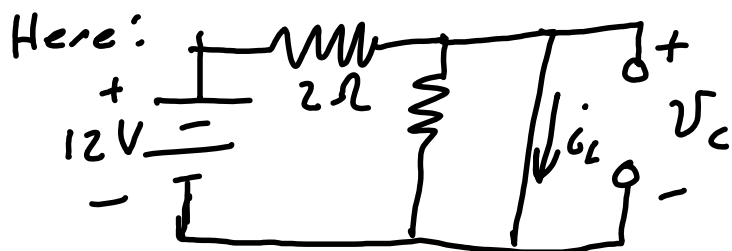The first thing we can do is find out the initial conditions by looking at $t=0^-$ and using instantaneous change rules.




$$\text{So, } i_L(0^-) = \frac{12}{2} = 6A$$

$$v_C(0^-) = 0V$$

$$\left\{ \begin{array}{l} \text{And } i_L(0^+) = i_L(0^-) = 6A \\ v_C(0^+) = v_C(0^-) = 0V. \end{array} \right.$$

After $t=0^- \dots$ for $t > 0$ we have!

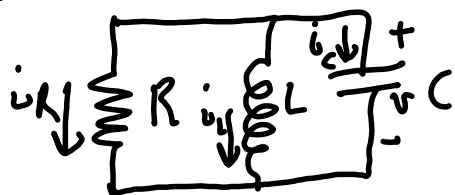

$$v_C = v_L = v_R \text{ \& } i_R + i_L + i_C = 0$$

$$\text{So, } \frac{v_C}{R} + i_L + C \frac{dv_C}{dt} = 0$$

$$\text{or since } v_C = v_L = L \frac{di_L}{dt}$$

$$C L \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = 0$$

Now we have things in a standard form and can

solve: $2\alpha = \frac{1}{RC}$ so $\alpha = \frac{1}{2RC}$ $\omega_n = \sqrt{\frac{1}{LC}}$

For this problem: $R = \frac{1}{3} \Omega$, $L = \frac{1}{4} H$, $C = \frac{1}{2} F$

So, $\alpha = 3$ and $\omega_n = \sqrt{8}$

Since $\alpha^2 > \omega_n^2$
this is OVERDAMPED

Our roots are: $-3 \pm \sqrt{\alpha^2 - \omega_n^2} = -3 \pm \sqrt{9-8} = -2, -4$

So, our solution is of the form:

$i_L(t) = A_1 e^{-2t} + A_2 e^{-4t}$ with two init. conditions
 $i_L(0^+) = 6A$, $v_L(0^+) = 0V$

$v_L(t) = L \frac{d}{dt} (A_1 e^{-2t} + A_2 e^{-4t})$
 $= \frac{1}{4} (-2A_1 e^{-2t} - 4A_2 e^{-4t})$ So, $A_1 + A_2 = 6$
and $-\frac{1}{2} A_1 - A_2 = 0$

This results in the solution:

So, $A_1 = 12$, $A_2 = -6$

$i_L(t) = \begin{cases} 6A & \text{for } t < 0 \\ (12e^{-2t} - 6e^{-4t})A & t \geq 0 \end{cases}$ and

$v(t) = \begin{cases} 0V & t < 0 \\ (-6e^{-2t} + 6e^{-4t})V & t \geq 0 \end{cases}$

2. (10 points) FoEE 3.61

3.61 For the circuit shown in Fig. P3.60, change the value of the resistor to $\frac{1}{3} \Omega$. For the resulting circuit, the switch opens at time $t = 0$ s. Find $i(t)$ and $v(t)$ for all time. (See p. 184.)

Here $\alpha = \frac{1}{2RC} = 2$ $\omega_n = \sqrt{8}$

Since $\alpha < \omega_n$ this is UNDERDAMPED.

so, our solution is of the form: $B_1 \cos \omega_d t + j B_2 \sin \omega_d t$

where $\omega_d = \sqrt{\omega_n^2 - \alpha^2} = \sqrt{8-4} = 2$

Here, the initial analysis is exactly the same. It differs in our solution to the new 2nd order D.E.

So, $i_L(t) = e^{-2t}(B_1 \cos 2t + B_2 \sin 2t)$
 $i_L(0) = e^0(B_1 \cdot 1 + B_2 \cdot 0) = B_1 = 6A$ from init. conditions

$v_L(t) = \frac{1}{4} \left[e^{-2t} \left(-2 \overset{B_1}{(6)} \sin 2t + 2B_2 \cos 2t \right) + \right.$
 $\left. -2e^{-2t} \left(\overset{B_1}{6} \cos 2t + B_2 \sin 2t \right) \right]$

$v_L(t) = \frac{1}{4} e^{-2t} \left[(2B_2 - 12) \cos 2t + (-2B_2 - 12) \sin 2t \right]$

$v_L(0) = \frac{1}{4} [(2B_2 - 12)] = 0 \quad \therefore B_2 = 6$

So, $i_L(t) = \begin{cases} 6A & t < 0 \\ e^{-2t} [6 \cos 2t + 6 \sin 2t] A & t \geq 0 \end{cases}$
 $v_L(t) = \begin{cases} 0 \text{ V} & t < 0 \\ -6e^{-2t} \sin 2t \text{ V} & t \geq 0 \end{cases}$

3. (10 points) FoEE 3.62

3.62 For the circuit shown in Fig. P3.60, change the value of the inductor to $\frac{1}{3}$ H. For the resulting circuit, the switch opens at time $t = 0$ s. Find $v(t)$ and $i(t)$ for all time. (See p. 184.)

Again, initial analysis is the same. Now $\alpha = \frac{1}{2RC} = 3$ and

$\omega_n = \sqrt{\frac{1}{LC}} = 3 \text{ rad/s}$

So, this is critically damped and our solution is of the form:

$i_L(t) = (A_1 t e^{-3t} + A_2 e^{-3t})$
 $i_L(0) = A_2 = 6$

So, $i_L(t) = A_1 t e^{-3t} + 6e^{-3t}$

$v_L(t) = \frac{2}{9} \left[A_1 e^{-3t} + A_1 t (-3) e^{-3t} - 18 e^{-3t} \right]$
 $= \frac{2}{9} \left[-3A_1 t + (A_1 - 18) \right] e^{-3t}$

$v_L(0) = \frac{2}{9} [A_1 - 18] = 0 \quad \text{so, } A_1 = 18$

So, $i_L(t) = \begin{cases} 6A & t < 0 \\ 18t e^{-3t} + 6e^{-3t} & t \geq 0 \end{cases}$
 $v_L(t) = \begin{cases} 0 \text{ V} & t < 0 \\ -12t e^{-3t} \text{ V} & t \geq 0 \end{cases}$