
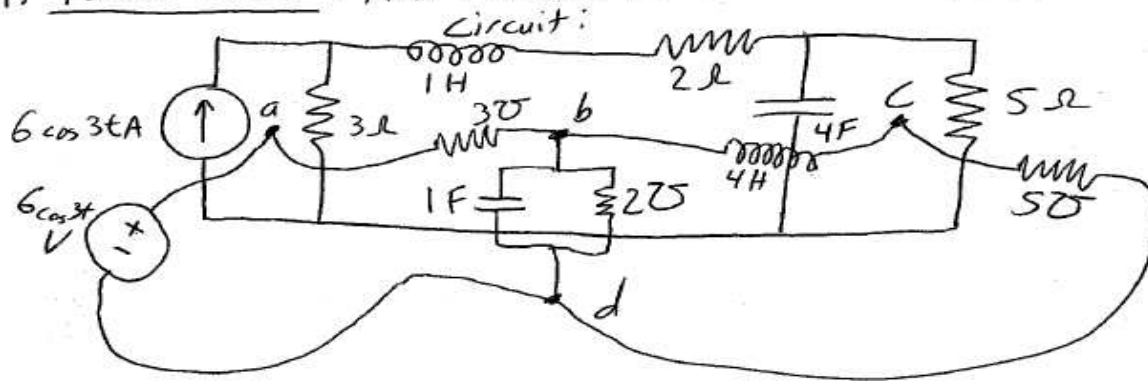


5pts.


1. F0EE 3.25 : Find the dual of this

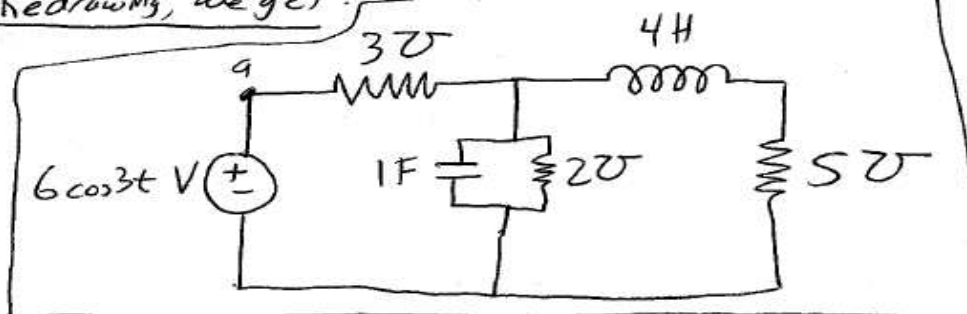

Redrawing, we get:



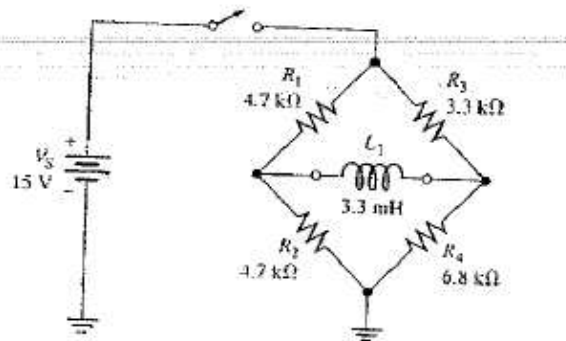2. (15 points) What is the current through the inductor 1.0μs after the switch closes?




If we use Thevenin, we can reduce this to a simple  $RL$  circuit with a source.

$$\text{First, } V_{oc} = V_{ab} = V_a - V_b \Rightarrow V_a = \left( \frac{4.7}{4.7 + 4.7} \right) 15 = 7.5V$$


$$V_b = \left( \frac{6.8}{3.3 + 6.8} \right) 15 = 10.1V$$

So,  $V$  between  $a$  &  $b$  is  $10.1 - 7.5V = 3.6V$

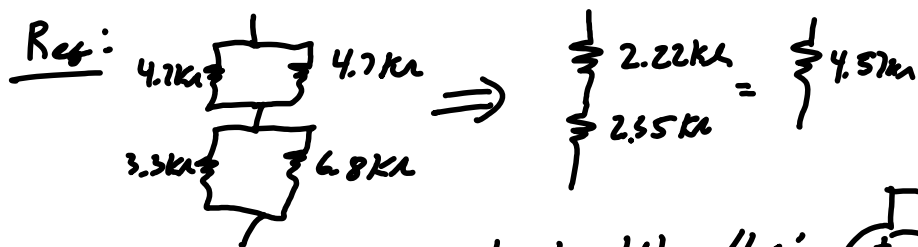Note since we just asked for the current through the inductor  $\rightarrow$  direction is arbitrary and  $V_{oc}$  can equal  $V_{bc}$ .



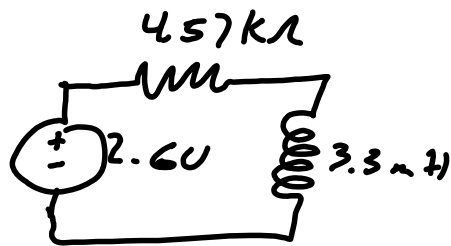So, an equivalent circuit looks like this:  
 (after,  $t=0$ )



Now, it should be simple to see that:

$$i_L(1\mu s) = \frac{V_s}{R} \left( 1 - e^{-tR/L} \right) = \frac{2.6V}{4.57k\Omega} \left( 1 - e^{-\frac{(1\mu s)(4.57k\Omega)}{3.3mH}} \right)$$

$i_L(1\mu s) = 0.426 \text{ mA}$

3) 10pts.

3.29 For the circuit shown in Fig. P3.28, replace the capacitor with a 5-H inductor. For the resulting circuit, the switch opens at time  $t = 0$  s. Write a differential equation in  $i(t)$  for  $t \geq 0$  s. Find  $i(t)$  and  $v(t)$  for all time and sketch these functions.

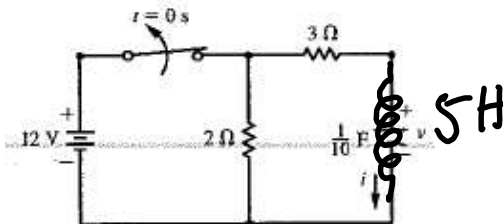


Fig. P3.28

For  $t < 0$

$i_L(0^-) = 4A = i_L(0^+)$


For  $t > 0$ :

RL discharge circuit:  
 $i_L(t) = i_L(0) e^{-tR/L}$

Graph of  $i(t)$  vs  $t$ :

$$i(t) = \begin{cases} 4e^{-t} \text{ A} & t \geq 0 \\ 4 & t < 0 \end{cases}$$

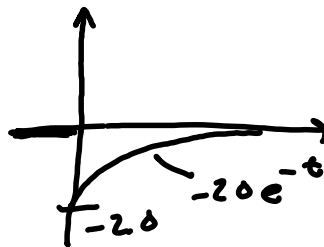$v(t) = 5 \frac{di}{dt} = \begin{cases} -20e^{-t} \text{ V} & t \geq 0 \\ 0 & t < 0 \end{cases}$



4)  
15 pts

3.37 For the circuit shown in Fig. P3.36, replace the inductor with a  $\frac{1}{8}$  F capacitor. For the resulting circuit, the switch opens at time  $t = 0$  s. Write a differential equation in  $v(t)$  for  $t \geq 0$  s. Find  $v(t)$  and  $i(t)$  for all time and sketch these functions.



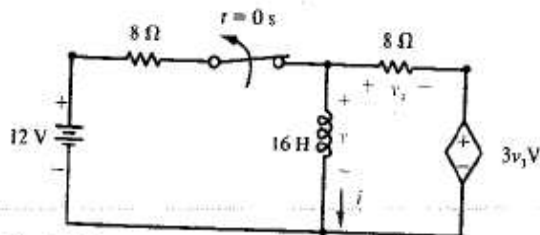


Fig. P3.36

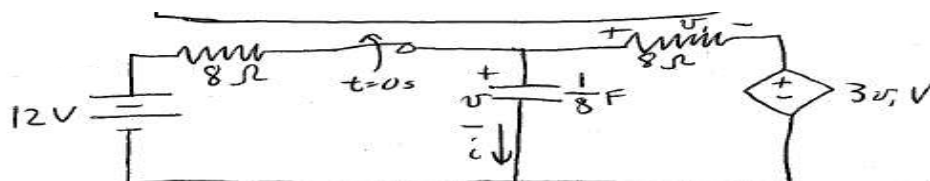

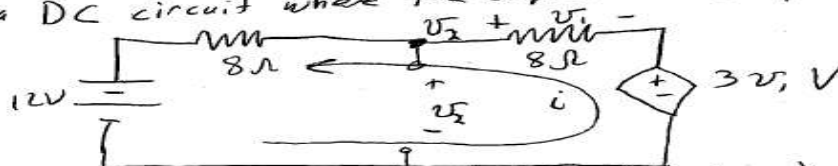First, we want to analyze this circuit for all  $t < 0$ . That's simply a DC circuit where the capacitor is an open circuit.



If we assume  $i$  is in this direction (as drawn), we know

$$3v_1 - v_2 = 8i \quad \text{and} \quad v_2 - 12V = 8i \quad \& \quad v_2 = 4v_1$$


$$\text{So, } 3v_1 - v_2 = v_2 - 12V$$

$$3v_1 - 4v_1 = 4v_1 - 12V \Rightarrow -5v_1 = -12V \quad v_1 = +\frac{12}{5}V$$

$$\text{So, } v_2 \text{ or } v_c(0^-) = \frac{12}{5} \cdot 4 = 9.6V$$

We know voltage can't change instantaneously across a capacitor so we start with 9.6V.

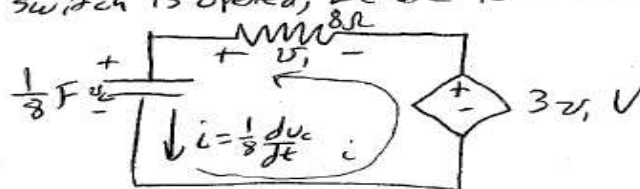After the switch is opened, we are left with:



$$v_c = 4v_1 = 4(8 \cdot -i) = -32i = -32 \cdot \frac{1}{8} \frac{dv_c}{dt}$$

$$\text{So, } 4 \frac{dv_c}{dt} + v_c = 0 \Rightarrow \boxed{\frac{dv_c}{dt} + \frac{1}{4} v_c = 0} \quad \text{Dist. eq. pg. 143 \& 144:}$$



$$\therefore v_c(t) = v_c(0) e^{-t/4} V \quad \frac{dx(t)}{dt} + ax(t) = b$$

$$\text{So, } i(t) = \frac{1}{8} \frac{dv_c}{dt} = \frac{1}{8} \frac{d}{dt} (9.6 e^{-t/4})$$

$$\boxed{i_c(t) = -\frac{9.6}{8 \times 4} e^{-t/4} = -0.3 e^{-t/4} A}$$


$$v_c(t) = \begin{cases} 9.6 & t < 0s \\ 9.6 e^{-t/4} & t \geq 0s \end{cases}$$
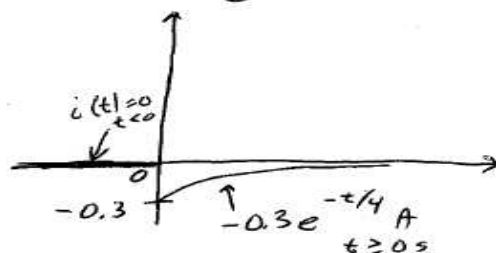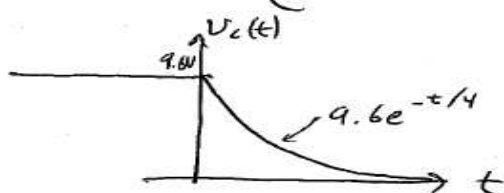
$$i_c(t) = \begin{cases} 0 & t < 0 \\ -0.3 e^{-t/4} & t \geq 0 \end{cases}$$



10 pts.

FoEE 3.48

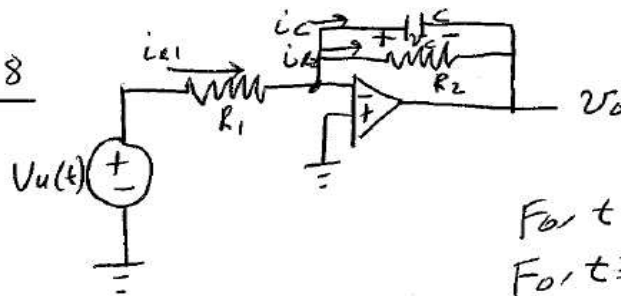

For  $t < 0$   $V_o = 0$

For  $t \geq 0$  ???

At  $0^+$ , let's see how the circuit behaves:

$$v_c(0^+) = 0V \quad (\text{because } v_c(0^-) = 0V)$$

$$v_R(0^+) = 0V \quad (\text{because } v_c(0^+) = 0V)$$

$$i_{R1}(0^+) = \frac{(V - 0)}{R_1} = \frac{V}{R_1}$$

$$i_{R2}(0^+) = 0A \quad (\text{because } v_{R2}(0^+) = 0V)$$

$$i_c(0^+) = \frac{V}{R_1} \quad (\text{by KCL it's the only place the current can go})$$

For  $t \geq 0$

By KCL at  $v_-$ :  $\frac{V - 0}{R_1} = i_c + i_{R2}$

$$\frac{V}{R_1} = C \frac{dv_c}{dt} + \frac{v_c}{R_2} \Rightarrow \frac{dv_c}{dt} + \frac{v_c}{R_2 C} = \frac{V}{R_1 C}$$

So, the solution to this diff. eq. is:

$$v_c(t) = \frac{\frac{V}{R_1 C}}{\frac{1}{R_2 C}} + A e^{-\frac{t}{R_2 C}} = \frac{V R_2}{R_1} + A e^{-t/R_2 C}$$

$$A = -\frac{V R_2}{R_1} \text{ so } v_c(0^+) \text{ is right.}$$

$$\therefore v_c(t) = \frac{V R_2}{R_1} (1 - e^{-t/R_2 C})$$

$$v_o(t) = -v_c(t) = -\frac{V R_2}{R_1} (1 - e^{-t/R_2 C}) u(t) \text{ Volts}$$

Optional Problems

FoEE 3.31

3.31 For the circuit shown in Fig. P3.30, replace the inductor with a 0.1-F capacitor. Suppose that  $i_s(t) = 10 \text{ A}$  for  $t < 0$  s and  $i_s(t) = 0 \text{ A}$  for  $t \geq 0$  s. Write a differential equation in  $v(t)$  for  $t \geq 0$  s. Find  $v(t)$  and  $i(t)$  for all time and sketch these functions.


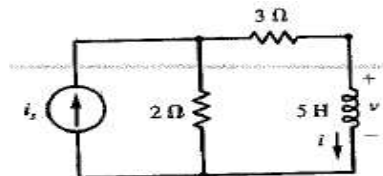


Fig. P3.30

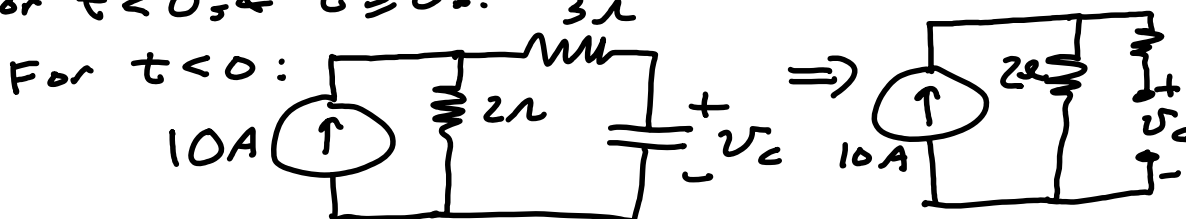
First let's redraw the circuit with the capacitor for  $t < 0$  &  $t \geq 0$  s.



Since we have been in this situation for a ~~very~~ long time AND have a DC source, we use the DC replacement and turn the capacitor into an open ckt.  $\therefore v_c(0^-) = v_{2\Omega}(0^-) = 10 \cdot 2 = 20V$

$v_c(0^+) = v_c(0^-)$  because of instantaneous charge rules.

For  $t > 0$ :

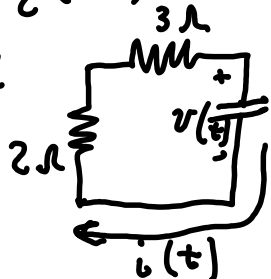


$$v(t) + 5i = 0$$

$$5(0.1) \frac{dv}{dt} + v = 0 \Rightarrow \frac{dv}{dt} + 2v = 0$$

$$v(t) = v(0) e^{-t/\tau_c} = \begin{cases} 20 e^{-2t} & t \geq 0 \\ 20V & t < 0 \end{cases}$$


So,  $i(t) = C \dot{v}(t) = \frac{1}{10} \cdot 20 \cdot (-2) e^{-2t} = -4 e^{-2t} A$   $t \geq 0$   
 $0 A$   $t < 0$

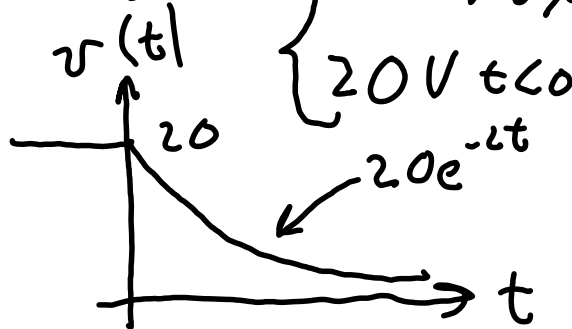

FoEE 3.35


$v_s(t) = 12V$  for  $t < 0$  s and  $v_s(t) = 0V$  for  $t \geq 0$  s.  
 Write a differential equation in  $i(t)$  for  $t \geq 0$ .  
 Find  $i(t)$  and  $v(t)$  for all time and sketch these functions.

So, at  $t < 0$ : DC: L + short

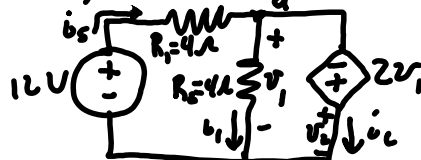

The only way this works is if  $v_1 = 0V$ . So,  $i_1 = 0A$ .  
 So, by KVL, all 12V drop across  $R_1$ . So,  $i_1 = 3A$  and by KCL at "a",  $i_L = 3A$ .

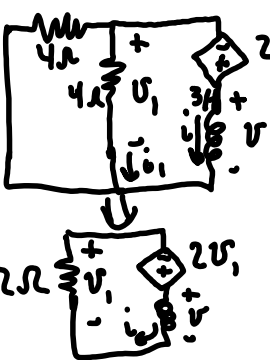For  $t > 0$ :  $v_s = 0$ , so source is short



$$v = 3v_1 \text{ (KVL)}$$

$$3 \frac{di}{dt} = 3(2(-i))$$

$$\text{So, } \frac{di}{dt} + 2i = 0$$

$$i(t) = i(0) e^{-t/\tau} = \begin{cases} 3 e^{-2t} A & t \geq 0 \\ 3 A & t < 0 \end{cases}$$

$$v(t) = L \frac{di}{dt} = 3(-2) 3 e^{-2t} = \begin{cases} -18 e^{-2t} V & t \geq 0 \\ 0 & t < 0 \end{cases}$$


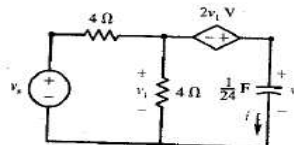
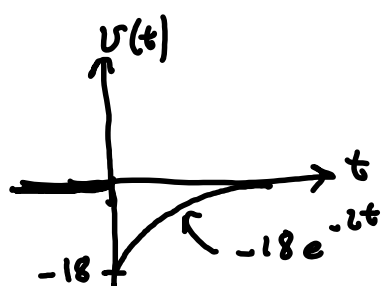


Fig. P3.34

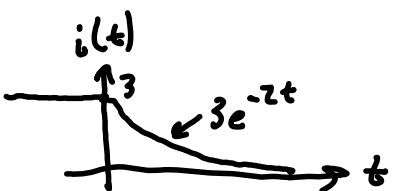3.35 For the circuit shown in Fig. P3.34, replace the capacitor with a 3-H inductor. Suppose that

