

## **E84: Introduction to Electrical Engineering**

# **Lab 10 Solutions**



### **Grading Rubric**

1 time spent

Warm-up

1: Twin-T

3 Correct transfer function

2 Correct w0 and Q

2 Bode plot

2: Sallen-Key

3 Correct transfer function

2 Bode plot

Lab

2 Correct component values for twin-T

2 Reasonable component values for Sallen-key

2 MultiSim Bode plots confirming component values meet specs

1 Monte Carlo results for 60 Hz notch meeting specs across variation

1 Photo of circuit

4 Measurement results consistent with simulations

Extra credit

3 test results connected to ECG board

#### Warm-Up

Simplify these:

1)
$$\frac{V_{in} - V_{A}}{R} + \frac{V_{out} - V_{A}}{R} + (\alpha V_{out} - V_{A})(2sC) = 0$$

$$(V_{in} - V_{B})sC + (V_{out} - V_{B})sC + \frac{(\alpha V_{out} - V_{B})}{\frac{R}{2}} = 0$$

$$\frac{V_{out} - V_{A}}{R} + (V_{out} - V_{B})sC = 0$$

$$V_{A} = \frac{V_{in} + V_{out} (1 + 2\alpha sRC)}{2(1 + sRC)}$$


$$V_{B} = \frac{V_{in} sRC + V_{out} (2\alpha + sRC)}{2(1 + sRC)}$$

$$V_{out}(1+sRC) = V_A + V_B sRC$$

Then substitute VA and VB into the Vout equation and simplify

$$\frac{V_{out}}{V_{in}} = \frac{1 + (sRC)^{2}}{1 + 4sRC(1 - \alpha) + (sRC)^{2}} = \frac{s^{2} + \omega_{0}^{2}}{s^{2} + s\frac{\omega_{0}}{Q} + \omega_{0}^{2}}$$

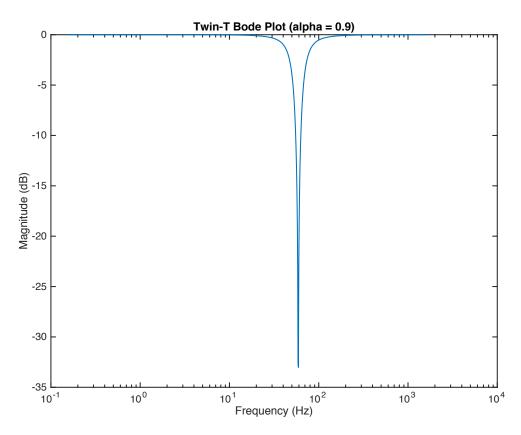with  $\omega_{_0}$  =1/RC and Q = 1/4(1- $\alpha$ ). This is a narrower band-stop filter with a magnitude of 1 at high and low frequency but 0 at  $\omega_{_0}$ . The quality factor and hence bandwidth can be tuned by adjusting  $\alpha$  via the potentiometer. The Bode plot is shown below.



2) By KCL at the two intermediate nodes and by approximating that V+ = V- for an ideal op-amp, we get the node equations.

$$\frac{b-x}{R_5} + \frac{c-x}{R_6} + j\omega C_6(c-x) = 0$$

$$\frac{x-c}{R_6} - j\omega C_5 c = 0$$

Solving, we find a 2<sup>nd</sup> order low pass transfer function:

$$x = c \left[ 1 + j\omega C_{5}R_{6} \right]$$

$$b = x \left[ 1 + \frac{R_{5}}{R_{6}} + j\omega C_{6}R_{5} \right] - c \left[ \frac{R_{5}}{R_{6}} + j\omega C_{6}R_{5} \right]$$

$$= c \left\{ \left( 1 + j\omega C_{5}R_{6} \right) \left[ 1 + \frac{R_{5}}{R_{6}} + j\omega C_{6}R_{5} \right] - \left[ \frac{R_{5}}{R_{6}} + j\omega C_{6}R_{5} \right] \right\}$$

$$= c \left[ 1 + j\omega C_{5}(R_{5} + R_{6}) + (j\omega)^{2}R_{5}C_{5}R_{6}C_{6} \right]$$

$$\frac{c}{b} = \frac{1}{1 + j\omega C_{5}(R_{5} + R_{6}) + (j\omega)^{2}R_{5}C_{5}R_{6}C_{6}} = \frac{1}{1 + 2\zeta \frac{j\omega}{\omega_{0}} + \left( \frac{j\omega}{\omega_{0}} \right)^{2}}$$


with


$$\omega_0 = \frac{1}{\sqrt{R_5 C_5 R_6 C_6}}; \zeta = \frac{C_5 (R_5 + R_6)}{2} \omega_0$$
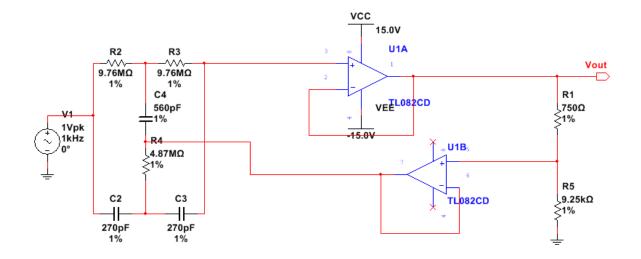
#### Lab

For the twin-T filter, C is specified as 270 pF. To achieve  $\omega_0 = 2\pi(60)$ , R =  $1/(C\omega_0) = 9.8$  M $\Omega$ . Hence, based on parts available from DigiKey in 0805 packages with 1% tolerances, choose R2 = R3 = 9.76M, R4 = 4.87M, C2 = C3 = 270 pF, C4 = 560 pF. This gives an actual center frequency of  $1/(2\pi RC) = 60.4$  Hz, neglecting the small error of C4 being slightly more than twice C2.

Alpha can be tuned using simulation. The following figure shows a Multisim schematic of the circuit with component tolerances. Run a 20-point Monte Carlo AC simulation to understand the impact of component variations and find that alpha = 0.925 gives attenuation of at least 20.8 dB at 60 Hz and less than 2.7 dB at 50 and 70 Hz.



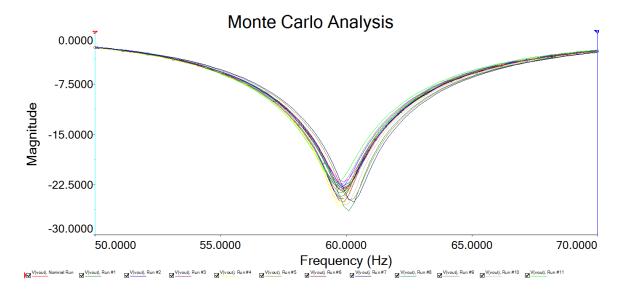

Use two identical Sallen-Key low-pass anti-aliasing filters to achieve steep roll-off. Use a critically damped design so that the response in the pass-band is fairly flat.

To achieve -30 dB at 1 KHz, each filter must have a gain of -15 dB = 0.178 at this point. The second order term dominates here, so we solve  $(\omega_0/\omega)^2$  = 0.178 for  $\omega$  = 2.37  $\omega_0$ . Choose  $\omega$  = 800 Hz rather than 1 KHz to give some margin, meaning  $\omega_0$  = 800 / 2.37 = 337 Hz, comfortably above the 140 Hz required corner frequency.

Choose  $\zeta = 0.707$  for critical damping to get a crisp transition at the corner.

Using the formula from the warm-up, we can solve for component values to get the desired  $\omega_0$  and  $\zeta$ .

$$\omega_0 = \frac{1}{\sqrt{R_5 R_6 C_5 C_6}}; \zeta = \frac{C_6 (R_5 + R_6)}{2} \omega_0$$

Choose R5 = R6 = R. Then substitute into these equations to find

$$\zeta = \frac{2RC_6}{2\sqrt{R^2C_5C_6}} = \sqrt{\frac{C_5}{C_6}} \triangleq \sqrt{\frac{1}{2}}$$

Hence C = C6 = 2C5 to obtain the desired damping.

Now substitute these component ratios into the natural frequency equation to find

$$\omega_0 = \frac{\sqrt{2}}{RC} \triangleq 2\pi \times 337$$

$$RC = \frac{1}{\pi\sqrt{2}\times337} = 334\,\mu s$$


To get in a reasonable range, choose C = 0.2 uF and R = 3.3k. Substitute these back for component values R5 = R6 = 3.3k, C5 = 0.1 uF, C6 = 0.2 uF. These give  $\zeta$  = 0.707,  $\omega_0$  = 2143 rad/s = 341 Hz .


The frequency response function of the cascaded active filters is thus

$$\left[\frac{1}{1+2\zeta j\frac{\omega}{\omega_0} + \left(j\frac{\omega}{\omega_0}\right)^2}\right]^2$$


To confirm the specifications, the attenuation at  $140~\rm Hz$  is -0.24 dB and the attenuation at  $1000~\rm Hz$  is -37.5 dB, much better than the -3 and -30 dB requirements for passband and stopband.

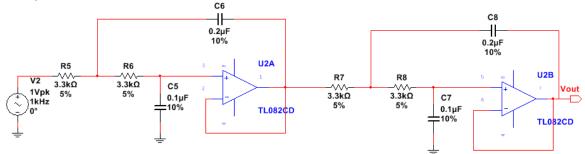These specs are also confirmed with Multisim simulation. Simulation shows attenuation of -0.24 dB at 140 Hz and -37.5 dB at 1000 Hz, in exact agreement with analysis.



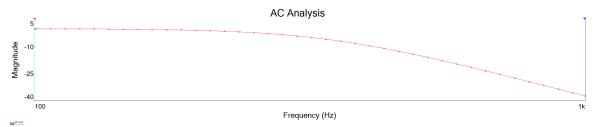

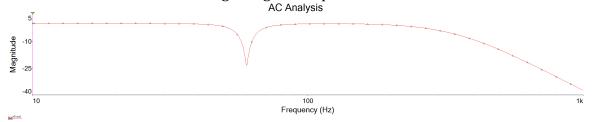Putting these together gives the complete desired frequency response function with a notch at 60 Hz and antialiasing of higher frequencies.



The bill of materials for the filter components is given below.

Ref	Component	Supplier	Part #	Cost	Quantity	Total
R2-R3	SMT 0805 1% 9.76	DigiKey	541-9.76MCCT-ND	0.39	2	
	$M\Omega$		<u>54 1-3.7 OMOCT-ND</u>			
R4	SMT 0805 1% 4.87 MΩ	DigiKey	1276-5454-1-ND	0.10	1	
C2-C3	SMT 0805 1% 270 pF	DigiKey	399-9213-1-ND	1.05	2	
C4	SMT 0805 1% 560 pF	DigiKey	478-6047-1-ND	0.64	1	
C5, C7	Thru-hole 0.1 uF 10%				2	
C6, C8	Thru-hole 0.2 uF 10%				2	
R5-R8	Thru-hole 3.3k 5%				4	

U1-U2	TL082CD Dual Op-	DigiKey	296-1284-5-ND	0.77	2	1.54
	Amp SOIC					
R1	10k Trim	DigiKey	A105870-ND	0.96	1	0.96
	Potentiometer		A 103070-IND			
J1	5-pin female header	DigiKey	S6103-ND	0.62	1	0.62
C1p, C1m	SMT 0805 0.1 uF Cap	DigiKey	1276-1003-1-ND	0.10	2	0.20

The measured frequency response function is shown below. The 60~Hz notch is 23.1~dB deep at the selected potentiometer setting and is centered exactly on 60~Hz +/- 1~Hz. The attenuation at high frequency is 28.5~dB, somewhat less than the 37.5~dB expected, because the 2-layer board picks up some 60~Hz noise after the notch filter, and this noise sets a floor that prevents the Sallen-Key filter from dropping off as fast as expected.

