

5.27 For the impedance shown in Fig. P5.27, suppose that $R = 1 \Omega$, $L = \frac{1}{5} \text{ H}$, and $C = 1 \text{ F}$. Find the resonance frequency.


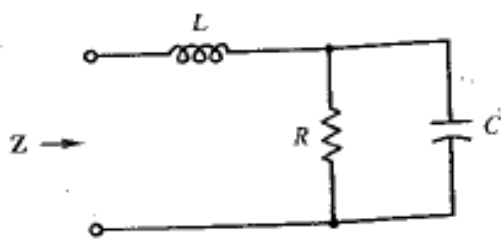


Fig. P5.27

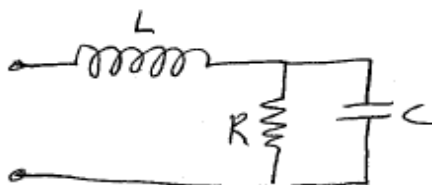For E5.27 Find the resonant frequency of:



Resonant frequency is the frequency where the imaginary part of the impedance is 0.

$$\text{So, } Z_R = R$$

$$Z_{RC} = \frac{-Rj}{\omega C} = \frac{-Rj}{\omega RC - j}$$

$$Z_L = j\omega L$$

$$Z_C = \frac{j}{\omega C}$$

$$Z_T = \frac{-Rj}{\omega RC - j} + j\omega L \left[\frac{\omega RC - j}{\omega RC - j} \right]$$

$$= \frac{-Rj + j\omega^2 RLC + \omega L \left[\frac{\omega RC + j}{\omega RC + j} \right]}{\omega RC - j}$$

$$= \frac{-R^2\omega Cj + j\omega^3 R^2 L C^2 + \omega^2 RLC + R - \omega^2 RLC + j\omega L}{\omega^2 R^2 C^2 + 1}$$

So imaginary portion is

$$j(-\omega R^2 C + \omega^3 R^2 L C^2 + \omega L) = 0$$

$$\text{So we have for } \omega \Rightarrow \omega^3 R^2 L C^2 = \omega(R^2 C - L)$$

$$\omega = 0 \frac{\text{rad}}{\text{s}} \dots \text{trivial case}$$


$$\omega_r = 2 \frac{\text{rad}}{\text{s}}$$

$$\omega^2 = \frac{R^2 C - L}{R^2 L C^2} = \frac{1}{LC} - \frac{1}{R^2 C^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{1}{R^2 C^2}} = \sqrt{5-1} = 2 \frac{\text{rad}}{\text{s}}$$

② 5.35 A $10\text{-}\Omega$ resistor and a 2-H inductor are connected in series, and $\omega = 50\text{ rad/s}$. (a) What is the Q of this series connection? (b) What parallel RL connection has the same admittance as the series connection? (c) What is the Q of this parallel connection?

③ 5.35 in P2EE

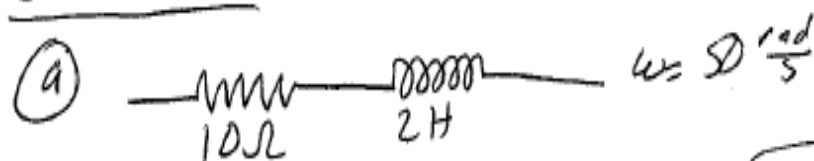


$$Z_R = 10\Omega \quad \text{So, } R_s = 10\Omega$$

$$Z_L = j100\Omega \quad X_s = 100\Omega$$

$$\therefore Q = \frac{|X_s|}{R_s} = 10$$

② $Y = \frac{1}{Z} = \frac{1}{10 + j100} \left(\frac{10 - j100}{10 - j100} \right)$
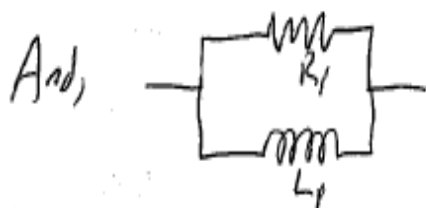
$$= \frac{10 - j100}{100 + 10000} = \frac{10}{10100} - \frac{j100}{10100} = \frac{1}{1010} - \frac{j}{101}$$



$$Z_T = \frac{1}{\frac{1}{R_p} + \frac{1}{Z_{L_p}}}$$

So,

$$Y_T = \frac{1}{R_p} + \frac{1}{Z_{L_p}} = \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

So, $R_p = 1010\Omega$

$$\frac{1}{j\omega L_p} = \frac{-j}{101}$$

$$\frac{1}{50 L_p} = \frac{1}{101} \Rightarrow L_p = \frac{101}{50} = 2.02\text{ H}$$

③ $Q = \frac{R_p}{|X_p|} = \frac{1010}{(2.02)(50)} = 10$

- 5.41 For the series RLC circuit shown in Fig. P5.15, suppose that $R = 2 \Omega$, $L = \frac{1}{2} \text{ H}$, $C = 2 \text{ F}$, and $v_1(t) = 20e^{-6t} \cos 3t \text{ V}$. Find (a) $v_R(t)$, (b) $v_L(t)$, and (c) $v_C(t)$.

For EE 5.41 If $v_1(t) = 20e^{-6t} \cos 3t \text{ V}$, then $Z_R = R = 2 \Omega$
 $Z_C = \frac{1}{sC} = \frac{1}{s2} \Omega$
 $Z_L = sL = \frac{1}{2}s \Omega$

Since these are in series, a simple voltage divider will yield the requested voltages

$$\text{a) } v_R(t) = \frac{Z_R}{Z_R + Z_L + Z_C} v_1(t) \Rightarrow \underline{V_R} = \frac{Z_R}{Z_R + Z_L + Z_C} \underline{V_1}$$

$$\underline{V_R} = \frac{2}{2 + \frac{1}{2}s + \frac{1}{s2}} \underline{V_1} = \frac{2s}{\frac{1}{2}s^2 + 2s + \frac{1}{2}} \underline{V_1} = \frac{4s}{s^2 + 4s + 1} \underline{V_1}$$

Here, $s = -6 + j3$ So, $\underline{V_R} = \frac{4(-6 + j3)}{(-6 + j3)^2 + 4(-6 + j3) + 1} \underline{V_1}$

$$= \frac{-24 + 12j}{36 - 36j - 9 - 24 + 12j + 1} \underline{V_1}$$

$$= \frac{-24 + 12j}{4 - 24j} \underline{V_1} = \frac{-6 + 3j}{1 - 6j} \underline{V_1}$$

$$= \frac{6.7 \angle 153.4^\circ}{6.08 \angle -80.5^\circ} 20 \angle 0^\circ$$

$$= 22.04 \angle 233.9^\circ$$

$$\text{So, } v_R(t) = 22.04 e^{-6t} \cos(3t + 233.9^\circ) \text{ V}$$

$$= 22.04 e^{-6t} \cos(3t - 126.1^\circ) \text{ V}$$

$$\text{b) } \underline{V_L} = \frac{Z_L}{Z_R + Z_L + Z_C} \underline{V_1} = \frac{\frac{1}{2}s}{\frac{1}{2}s^2 + 2s + \frac{1}{2}} \underline{V_1} = \frac{s^2}{s^2 + 4s + 1} \underline{V_1}$$

From math above we get $= \frac{(-6 + j3)^2}{4 - 24j} \underline{V_1} = \frac{27 - 36j}{4 - 24j} \underline{V_1} = \frac{45 \angle -53.1^\circ}{24.3 \angle -80.5^\circ} 20 \angle 0^\circ$

$$\underline{V_L} = 37 \angle 27.4^\circ$$

$$v_L(t) = 37 e^{-6t} \cos(3t + 27.4^\circ) \text{ V}$$

$$\text{c) } \underline{V_C} = \frac{Z_C}{Z_R + Z_L + Z_C} \underline{V_1} = \frac{\frac{1}{2s}}{\frac{1}{2}s^2 + 4s + 1} \underline{V_1} = \frac{1}{s^2 + 4s + 1} \underline{V_1} = \frac{1}{4 - 24j} \underline{V_1} = \frac{1}{24.3 \angle -80.5^\circ} 20 \angle 0^\circ$$

$$\underline{V_C} = 0.82 \angle 80.5^\circ$$


$$v_C(t) = 0.82 e^{-6t} \cos(3t + 80.5^\circ) \text{ V}$$

- 5.45 For the series RLC circuit shown in Fig. P5.15, suppose that $R = 2 \Omega$, $L = \frac{1}{2} \text{ H}$, and $C = 2 \text{ F}$. Draw a pole-zero plot for (a) $\underline{I}/\underline{V}_1$, (b) $\underline{V}_R/\underline{V}_1$, (c) $\underline{V}_L/\underline{V}_1$, and (d) $\underline{V}_C/\underline{V}_1$.

FOEE S. 45 $R = 2 \Omega$, $L = \frac{1}{2} \text{ H}$, $C = 2 \text{ F}$


So, a) $\frac{\underline{I}}{\underline{V}_1} = \frac{1}{\underline{Z}_T} = \frac{1}{2 + \frac{1}{2}s + \frac{1}{2s}} = \frac{2s}{s^2 + 4s + 1}$

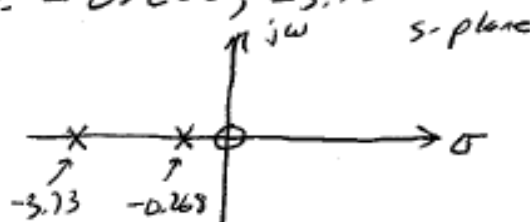zeros: $s = 0$
 poles: roots of $s^2 + 4s + 1 = 0$ (using quad. eqn.)
 $s = -0.268, -3.73$



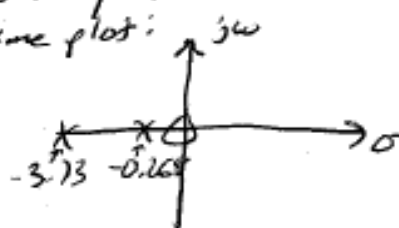
b) $\frac{\underline{V}_R}{\underline{V}_1} = \frac{\underline{Z}_R}{\underline{Z}_T} = \frac{2}{2 + \frac{1}{2}s + \frac{1}{2s}} = \frac{4s}{s^2 + 4s + 1}$

So, same zeros and poles as in part (a).
 Same plot:



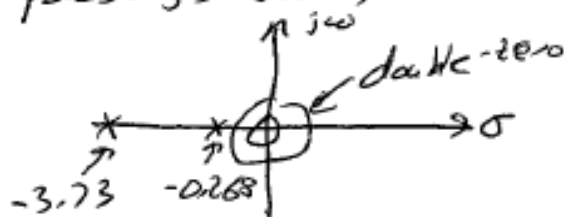
c) $\frac{\underline{V}_L}{\underline{V}_1} = \frac{\underline{Z}_L}{\underline{Z}_T} = \frac{\frac{1}{2}s}{2 + \frac{1}{2}s + \frac{1}{2s}} = \frac{s^2}{s^2 + 4s + 1}$

zeros: $s = 0, 0$
 poles: $s = -0.268, -3.73$



d) $\frac{\underline{V}_C}{\underline{V}_1} = \frac{\underline{Z}_C}{\underline{Z}_T} = \frac{\frac{1}{2s}}{2 + \frac{1}{2}s + \frac{1}{2s}} = \frac{1}{s^2 + 4s + 1}$

No zeros
 poles: $s = -0.268, -3.73$

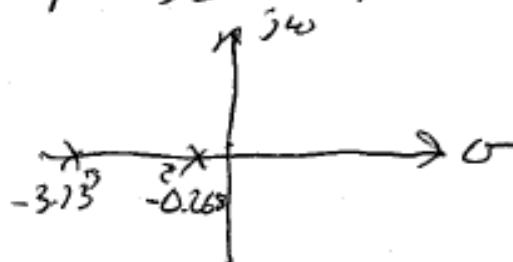

5.49 For the op-amp circuit shown in Fig. P5.49, draw the pole-zero plot of $H(s) = V_2/V_1$ for the case that C is (a) $\frac{1}{2}$ F, (b) 1 F, and (c) 2 F.



19

Need a pole-zero plot of $\frac{V_2}{V_1}$... so first KCL on V_x & V_+

$$V_1 - V_x = \frac{1}{3}V_x - \frac{1}{3}V_2 + 5V_x - 5V_2$$

$$V_1 - \left(\frac{4}{3} + s\right)V_x = \left(-\frac{1}{3} - s\right)V_2$$

(2) KCL on V_x : $\frac{(V_x - V_2)}{3} = \frac{V_2}{\frac{1}{5C}} \Rightarrow \frac{V_x}{3} = \frac{V_2}{3} + V_2 \leq C$
 $V_x = V_2 + 3 \leq C V_2$

So (1) becomes: $V_1 - \left(\frac{4}{3} + s\right)(1 + 3sC)V_2 = \left(-\frac{1}{3} - s\right)V_2$


$$V_1 - \left(\frac{4}{3} + s + 4sC + 3s^2C \right) V_2 = \left(-\frac{1}{3} - s \right) V_2$$

$$V_1 = (+1 + 45G + 330) V_2$$

$$\frac{V_2}{V_1} = \frac{1}{3s^2C + 4sC + 1}$$

$$\text{So, for (i) } C = \frac{1}{2} \Rightarrow \frac{V_2}{V_1} = \frac{1}{\frac{3}{2}s^2 + 2s + 1}$$

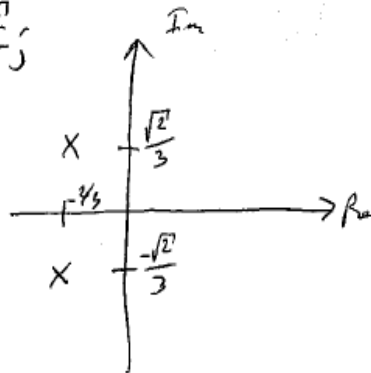
roots: poles = $-\frac{2}{3} + \frac{\sqrt{2}}{3}j, -\frac{2}{3} - \frac{\sqrt{2}}{3}j$



b) $C = 1F$

$$\frac{V_L}{V_i} = \frac{1}{3s^2 + 4s + 1} = \frac{1}{(3s+1)(s+1)}$$


poles = $-\frac{1}{3}, -1$

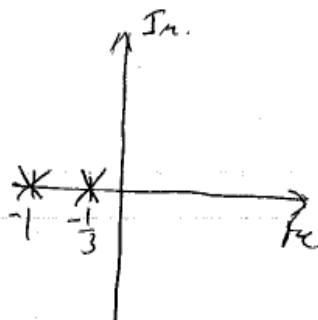

d) $C = 2F$

$$\frac{V_L}{V_i} = \frac{1}{6s^2 + 8s + 1} \Rightarrow \text{poles} = \frac{-2 \pm \sqrt{40}}{12}$$

= $-1.194, -0.14$

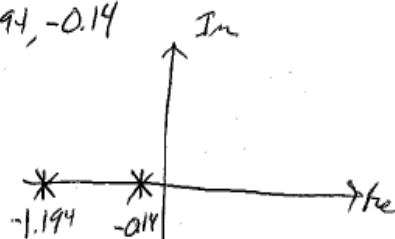

⑥


5.52 Use integrators, adders, and scalars to simulate the transfer function

$$H(s) = \frac{(s^2 + 2)}{(s^2 + 3s + 4)}$$

$$H(s) = \frac{Y(s)}{X(s)} = \frac{(s^2 + 2)}{(s^2 + 3s + 4)}$$

$$s^2 X(s) + 2X(s) = Y(s)s^2 + Y(s)3s + Y(s)4$$
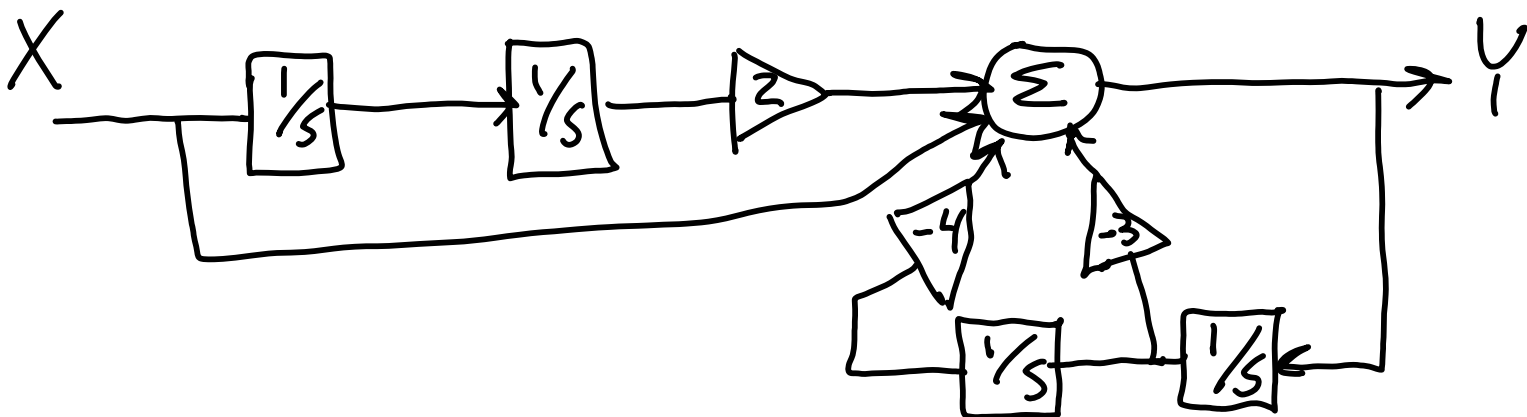
$$Y(s) = X(s) + \frac{2}{s^2} X(s) - \frac{3}{s} Y(s) - \frac{4}{s^2} Y(s)$$



7. (0 points) FoEE 5.17

5.17 For the circuit shown in Fig. P5.15, with $R = 2 \Omega$, $L = 1 \text{ H}$, and $C = 1 \text{ F}$, then

$$H_C(j\omega) = \frac{V_C}{V_1} = \frac{1}{1 + j\omega 2 + (j\omega)^2}$$

$$= \left(\frac{1}{1 + j\omega} \right) \left(\frac{1}{1 + j\omega} \right)$$


Thus $H_C(j\omega)$ can be expressed as the product $H_C(j\omega) = H_1(j\omega)H_2(j\omega)$, where $H_1(j\omega) = H_2(j\omega) = 1/(1 + j\omega)$. Use only the straight-line asymptotic to sketch the Bode plot—both the amplitude and phase responses—for $H_C(j\omega)$ by adding the Bode plots for $H_1(j\omega)$ and $H_2(j\omega)$. What type of filter is this?

⑦ FoEE 5.17 : $H_1(j\omega) = H_2(j\omega) = \frac{1}{1 + j\omega}$

$$|H_1(j\omega)| = |H_2(j\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$

$$\angle H_1(j\omega) = \angle H_2(j\omega) = -\tan^{-1} \omega$$


So,

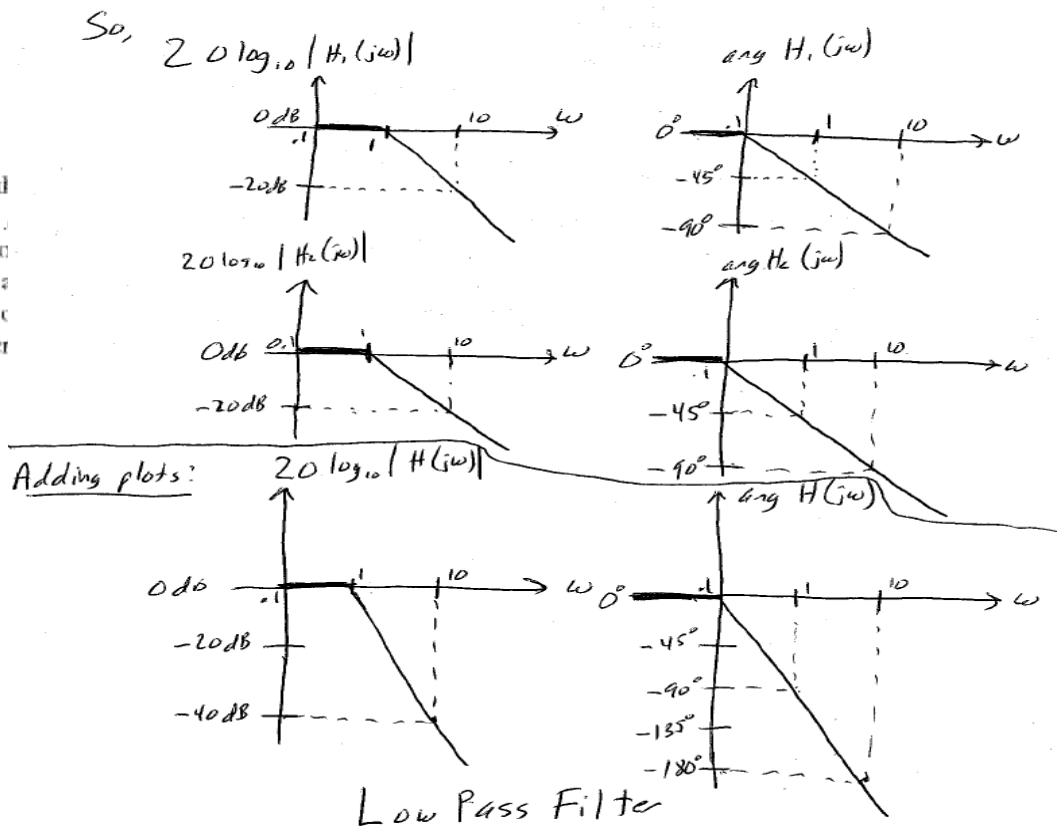

8. (0 points) FoEE 5.38

5.38 Consider the practical tank circuit shown in Fig. 5.17 on p. 285. Suppose that $R_s = 50 \Omega$, $L = 50 \text{ mH}$, and $C = 0.005 \mu\text{F}$. Approximate this admittance by a parallel RLC connection. What is the quality factor of this parallel connection?

⑧ FoEE 5.38

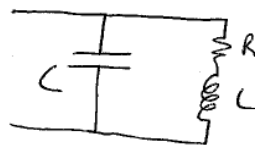


$$C = 0.005 \mu\text{F}$$

$$R = 50 \Omega$$

$$L = 50 \text{ mH}$$

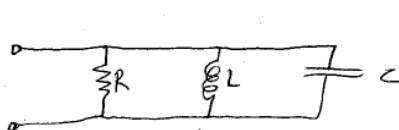This is a high Q coil, so we can approximate this as:



So, $R = \frac{50 \text{ mH}}{50 \cdot (0.005) \mu\text{F}}$

$$R = 200 \text{ k}\Omega$$

$$Q = R \sqrt{\frac{C}{L}} = 200 \text{ k} \sqrt{\frac{0.005 \mu\text{F}}{50 \text{ mH}}} = 63.2$$

where $R = \frac{L}{R_s C}$
See pgs. 285-286

5.51 Use integrators, adders, and scalers to simulate the transfer function

$$H(s) = \frac{4s}{(s^2 + 2s + 3)}$$

FoEE 5.51

$$H(s) = \frac{Y}{X} = \frac{4s}{s^2 + 2s + 3} \quad (s^2 + 2s + 3)Y = 4sX$$

$$s^2 Y + 2sY + 3Y = 4sX$$

$$Y + \frac{2Y}{s} + \frac{3Y}{s^2} = \frac{4X}{s}$$

$$Y = \frac{4X}{s} - \frac{2}{s}Y - \frac{3}{s^2}Y$$

