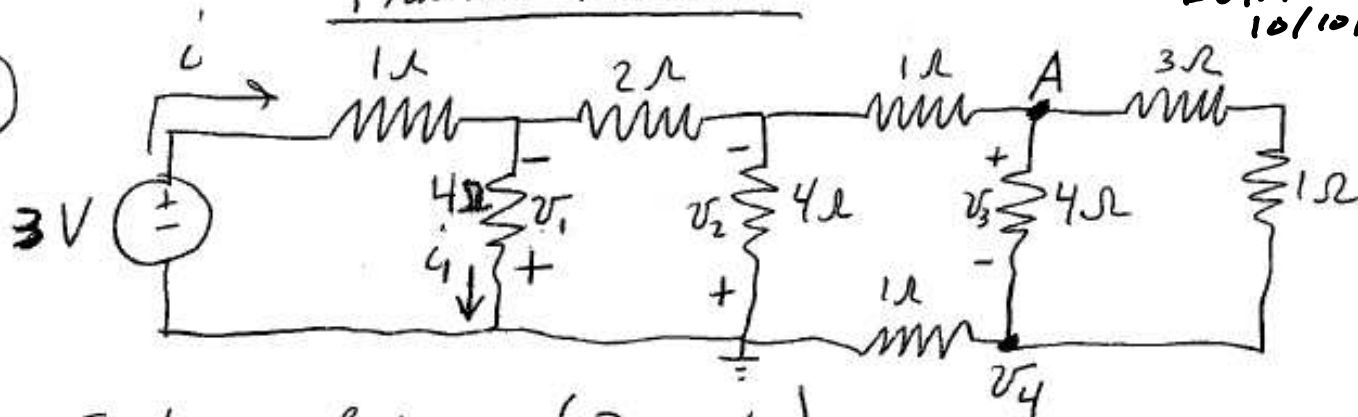


# Practice Problems

Handout 13  
E84: Fall '07  
10/10/07


①




Find  $v_1$  &  $i_1$ . (2 minutes)

② Write a KCL equation for node A in terms of  $v_2$ ,  $v_3$  and  $v_4$ . (5 min.)

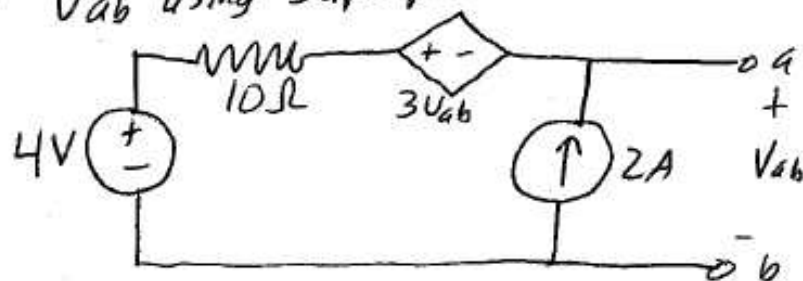③ Find  $V_{ab}$  using superposition in the following circuit (10 min)




④

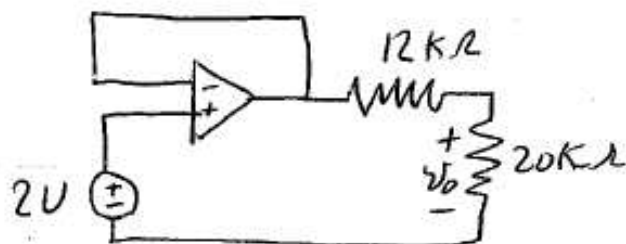


Find  $v_0$ . (5 min.)

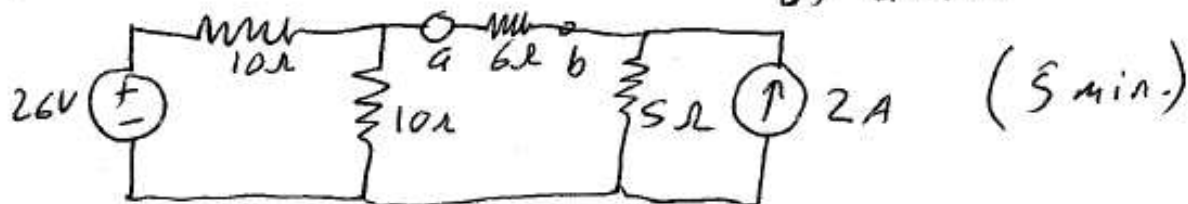⑤ Find the Thevenin & Norton Equivalents from the perspective of a & b. (5 min.)



What would you replace the  $6\Omega$  resistor with to get maximum power?

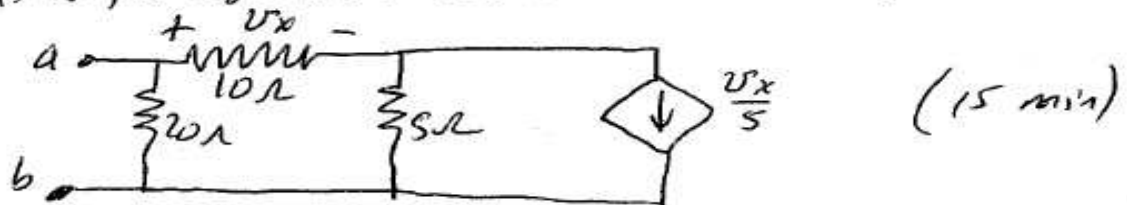
- ⑥ What is the equivalent resistance as seen by  $a$  &  $b$ :




- ⑦ Assuming a switch has been in position A for a long time and is moved to position B at  $t=0$ .

- a) What is  $i_c(0^+)$ ?  
b) What is  $v_o(t)$  for  $t \geq 0$ ?


10-  
(20 min.)

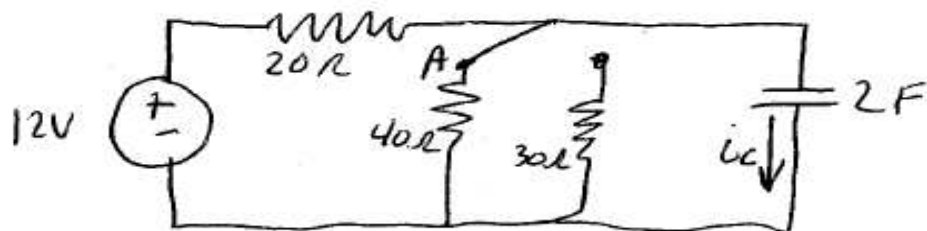

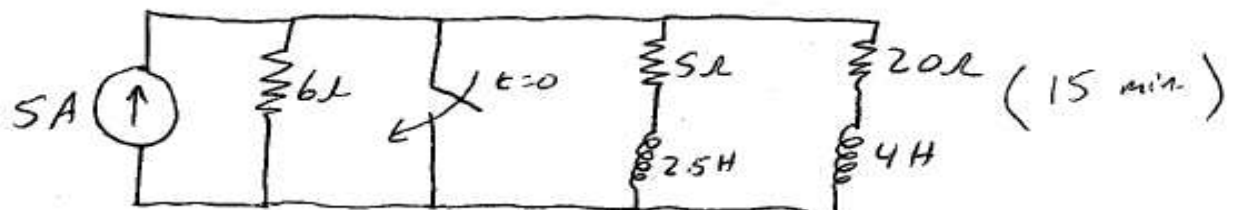- ⑧ Find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$  in the circuit below.



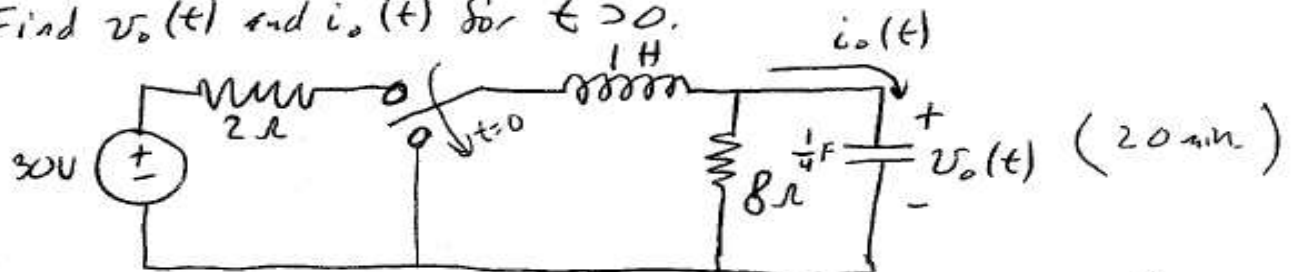- ⑨ Find  $v_o(t)$  and  $i_o(t)$  for  $t > 0$ .



What would  $R$  have to be to make this a critically damped circuit?