

[Next](#) [Up](#) [Previous](#)

**Next:** [About this document ...](#)

## E84 Home Work 6

1. The resistance  $R$  of a circuit is a real value which can be measured by a multimeter. However, the impedance  $Z$  of a component in the circuit is complex which cannot be measured directly. Instead, one can use an oscilloscope to find sinusoidal voltage  $\overline{v(t)}$  across and current  $\overline{i(t)}$  through the component, and then obtain the impedance as the ratio between the complex representations of the voltage and current. Suppose we find:

$$v(t) = 12\cos(1000t - 30^\circ), \quad i(t) = 6\cos(1000t + 15^\circ)$$

Find the impedance (both resistance and reactance) and the admittance (both conductance and susceptance) of the circuit.

### Solution:

Represent voltage and current in complex forms:

$$v(t) = \operatorname{Re}[12e^{j(1000t-30^\circ)}], \quad i(t) = \operatorname{Re}[6e^{j(1000t+15^\circ)}]$$

$$Z = 2e^{-j45^\circ} = 2\angle -45^\circ = \sqrt{2} - j\sqrt{2}$$

$$R = \sqrt{2}, \quad X = -\sqrt{2}.$$

$$Y = 1/Z = G + jB = G + jB, \quad G = R/(R^2 + X^2) = \sqrt{2}/4,$$

$$B = -X/\sqrt{R^2 + X^2} = \sqrt{2}/4$$

2. A voltage  $v(t) = 120\sqrt{2}\cos(1000t + 90^\circ)V$  (volt) is applied to a resistor  $R = 15\Omega$ , a capacitor  $C = 83.3\mu F$  and an inductor  $L = 30\text{ mH}$  connected in parallel. Find the over all steady

state current  $\underline{i = i_R + i_C + i_L}$  by phasor method.

### Solution:

Express input voltage as a phasor  $\dot{V} = 120\angle 90^\circ$ . Then

$$\dot{I}_R = \dot{V}/R = 120\angle 90^\circ / 15 = 0 + j8A$$

$$\dot{I}_C = \dot{V}/Z_C = j\omega C \dot{V} = (0.00833\angle 90^\circ)(120\angle 90^\circ) = 10\angle 180^\circ = -10 + j0A$$

$$\dot{I}_L = \dot{V}/Z_L = \dot{V}/j\omega L = (120\angle 90^\circ)/(30\angle 90^\circ) = 4 + j0A.$$

By KCL, we have

$$\dot{I} = \dot{I}_R + \dot{I}_C + \dot{I}_L = (0 - 10 + 4) + j(8 + 0 + 0) = -6 + j8 = 10\angle 127^\circ A$$

$$i(t) = 10\sqrt{2} \cos(1000t + 127^\circ) A$$

3. A voltage  $v(t) = 12\sqrt{2} \cos 5000t$  (volt V) is applied to a circuit composed of two branches in parallel. One branch has a capacitor  $C = 10\mu F$ , while the other has a resistor  $R = 20\Omega$  and an inductor  $L = 3mH$  in series. Using phasor method, find the impedances  $Z_C$  and  $Z_{RL}$  of the two branches, and then the overall combined impedance  $Z_{all}$  of the circuit. Then find the steady state current  $\underline{i(t)}$  through the circuit.

### Solution:

$$Z_R = R = 20 + j0 = 20\angle 0^\circ \Omega, \quad Z_L = j\omega L = j5000 \times 0.003 = 15\angle 90^\circ \Omega,$$

$$Z_C = 1/j\omega C = -j/5000 \times 10^{-5} = -j20 = 20\angle -90^\circ \Omega$$

$$Z_{RL} = Z_R + Z_L = 20 + j15 = 25\angle 37^\circ \Omega$$

$$Z_{all} = Z_C // Z_{RL} = Z_C Z_{RL} / (Z_C + Z_{RL}) = 25\angle 37^\circ 20\angle -90^\circ / (20 + j15 - j20) = 500\angle -53^\circ / 20.6\angle -14^\circ = 24.3\angle -39^\circ = 18.9 - j15.3\Omega$$

$$\dot{I} = \dot{V}/Z = 12\angle 0^\circ / 24.3\angle -39^\circ = 0.49\angle 39^\circ A$$

$$i(t) = 0.49\sqrt{2} \cos(5000t + 39^\circ) A$$

4. Solve the problem above again but this time use the admittances  $Y_C = 1/Z_C$ ,  $Y_{RL} = 1/Z_{RL}$ ,  $Y_{all} = 1/Z_{all}$  (instead of the impedances  $Z_C$ ,  $Z_{RL}$ ,  $Z_{all}$ ). Recall that Ohm's law becomes  $\dot{I} = \dot{V}/Z = \dot{V}Y$ . (Make sure all impedances you found in previous problem are correct before you find the admittances as their reciprocals.)

### Solution:

$$Y_C = 1/Z_C = 1/20\angle 0^\circ = 0.05\angle 90^\circ = 0 + j0.05 \text{ S}$$

$$Y_{RL} = 1/Z_{RL} = 1/25\angle 37^\circ = 0.04\angle -37^\circ = 0.032 - j0.024 \text{ S}$$

$$Y_{all} = Y_C + Y_{RL} = 0 + j0.05 + 0.032 - j0.024 = 0.032 + j0.026 = 0.04\angle 39^\circ$$


$$I_C = Y_C V = 0.05\angle 90^\circ \times 12\angle 0^\circ = 0.6\angle 90^\circ \text{ A}$$

$$I_{RL} = Y_{RL} V = 0.04\angle -37^\circ \times 12\angle 0^\circ = 0.48\angle -37^\circ \text{ A}$$

$$I = I_C + I_{RL} = 0 + j0.6 + 0.384 - j0.288 = 0.384 + j0.312 = 0.49\angle 39^\circ$$

Alternatively,  $I = Y_{all} V = 0.041\angle 39^\circ \times 12\angle 0^\circ = 0.49\angle 39^\circ$

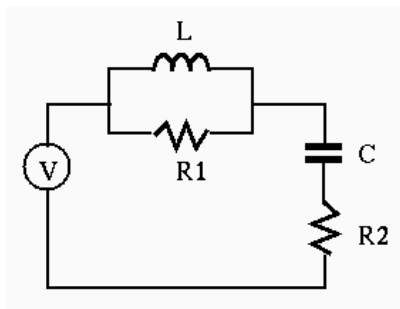5. Find the output voltage  $\underline{v_{out}(t)}$  across the right most branch containing  $R_2$  and  $C$ , when  $\omega = 0$  and  $\omega \rightarrow \infty$  and the input  $\underline{v_{in}(t)} = V = 10 \cos(\omega t)$ , assuming  $R_1 = 100\Omega$ ,  $R_2 = 100\Omega$ ,  $C = 10\mu F$  and  $L = 10 \text{ mH}$ .



### Solution

When  $\omega = 0$ , the inductor is short circuit, and the capacitor is open circuit,  $\overline{v_{out}(t) = v_{in}(t)}$ . When  $\omega = \infty$ , the inductor is open circuit, and the capacitor is short circuit,  $\underline{v_{out}(t) = v_{in}(t)/2 = 5 \cos(\omega_0 t)}$ .

---

- [About this document ...](#)
- 

[Next](#) [Up](#) [Previous](#)

**Next:** [About this document ...](#)

*Ruye Wang 2008-01-16*