$$R_1 = R_2 = 5\,\Omega$$

$$v_{in}(t) = 10 + 20\cos 5t + 30\cos 10t$$

$$v_{out}(t)$$

$$v'_{out}(t) = 10 \times \frac{5}{5+5} = 5 V$$

$$j5//(-j20) + (-j20/3) = 0$$

$$v_{out}''(t) = 0$$

$$j10//(-j10) + (-j10/3) = \infty$$

$$v_{out}^{""}(t) = v_{in}(t)\frac{5}{5+5} = 15\cos 10t \ V$$

$$v_{out}(t) = v'_{out}(t) + v'''_{out}(t) = 5 + 15\cos 10t V$$

$$R_1 = R_2 = R_3 = 1k\Omega$$

$$\tau = L/R$$

$$\tau = L/R = 10^{-6}$$

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau} = 6 + (4 - 6)e^{-t/0.001} = 6 - 2e^{-1000t}$$
 (mA)

 $v_L(t) = L \frac{d}{dt} i(t) = -2L \frac{d}{dt} e^{-t/\tau} = 2e^{-t/\tau} V$

$$R_2 = 2\Omega$$

$$R_3 = 8\Omega$$

$$v'(0^+)$$

$$v''(0^+)$$

$$v(t) = v'(t) + v''(t)$$

$$i_L(0^-) = 20V/10\Omega = 2A$$

$$i_L(0^+) = i_L(0^-) = 2A$$

$$v'(0^+) = i_L(0^+)R_3 = 2 \times 8 = 16V$$

$$\tau = L/R = 2H/(2+10+8)\Omega = 0.1$$

$$i_L(t) = 2e^{-t/\tau}A$$

$$v'(t) = v'(0^+)e^{-t/tau} = 16e^{-10t}$$

$$v''(0^+) = -1.25 \times 8 = -10V$$

$$v''(\infty) = -1.25 \times \frac{8+12}{8 \times 12} = -6V$$

$$v''(t) = v''(\infty) + [v''(0^+) - v''(\infty)]e^{-t/\tau} = -6 + (-10 + 6)e^{-10t} = -6 - 4e^{-10t}$$

$$v(t) = v'(t) + v''(t) = 16e^{-10t} + (-6 - 4e^{-10t}) = 12e^{-10t} - 6$$