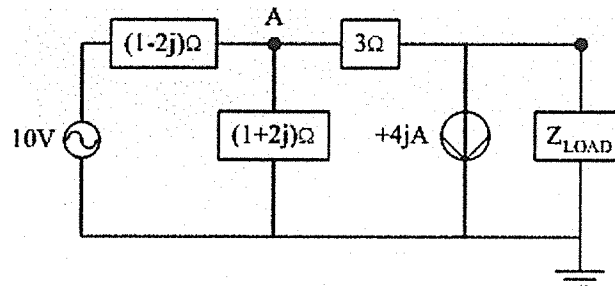


E-84 Problem Set #5 Key

Ch 3 #11.

11. Show that for the circuit shown below: $Z_{th} = 5.5 \Omega$ and $V_{th} = 13/-67.4^\circ \text{ V}$



Hint: first find V_A using node analysis with the load removed.

To calculate Z_{Th} replace the current source with an open circuit and the voltage source with a short circuit. That makes the impedance from the top of the load to ground 3Ω plus the other two impedance going in parallel to ground. Hence

$$Z_{Th} = 3 + (1 + 2j)(1 - 2j)/(1 + 2j + 1 - 2j) = 3 + 5/2 = \underline{5.5 \Omega}$$

To calculate V_{Th} we remove the load and calculate V_A using node analysis at A: We have

$$(10 - V_A)/(1 - 2j) = V_A/(1 + 2j) + 4j \text{ so that collecting terms,}$$

$$\frac{10}{1 - 2j} - 4j = V_A \left(\frac{1}{1 + 2j} + \frac{1}{1 - 2j} \right) = \frac{2V_A}{5}, \text{ so that (multiplying the first term}$$

by $(1 + 2j)/(1 + 2j)$ we have;

$$2((1 + 2j) - 4j) = 2V_A/5 \text{ from which we easily find } \underline{V_A = 5 \text{ V.}}$$

But with Z_{LOAD} removed, $V_{Th} = V_A - 12j$ (where the second term is the voltage drop across the 3Ω resistor. Hence



$$\underline{V_{Th} = 5 - 12j} \text{ (which also equals } 13/\tan^{-1}(-12/5) = 13/-67.4^\circ$$

E-84 Problem Set #5 Key - continued

Chapter 5

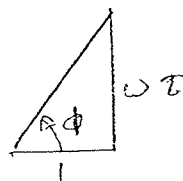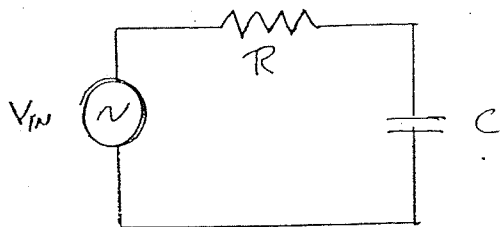1. a. Show that for a sinusoidal input voltage $v_{IN} = A \sin \omega t$ the steady state solution for the voltage across the capacitor in the R-C circuit shown below is

$$v_{ss}(t) = \frac{A \sin(\omega t - \phi)}{\sqrt{1 + \omega^2 \tau^2}} \quad \text{where } \phi = \tan^{-1} \omega \tau \text{ and } \tau = RC$$



Thus the voltage on the capacitor oscillates at the same frequency as the source, but with a smaller amplitude and a time lag, $t_{lag} = \phi/\omega$.

- b. Show that for low frequency oscillations, when $\omega \tau \ll 1$, the time lag $t_{lag} \approx \tau$, while for high frequency oscillations when $\omega \tau \gg 1$, the time lag $t_{lag} \approx T/4$, where $T = 1/f = 2\pi/\omega$ is the period of the oscillations.

- c. Show that the complete solution, including the homogeneous (or transient) term is

$$v_C(t) = v_{ss}(t) + C e^{-t/\tau}, \quad \text{where, for } v_C(0) = 0, \quad C = (A \sin \phi) / (1 + \omega^2 \tau^2)^{1/2}$$

- a. The governing equation for this system is:

$$v_{IN} = iR + v_C = RC \frac{dv_C}{dt} + v_C = \tau \dot{v}_C + v_C$$

If we try the particular solution

$$v_{ss}(t) = \frac{A \sin(\omega t - \phi)}{\sqrt{1 + \omega^2 \tau^2}}$$


$$(\tau = RC)$$

Then

$$\dot{v}_{ss} = \frac{A \omega \cos(\omega t - \phi)}{\sqrt{1 + \omega^2 \tau^2}}$$

BST (3)
PS#5

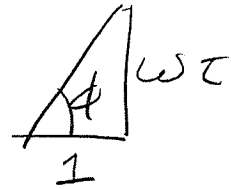However for $\phi = \tan^{-1} \omega \tau$



$$\therefore \frac{1}{\sqrt{1+\omega^2\tau^2}} = \cos\phi$$

$$\frac{\omega\tau}{\sqrt{1+\omega^2\tau^2}} = \sin\phi$$

Hence

$$v_{ss} + \tau \dot{v}_{ss} = A \left[\cos\phi \sin(\omega t - \phi) + \sin\phi \cos(\omega t - \phi) \right]$$

$$\sin(\omega t - \phi + \phi) = \sin \omega t!$$

(Using $\sin a \cos b + \cos a \sin b = \sin(a+b)$)

$$\therefore v_{ss} + \tau \dot{v}_{ss} = \underline{A \sin \omega t = v_{in}}$$

b. $v_{ss} = \frac{A \sin[\omega t - t_{lag}]}{\sqrt{1+\omega^2\tau^2}}$ where $\underline{t_{lag} = \frac{\phi}{\omega}}$

$$\therefore t_{lag} = \frac{\tan^{-1}(\omega\tau)}{\omega}$$

(i) for $\omega\tau \ll 1$, $\tan^{-1} \omega\tau \approx \omega\tau$

$$t_{lag} \approx \frac{\omega\tau}{\omega} = \tau$$

(iii) for $\omega\tau \gg 1$, $\tan^{-1}(\omega\tau) \approx \frac{\pi}{2}$

BST ④

PS# 5

∴

$$t_{\text{lag}} \cong \frac{\pi}{2\omega}$$

$$\text{But } \omega = 2\pi f = \frac{2\pi}{T}$$

$$\therefore t_{\text{lag}} \cong \frac{\pi T}{2 \cdot 2\pi} = \underline{\underline{\frac{T}{4}}}$$

c) As shown in notes: $v_c(t) = v_{ss}(t) + v_H(t)$ where

$$\tau \dot{v}_H + v_H = 0$$

∴

$$\text{Try } v_H = C e^{st} \Rightarrow \dot{v}_H = s C e^{st}$$

so that we get

$$C e^{st} [s\tau + 1] = 0 \Rightarrow s = \underline{\underline{-\frac{1}{\tau}}}$$

$$\therefore v_H = C e^{-t/\tau}$$

$$\& v_c(t) = C e^{-t/\tau} + \frac{A \sin(\omega t - \phi)}{\sqrt{1 + \omega^2 \tau^2}}$$

To find C, suppose $v_c(0) = 0$:

$$\text{Then } 0 = C + \frac{A \sin(-\phi)}{\sqrt{1 + \omega^2 \tau^2}} \Rightarrow C = \underline{\underline{\frac{A \sin \phi}{\sqrt{1 + \omega^2 \tau^2}}}}$$

3. a. Prove that for an underdamped series R-L-C circuit, with $v(t) = \sin \omega_0 t$

$$v_c(t) = Q \left[e^{-\alpha t} \left(\cos \beta t + \frac{\alpha}{\beta} \sin \beta t \right) - \cos \omega_0 t \right], \text{ where } Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{\omega_0}{2\alpha} \text{ and } v_c(0) = v_c'(0) = 0$$

Thus as expected from the results in Chapter 4 for a band pass filter, the steady state amplitude of these oscillations is Q (the quality factor for the filter). Note that for a high Q system, the damping is minimal, so that $\alpha \ll \omega_0$ and $\beta \approx \omega_0$, so that

$$v_c(t) \approx -Q(1 - e^{-\alpha t}) \cos \omega_0 t,$$

b. Show that for a high Q system it takes about Q cycles before the full amplitude of the steady state solution is achieved. Hint: show that after Q cycles, $\alpha t = \pi$, so that $e^{-\alpha t}$ becomes negligible.

a) First as shown in notes the homogeneous soln to the equation

$$(1) \quad v_c(t) = \frac{1}{\omega_0^2} \ddot{v}_c + \frac{2\alpha}{\omega_0^2} \dot{v}_c + v_c$$

$$\text{is } v_c = e^{-\alpha t} (A \cos \beta t + B \sin \beta t)$$

For $v_p(t)$ try $v_p = C \sin(\omega_0 t + \phi)$ - to match $v(t)$ in we set in (1)

$$\sin \omega_0 t = -C \sin(\omega_0 t + \phi) + \frac{2\alpha}{\omega_0^2} C \cos(\omega_0 t + \phi) + C \sin \omega_0 t$$

Hence we let $\phi = +90^\circ$ so that $\cos(\omega_0 t + \phi) = -\sin \omega_0 t$
or

$$\sin \omega_0 t = -\frac{2\alpha C}{\omega_0^2} \sin \omega_0 t \Rightarrow \boxed{C = -\frac{\omega_0^2}{2\alpha} = -Q}$$

\therefore before apply BC's we have

$$(\text{using } v_p = -Q \sin(\omega_0 t + 90^\circ) = -Q \cos \omega_0 t)$$

BST ⑥

PS#5

$$(2) v_c(t) = e^{-\alpha t} (A \cos \beta t + B \sin \beta t) - Q \cos \omega_0 t$$

To find A & B we use The initial conditions

$$v_c(0) = A - Q = 0 \Rightarrow \underline{A = Q}$$

$$v_c'(0) = -\alpha A + B\beta = 0 \Rightarrow \underline{B = \frac{\alpha A}{\beta} = \frac{\alpha Q}{\beta}}$$

\therefore Substituting These values into (2),

$$v_c(t) = Q \left[e^{-\alpha t} \left(\cos \beta t + \frac{\alpha}{\beta} \sin \beta t \right) - \cos \omega_0 t \right]$$

For a high Q system $\frac{\alpha}{\beta} \ll 1$ and $\beta \approx \omega_0$

\therefore to a good approximation

$$v_c(t) = Q \cos \omega_0 t (e^{-\alpha t} - 1)$$

b) Recall That $2\alpha = \frac{\omega_0}{Q} = \frac{2\pi f_0}{Q} = \frac{2\pi}{QT}$

where $T = \frac{1}{f_0}$ is The period for an oscillation

$$\alpha = \frac{\pi}{QT} \quad \text{and for } t_0 = QT, \quad \underline{\alpha t_0 = \pi}$$

\therefore After Q cycles $t = t_0 = QT$ and

$$e^{-\alpha t_0} = e^{-\pi} = .0432 \Rightarrow \underline{v_c(t) \approx -Q \cos \omega_0 t}$$

4. a. Show that to a good approximation if a voltage V is applied at t' for a very short time dt' , the voltage across the capacitor for an R-C circuit with time constant τ is

$$v_C(t) \approx (Vdt'/\tau)e^{-(t-t')/\tau}$$

b. If the same short pulse at t' is applied to an L-C circuit with resonant frequency ω_0 , show that


$$v_C(t) \approx (V\omega_0 dt') \sin \omega_0(t-t')$$

These results are called the impulse response of these systems, and Vdt' is the "strength" of the impulse.

These results are easily extended to a "series of impulses" with strength $V(t')dt'$, to show that for a circuit driven by an arbitrary function $V(t')$, the voltage across the capacitor is given by

$$v_C(t) = (1/\tau) \int_0^t V(t') e^{-(t-t')/\tau} dt', \text{ for an R-C circuit, and}$$

$$v_C(t) = \omega_0 \int_0^t V(t') \sin \omega_0(t-t') dt', \text{ for an L-C circuit, and}$$

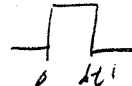a) For a pulse of length dt' ;  we've shown


$$v_C(t) = V [1 - e^{-t/\tau}] - V [1 - e^{-(t-dt')/\tau}]$$

$$= V e^{-t/\tau} [e^{dt'/\tau} - 1] \approx V e^{-t/\tau} [1 + \frac{dt'}{\tau} - 1]$$

$$= \frac{V e^{-t/\tau} dt'}{\tau} \quad (\text{pulse applied at } t=0)$$

If pulse is applied at t' we get the same result but with $t-t'$ replacing t ; i.e.

$$v_C(t) = \begin{cases} 0, & t < t' \\ \frac{V}{\tau} e^{-(t-t')/\tau} dt', & \text{for } t > t' \end{cases}$$

b) For  we've shown that

$$\text{for } v_C(t) = V; \quad v_C(t) = V [1 - \cos \omega_0 t] \quad (\text{Eq. 5.24})$$

∴ for $V(t) \rightarrow \int_0^{dt'} \square$

$$\begin{aligned} V_c(t) &= V[1 - \cos \omega_0 t] - V[1 - \cos \omega_0 (t - dt')] \\ &= V[\cos \omega_0 (t - dt') - \cos \omega_0 t] \end{aligned}$$

But $\cos \omega_0 (t - dt') = \cos \omega_0 t \cos \omega_0 dt' + \sin \omega_0 t \sin \omega_0 dt'$

and as $dt' \rightarrow 0$, $\cos \omega_0 dt' \approx 1$ while $\sin \omega_0 dt' \approx \omega_0 dt'$

∴ we get

$$\begin{aligned} V_c(t) &\approx V[\cos \omega_0 t + \omega_0 dt' \sin \omega_0 t - \cos \omega_0 t] \\ &= V \omega_0 dt' \sin \omega_0 t \end{aligned}$$

If The short pulse is applied at t' we get The same result (for $t > t'$) but with $t \rightarrow (t - t')$; i.e.

$$V_c(t) = \begin{cases} 0, & t < t' \\ V \omega_0 \sin \omega_0 (t - t') dt', & t > t' \end{cases}$$

Hence, for an arbitrary $V(t')$ we have

for RC: $V_c(t) = \frac{1}{\tau} \int_0^t V(t') e^{-(t-t')/\tau} dt'$

for RL: $V_c(t) = \omega_0 \int_0^t V(t') \sin \omega_0 (t - t') dt'$