

**2.26** Assume clockwise mesh currents for the circuit shown in Fig. P2.26 (below). Use mesh analysis to find these mesh currents.

**2.27** For the circuit shown in Fig. P2.27, find  $v_o$  when the ideal amplifier (a) is an op amp, and (b) has finite gain  $A$ .

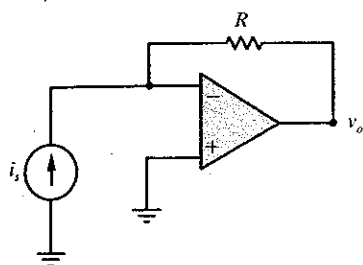


Fig. P2.27

**2.28** For the op-amp circuit shown in Fig. P2.28, find (a)  $v_o$ , and (b)  $i_o$ .

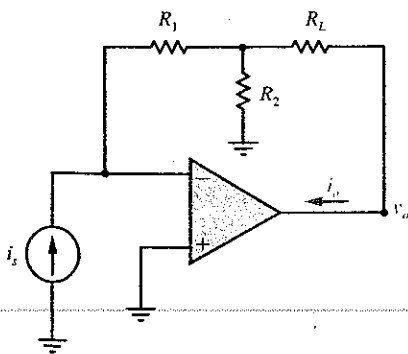


Fig. P2.28

**2.29** For the op-amp circuit shown in Fig. P2.29, find (a)  $v_o$ , and (b)  $i_o$ .

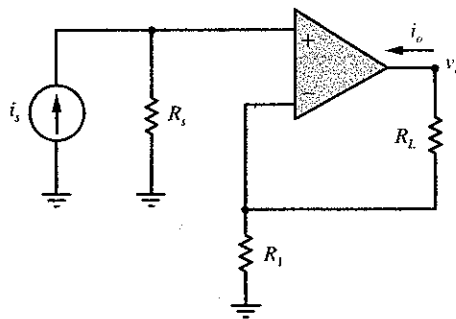


Fig. P2.29

**2.30** The op-amp circuit shown in Fig. P2.30 is known as a **negative-impedance converter**. For this circuit, find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ .

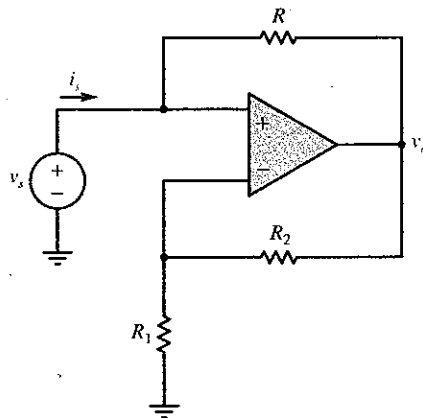


Fig. P2.30

**2.31** For the op-amp circuit shown in Fig. P2.31, find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ . (See p. 104.)

**2.32** For the op-amp circuit shown in Fig. P2.31, interchange the 1- $\Omega$  and 2- $\Omega$  resistors, and find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ . (See p. 104.)

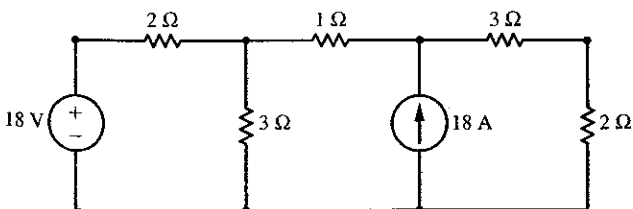


Fig. P2.26

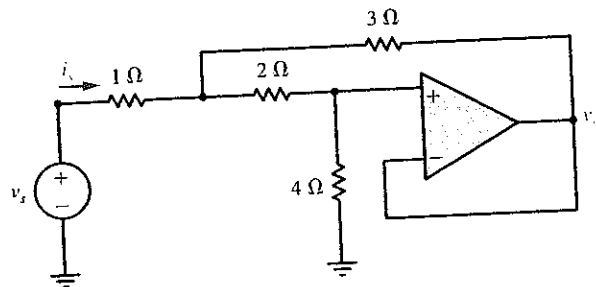


Fig. P2.31

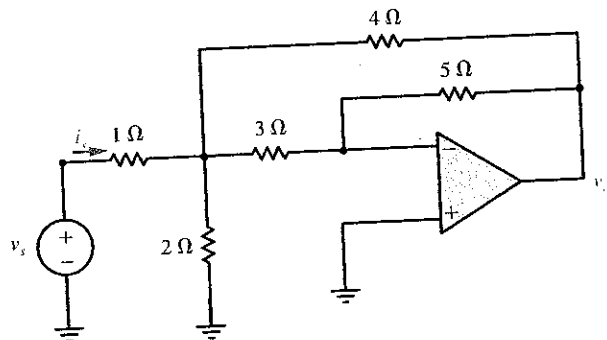


Fig. P2.33

**2.33** For the op-amp circuit shown in Fig. P2.33, find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ .

**2.34** For the op-amp circuit shown in Fig. P2.34, find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ . (See p. 105.)

**2.35** For the op-amp circuit shown in Fig. P2.35, find  $v_o$ .

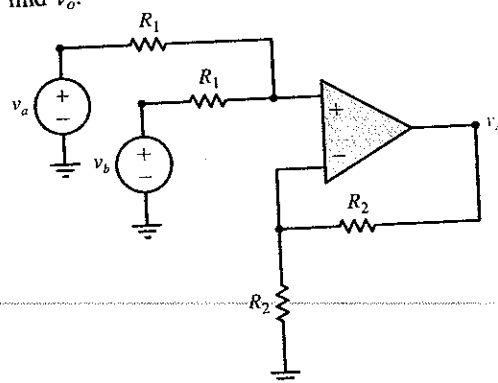


Fig. P2.35

**2.36** For the op-amp circuit shown in Fig. P2.36, find  $v_o$ . (See p. 105.)

**2.37** Consider the circuit shown in Fig. P2.37. (a) Find the Thévenin equivalent of the circuit to the left of terminals  $a$  and  $b$ . (b) Use the Thévenin-equivalent circuit to find the power absorbed by  $R_L = 2 \Omega$ . (c) Determine the value of  $R_L$ , which absorbs the maximum amount of power, and find this power.

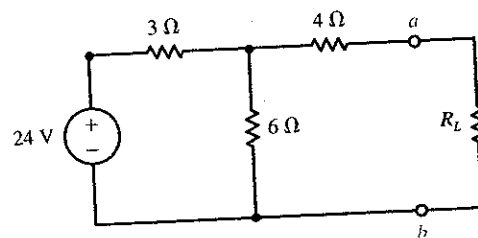


Fig. P2.37

**2.38** For the circuit shown in Fig. P2.37, connect a  $12\text{-}\Omega$  resistor between terminal  $a$  and the positive terminal of the voltage source. (a) Find the Thévenin equivalent of the resulting circuit to the left of ter-

**2.45** Find the Thévenin equivalent of the op-amp circuit shown in Fig. P2.45. (Hint: To find  $R_o$ , apply a current source  $i_o$  and calculate the resulting voltage  $v_o$ .)

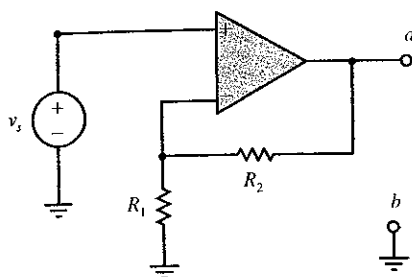


Fig. P2.45

**2.46** Find the Thévenin equivalent of the op-amp circuit shown in Fig. P2.46. (Hint: To find  $R_o$ , apply a current source  $i_o$  and calculate the resulting voltage  $v_o$ .)

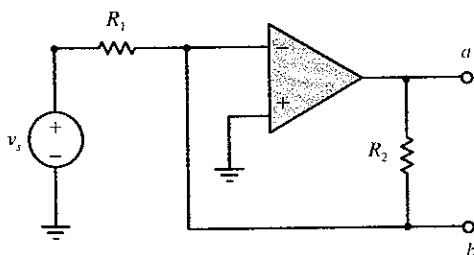


Fig. P2.46

**2.47** Show that the Norton equivalent of the circuit shown in Fig. P2.47 is an ideal current source. (Hint: To find  $R_o$ , apply a voltage source  $v_o$  and calculate the resulting current  $i_o$ .)

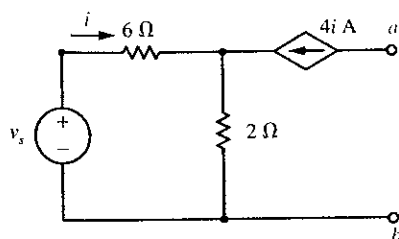


Fig. P2.47

**2.48** For the circuit shown in Fig. P2.48, find (a) the Norton-equivalent circuit, and (b) the Thévenin-equivalent circuit.

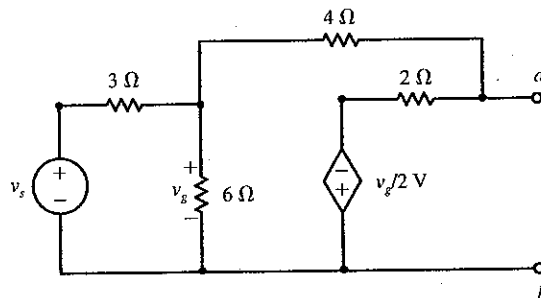


Fig. P2.48

**2.49** Figure P2.49 demonstrates the concept of a **source transformation**. Specifically, the voltage source  $v_s$  connected in series with a resistance  $R_s$  is equivalent to a current source  $v_s/R_s$  connected in parallel with  $R_s$ . Without using Thévenin's or Norton's theorem, confirm the equivalence of Fig. P2.49a and b by writing expressions relating  $i$  and  $v$ .

**2.50** Figure P2.50 also demonstrates the concept of a **source transformation**. Specifically, the current source  $i_g$  connected in parallel with  $R_g$  is equivalent to a voltage source  $R_g i_g$  connected in series with a resistance  $R_g$ . Without using Thévenin's or Norton's theorem, confirm the equivalence of Fig. P2.50a and b by writing expressions relating  $i$  and  $v$ .

**2.51** Use source transformations as described in Problems 2.49 and 2.50 to reduce the circuit given in Fig. P2.8 to a circuit having one mesh. Calculate  $v_3$  from this reduced circuit.

**2.52** Use source transformations as described in Problems 2.49 and 2.50 to reduce the circuit given in Fig. P2.9 to a circuit having one mesh. Calculate  $v_3$  from this reduced circuit.

**2.53** Use source transformations as described in Problems 2.49 and 2.50 and combine independent sources to reduce the circuit given in Fig. P2.39 to a circuit having one mesh. Calculate  $i$  from this reduced circuit when  $R_L = 6 \Omega$ .

## Problems

**3.1** For the circuit shown in Fig. P3.1a, suppose that  $i(t)$  is described by the function given in Fig. P3.1b. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $v_R(t)$ , and (e)  $v_s(t)$ .

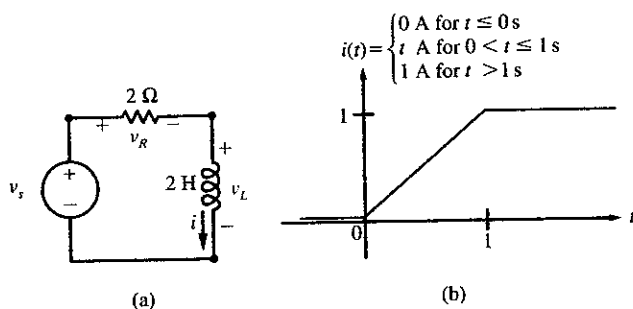


Fig. P3.1

**3.2** For the circuit shown in Fig. P3.1a, suppose that  $i(t)$  is described by the function given in Fig. P3.2. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $v_R(t)$ , and (e)  $v_s(t)$ .

**3.3** For the circuit shown in Fig. P3.3, suppose that  $i(t)$  is described by the function given in Fig. P3.1b. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $i_R(t)$ , and (e)  $i_s(t)$ .

**3.4** For the circuit shown in Fig. P3.3, suppose that  $i(t)$  is described by the function given in Fig. P3.2. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $i_R(t)$ , and (e)  $i_s(t)$ .

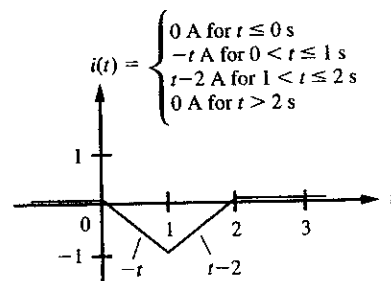


Fig. P3.2

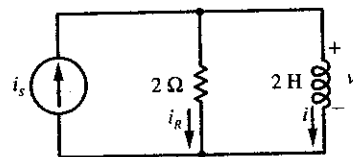


Fig. P3.3

**3.5** For the circuit shown in Fig. P3.5, suppose that  $i(t)$  is described by the function given in Fig. P3.1b. Sketch (a)  $v_R(t)$ , (b)  $v_L(t)$ , and (c)  $v(t)$ .

**3.6** For the circuit shown in Fig. P3.5, suppose that  $i(t)$  is described by the function given in Fig. P3.2. Sketch (a)  $v_R(t)$ , (b)  $v_L(t)$ , and (c)  $v(t)$ .

**3.7** For the circuit shown in Fig. P3.7a, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $w_C(t)$ , (c)  $p_R(t)$ , (d)  $v_R(t)$ , and (e)  $v_s(t)$ .

**3.8** For the circuit shown in Fig. P3.8, suppose that  $v(t)$  is described by the function given in Fig. P3.7b.

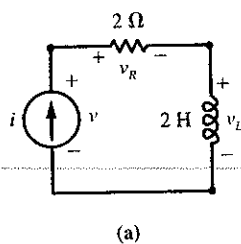


Fig. P3.5

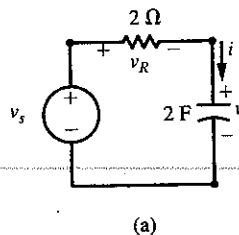


Fig. P3.7

Sketch (a)  $i(t)$ , (b)  $w_C(t)$ , (c)  $p_R(t)$ , (d)  $i_R(t)$ , and (e)  $i_s(t)$ .

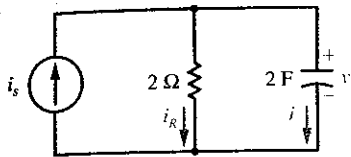


Fig. P3.8

**3.9** For the op-amp circuit shown in Fig. P3.9, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

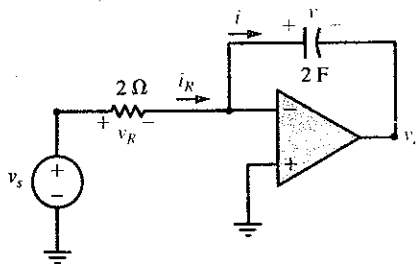


Fig. P3.9

**3.10** For the op-amp circuit shown in Fig. P3.9, connect an additional 2- $\Omega$  resistor in parallel with the capacitor. Suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

**3.11** For the op-amp circuit shown in Fig. P3.11, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

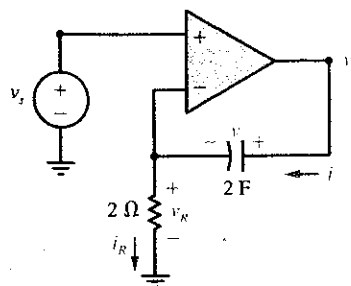


Fig. P3.11

**3.12** For the op-amp circuit given in Fig. P3.11, connect an additional 2- $\Omega$  resistor in parallel with the capacitor. Suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

**3.13** For the op-amp circuit shown in Fig. P3.13, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

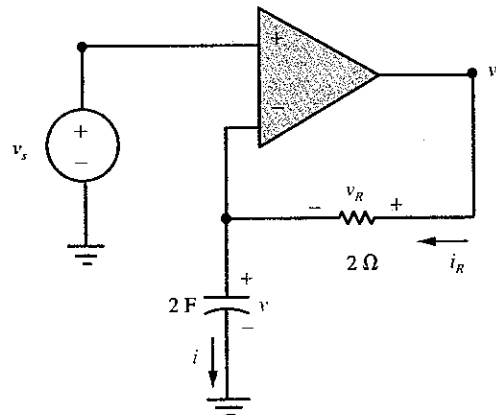


Fig. P3.13

**3.14** For the op-amp circuit shown in Fig. P3.13, connect an additional 2- $\Omega$  resistor in parallel with the capacitor. Suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

**3.15** Show the following: (See p. 178.)

- (a) Inductors connected in series can be combined as depicted in Fig. P3.15a.
- (b) Inductors connected in parallel can be combined as depicted in Fig. P3.15b.
- (c) Capacitors connected in parallel can be combined as depicted in Fig. P3.15c.
- (d) Capacitors connected in series can be combined as depicted in Fig. P3.15d.

**3.16** For the circuit shown in Fig. P3.1a, suppose that  $v(t)$  is described by the function given in Fig. P3.16. Sketch (a)  $i(t)$ , (b)  $v_R(t)$ , and (c)  $v_s(t)$ . (See p. 178.)