$$i=1,\cdots,n$$

$$\frac{V_1 - V_0}{R} + \frac{V_2 - V_0}{R} + \frac{V_3 - V_0}{R} = \frac{V_0}{R}, \quad V_0 = \frac{V_1 + V_2 + V_3}{4}$$

$$V_0 = \frac{1}{n+1} \sum_{i=1}^{n} V_i$$

$$V_2 = V_3 = 10V$$

$$R_1 = R_5 = 10\Omega$$

$$R_2 = R_4 = 5\Omega$$

$$R_3 = 6\Omega$$

$$V_{ab} = V_a - V_b = V_1 \frac{R_5}{R_1 + R_5} - V_2 \frac{R_4}{R_2 + R_4} = 20 \frac{10}{10 + 10} - 10 \frac{5}{5 + 5} = 10 - 5 = 5$$

$$R_T = R_1//R_5 + R_6 + R_2//R_4 = \frac{R_1 R_5}{R_1 + R_5} + R_6 + \frac{R_4 R_2}{R_2 + R_4} = 9$$

$$I = \frac{V_T - V_3}{R_T + R_3} = \frac{5 - 10}{9 + 6} = -\frac{1}{3}$$

$$V_{ab} = -\frac{1}{3} \times 6 + 10 = 8V$$

$$R_2 = R_4 = 4\Omega$$

$$R_1 = 2\Omega$$

$$R_3 = 8\Omega$$

$$R_5 = 6\Omega$$

$$R_a = \frac{2 \times 4}{2 + 6 + 4} = \frac{2}{3}, \quad R_b = \frac{2 \times 6}{2 + 6 + 4} = 1, \quad R_c = \frac{4 \times 6}{2 + 6 + 4} = 2$$

$$I_{total} = 5V/15\Omega = 1/3 A$$

$$I = I' + I'' = 1/6 A$$