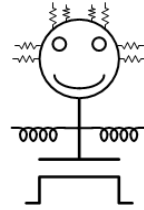





E84: Introduction to Electrical Engineering

Lab 3: Sensors




Warm-Up

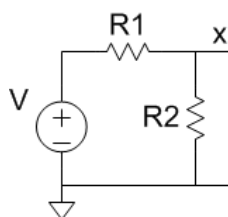
- 1) Suppose a potentiometer of resistance R is connected between GND and VDD, and the wiper position x is expressed in the range $[0, 1]$, with 0 being at the bottom by the ground node and 1 being at the top near the VDD node. Develop a Thevenin equivalent circuit for the potentiometer as a function of x .
- 2) Compute the Thevenin and Norton equivalents for the following attenuators viewed from node x .



(a) L-attenuator

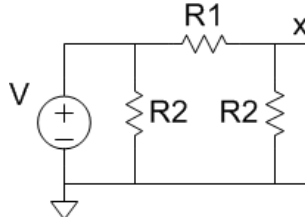


(b) Π -attenuator

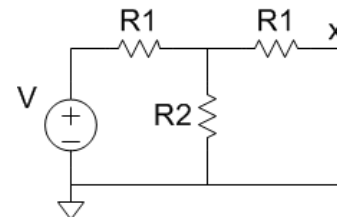

(c) T-attenuator

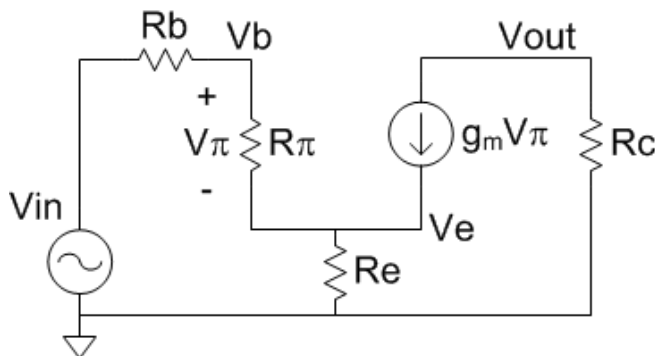- 3) The following circuit diagram is a small-signal model of a common emitter bipolar transistor amplifier with emitter degradation (you will derive such a model later this semester). Note that V_n is the voltage drop across resistor R_n , and that the voltage-dependent current source produces a current that is proportional to this voltage. Compute the relationship between V_{in} and V_{out} .



Lab

*** load cell on Wheatstone bridge? Later lab adds amplifier?

Solutions

Warm-Up

1) Using the voltage divider equation and parallel and series combinations, these can be solved by inspection:

(a) 1 V (b) 2 V (c) 3 V


2) This circuit is called an R-2R ladder and functions as a 3-bit digital-to-analog converter. This can be done painfully by KCL or intuitively by recursively applying Thevenin equivalents.

$$X = [R_L / (R + R_L)] (D_0 + 2D_1 + 4D_2)/8$$


This circuit can be extended to N inputs by adding more stages of the R-2R ladder.

Lab

1) 10k Potentiometer

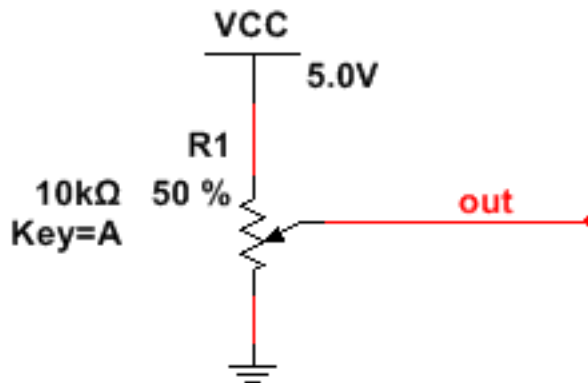

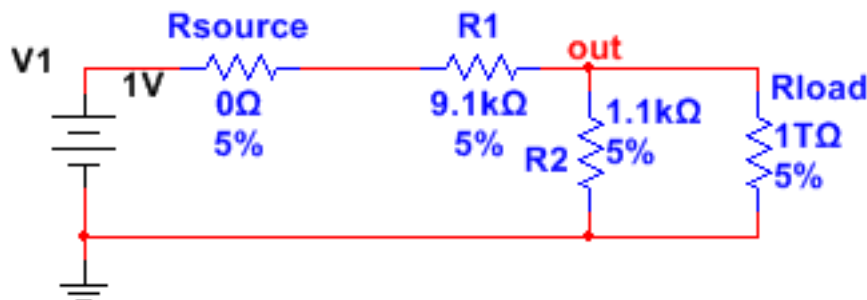The output varies from 0 to 5 V as the knob is turned.



2)


$$V_{out} = V_{in} [(R_2 || R_L) / (R_2 || R_L + R_1 + R_s)]$$

Choose $R_1 = 9.1k$, $R_2 = 1.1k$ to achieve the following performance

Case	R1	R2	RL	Rs	Gain
Unloaded	9.1k	1.1k	Infinity	0	0.108
Load impedance	9.1k	1.1k	10k	0	0.098
Source impedance	9.1k	1.1k	Infinity	1k	0.098
Both	9.1k	1.1k	10k	1k	0.089
Unloaded w/ variation	9.1k - 5%	1.1k + 5%	Infinity	0	1.18
Fully loaded w/ variation	9.1k + 5%	1.1k - 5%	10k	1k	0.082


The DC sweep with nominal values and no source or load impedance confirms the unloaded gain of 0.108.

DC Transfer Characteristic

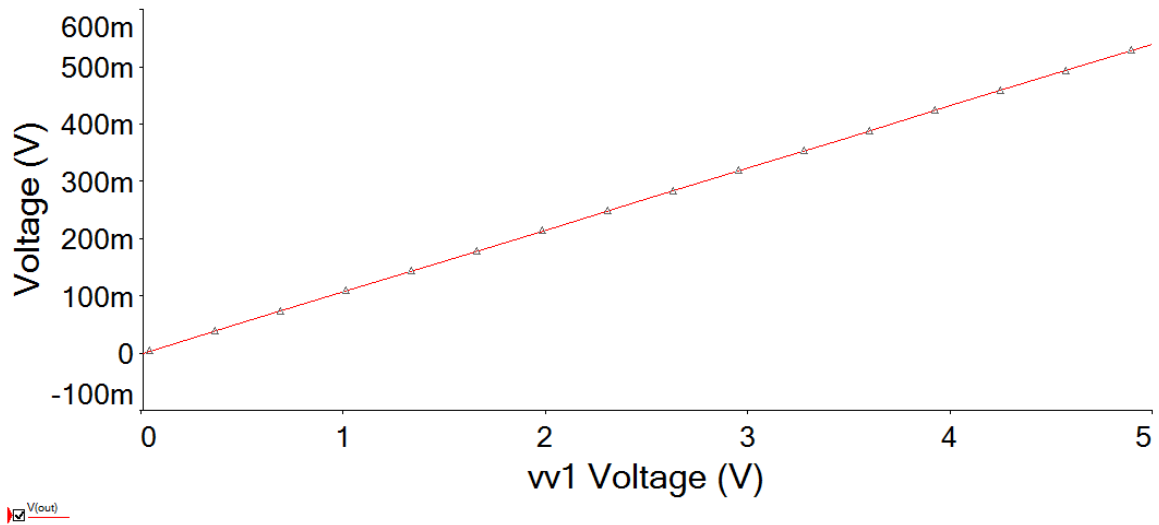

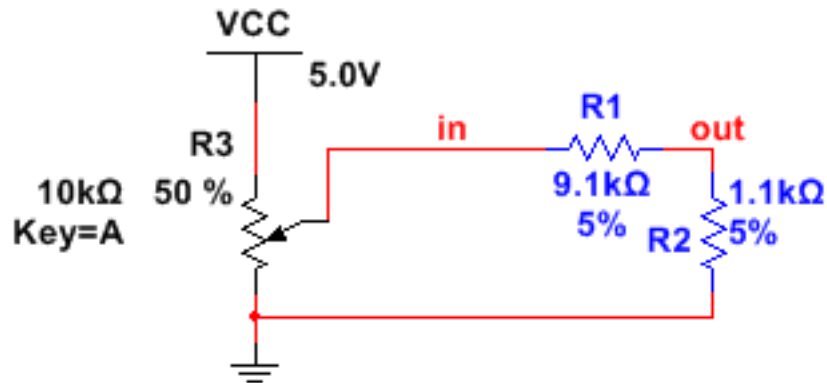3) The potentiometer has a Thevenin equivalent of 2.5 V in series with 5k.

When the source impedance is 5k and load impedance is infinite, the attenuator has a nominal gain of 0.0867. Hence, the output is 0.216 V rather than the nominal 0.25 V achieved by a perfect divide-by-10 attenuator. In other words, the attenuator loads the potentiometer and reduces the voltage.



$V_{in} = 2.008 \text{ V}$; $V_{out} = 0.216 \text{ V}$

Grading Rubric:

- | | |
|---|--|
| 2 | Complete, succinct, and coherent typed lab report |
| | WARM-UP |
| 3 | Warm-up Problem 1 (1 each) |
| 4 | Warm-up Problem 2 (2 for correct equation, 1 for application, 1 for extension to N bits) |
| | PART 1 |
| 1 | Schematic for potentiometer circuit |
| 1 | Test results indicating potentiometer circuit operates |
| | PART 2 |
| 1 | Multisim schematic for attenuator |
| 2 | Analysis of attenuator (including proof that attenuation is within spec across source and load impedance and component variation effects) |
| 2 | Simulation of attenuator (including component variation) |
| 2 | Test results showing attenuator works across loading |
| | PART 3 |
| 1 | Measured attenuator output of about 0.18 V |
| 2 | Analysis or simulation agreeing with measurement and explanation of result (including noting that source impedance higher than attenuator was designed to accept so output is $< 0.25 \text{ V}$) |

Total: 19