

1. (10 points) FoEE 6.39

 


Fig. P6.38

6.39 For the ideal-diode circuit given in Fig. P6.38, reverse the polarity of the 3-V source. The input voltage to the resulting clipper circuit is $v_s = 12 \sin \omega t$ V. Determine the output voltage v_o and sketch this function.

6.44 The ideal-diode circuit shown in Fig. P6.44 is known as a **full-wave (or bridge) rectifier circuit**. Determine which diodes are ON and which are OFF when (a) $v_s > 0$ V, and (b) $v_s < 0$ V. Sketch the output voltage v_o for the case that the input voltage is $v_s = A \sin \omega t$ V.

 


Fig. P6.44

2. (10 points) FoEE 6.44

a) When $v_s > 0$ V
 D_1, D_3 are on.
 D_2, D_4 are off.

Ckt would look like this:

Inspection of this circuit verifies that $v_2, v_4 \leq 0$ V.
 $i_1 = i_3 > 0$ A.



So, $v_o = +v_s$ V.

b) When $v_s < 0$
 D_1, D_3 off
 D_2, D_4 on

If $v_s < 0$, then $v_o = -v_s$ for $v_s < 0$


Inspection to verify D_1, D_3 off: $v_1, v_3 \leq 0$
 D_2, D_4 on, $i_2, i_4 > 0$

If $v_s(t) = A \sin \omega t$

  

⑥ FoEE 6.39

When diode is ON:

 

$$i_1 = \frac{v_s - 3}{1K}$$


$$i_2 = \frac{v_o}{3K} = 1mA$$

$$i = i_2 - i_1 = 1mA - \frac{v_s - 3}{1K} = \frac{3 - 3v_s + 9}{3K} = \frac{-3v_s + 12}{3K}$$

This i has to be > 0 so, $-3v_s + 12 > 0$

$$v_s < 4V$$

When diode is off:

 

$$v_o = \frac{3K}{4K} \cdot v_s = \frac{3}{4}v_s$$

$$v = -v_o + 3 = -\frac{3}{4}v_s + 3$$

In summary: $v_o = \begin{cases} 3 & \text{for } v_s < 4 \text{ (Diode ON)} \\ \frac{3}{4}v_s & \text{for } v_s \geq 4 \text{ (Diode OFF)} \end{cases}$

$$v \leq 0, -\frac{3}{4}v_s + 3 \leq 0$$

$$\text{So, } v_s \geq 4V$$


3. (10 points) FoEE 6.35

6.35 A silicon diode has a saturation current of 10 nA at 300 K.


(a) Plot an i - v characteristic curve on a piece of graph paper.

 (b) Suppose that this diode is used in the circuit given in Fig. 6.16a, on p. 368, where $v_1 = 1$ V and $R = 100 \Omega$. Use the i - v curve obtained in part (a) to determine graphically i and v .

For a silicon diode we use $\gamma = 2$, $V_T = \frac{\text{temperature in K}}{11,586}$
 We are told that $I_S = 10 \text{ nA}$ at 300 K.
 Using the equation: $i = I_S (e^{v/\gamma V_T} - 1)$ we can plot i .



b) If the diode is used in this circuit:

 

We can add the $i = \frac{-v}{100} + \frac{1}{100}$ load line as seen in the plot above.

The crossing point tells us: $i = 3.4 \text{ mA}$, $v = 0.66 \text{ V}$

4. (15 points) FoEE 6.60

6.60 For the half-wave rectifier circuit given in Fig. 6.20, on p. 373, replace the ideal diode with a diode having $R_f = 20 \Omega$ and $V_g = 0.6$ V (see Fig. 6.42 on p. 388). Sketch the output voltage v_o , labeling it sufficiently, for the case that the input voltage is $v_s = 6 \sin \omega t$ V and $R = 100 \Omega$.


 


Fig. 6.20 An ideal-diode circuit.

 


When $v_s > 0.6$ V D is on. Justification for this? When D is on:

$$v_s = 0.6 + 20i + 100i = 0.6 + 120i$$


$$\frac{v_s - 0.6}{120} = i \quad i \text{ has to be } > 0 \text{ if D is on.}$$

$$\text{So } v_s > 0.6. \text{ When D is on, } v_o = 100i = \frac{5}{6}v_s - 0.5.$$

When D is off, $v_o = 0$.

 

 6.62 For the circuit given in Fig. 6.50, on p. 395, reverse D_1 . The identical silicon Zener diodes have saturation currents of 10 nA at 300 K. Find i , v_1 , and v_2 when $V_S = 6$ V and the breakdown voltage of the diodes is (a) 9 V and (b) 5 V.



By KCL, we know $i_1 = -i_2$. Given the orientation of the source and the diodes, we can be reasonably sure that D_1 will be on and that D_2 will either be in reverse bias or breakdown.

a) $V_Z = 9$ V.

Since the source is well below the breakdown voltage, the logical guess of these states would be:

D_1 forward bias and D_2 reverse bias.

So, i_2 is going to be forced to be at $-I_S$, 10 nA.

This diode can allow a range of voltages, but the current is fixed. So, we can use this current to find i_1 , then use that to find v_1 . And KVL to find v_2 .

$$i_1 = I_S (e^{v_1/4V_T} - 1) \text{ so,}$$

$$v_1 = \ln\left(\frac{i_1}{I_S} + 1\right) \eta V_T$$

$$i_1 = -i_2 = I_S \Rightarrow v_1 = \ln(2) \cdot 2 \cdot \frac{300}{11586} = 0.036 \text{ V}$$

By KVL: $v_2 = -5.964 \text{ V}$ i as originally drawn is -10 nA.

b) $V_Z = 5$ V. Now, by the same logic as above, we can say D_1 is forward bias and D_2 is likely broken down. If this is the case, v_2 will be fixed at -5V, but can allow a large range of negative currents.

So, by KVL $v_1 = 1 \text{ V}$. $v_2 = -5 \text{ V}$

And $i_1 = I_S (e^{v_1/4V_T} - 1) = 2.43 \text{ A}$

So, $i \text{ (as drawn)} = -2.43 \text{ A}$

Note that if you kept the polarity of v_1 as originally drawn instead of flipping it with the diode, your answers for v_1 would be flipped.

6.79 For the clamping circuit shown in Fig. P6.79, the Zener diode has a breakdown voltage of 6 V. Sketch the output voltage v_o when the input voltage is $v_s = 24 \sin \omega t$ V and $RC \gg T = 2\pi/\omega$.


 


Fig. P6.79

8/6.79

$$v_s = 24 \sin \omega t$$

 

$$D_2: V_Z = 6V$$

$$RC \gg T = \frac{2\pi}{\omega}$$


The first time v_s goes to positive 24, D_2 is in breakdown and D_1 is on. In breakdown, $v_c = -6V \therefore v_o = 6V$.

By KVL, $v_c = 18V$.

Because the RC time constant is very high compared to the frequency of the input, the capacitor charges to 18V and doesn't have time to discharge. Thus, this capacitor is always on.

$v_o = -v_c + v_s$ So, v_o will just be a shifted down version of v_s .

$$v_o = 24 \sin \omega t - 18$$

 

7. (0 points) FoEE 6.41

6.41 The input voltage to the clipper circuit shown in Fig. P6.41 is $v_s = 12 \sin \omega t$ V. Determine the output voltage v_o and sketch this function.


 


Fig. P6.41

1st get a feel for what happens in this circuit.

 If D_2 is on $v_a = 6$ V and D_1 is off (I)



$$v_a = 6 \text{ V}$$

$$i_a = \frac{6}{3\text{k}} = 2 \text{ mA}$$


$$i_2 = \frac{v_s - 6}{1\text{k}} - 2 \text{ mA}$$

$$i_2 > 0 \text{ when } v_s > 8$$

(III)

Both can't be on...

(IV) Both can be off

 

$$v_a = \frac{3}{4} v_s$$

$$v_2 = v_a - 6$$

$$v_1 = -v_a - 3$$

$$= \frac{3}{4} v_s - 6$$

$$= -\frac{3}{4} v_s - 3$$

$$v_2 < 0$$

when

$$v_1 < 0$$

$$\text{when } -\frac{3}{4} v_s < 3$$


$$\frac{3}{4} v_s - 6 < 0$$

$$v_s > -4$$

$$\frac{3}{4} v_s < 6$$

$$v_s < 8$$
 
$$\text{So, } v_o = \begin{cases} -3 \text{ V} & v_s < -4 \\ \frac{3}{4} v_s \text{ V} & -4 \leq v_s \leq 8 \\ 6 \text{ V} & v_s \geq 8 \end{cases}$$



6.31 For the diode circuit shown in Fig. P6.31, D_1 and D_2 are silicon diodes with saturation currents of 5 nA and 10 nA, respectively, at 300 K. Given that both diodes are reverse biased, find v_1 and v_2 .


 


Fig. P6.31

 

We are given saturation currents of 5 nA for D_1 and 10 nA for D_2 .

We know that neither diode can allow more negative current than its negative I_s .

$$\text{So, } i_1 = -5 \text{ nA}$$

$$i_2 = -5 \text{ nA}$$

$$v_2 = \eta V_T \ln\left(\frac{i_2}{I_{s2}} + 1\right) = 2 \frac{300}{11.586} \ln\left(\frac{-5 \text{ nA}}{10 \text{ nA}} + 1\right) = -0.036 \text{ V}$$

$$\text{By KVL } v_1 = -5.964 \text{ V, } v_2 = -0.036 \text{ V}$$

6.32 For the diode circuit shown in Fig. P6.32, D_1 and D_2 are silicon diodes having saturation currents of 5 nA and 10 nA, respectively, at 300 K. Given that both diodes are forward biased, find the value of R for which the current is 15 mA.


 


Fig. P6.32

 

Find R that yields the current of 15 mA.

$$\text{If } i = 15 \text{ mA, } i_1 = i_2 = 15 \text{ mA}$$

$$v_1 = \eta V_T \ln\left(\frac{15 \text{ mA}}{5 \text{ nA}} + 1\right) = 0.772 \text{ V}$$

$$v_2 = \eta V_T \ln\left(\frac{15 \text{ mA}}{10 \text{ nA}} + 1\right) = 0.736 \text{ V}$$

$$\therefore \text{By KVL } v_R = 6 - 0.772 - 0.736 = 4.49 \text{ V}$$

$$R = \frac{v_R}{i} = \frac{4.49}{15 \text{ mA}} = 299 \Omega$$