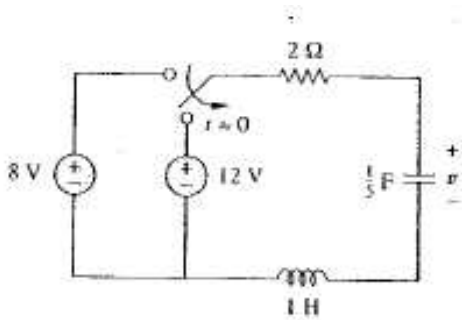


E84: HW5 (Due Wednesday, Oct. 10th - NO LATE DAYS)

1. (15 points) FoEE 3.57
2. (10 points) FoEE 3.58
3. (10 points) FoEE 3.59
4. (15 points) Determine $v(t)$ for $t > 0$ for the following circuit:



5. (15 points) FoEE 3.82 – Only set up the 2nd order differential equation that will allow you to solve for the step response, $v_o(t)$ when $C=0.2\text{ F}$ and $v_s(t) = 2u(t)\text{ V}$.
 6. (5 points) 4.5 b
- Optional problems:
7. (0 points) 3.60
 8. (0 points) 3.61
 9. (0 points) 3.62