| Energy Level (n) | 1 | 2 | 3 | 4 | 5 | 6 |
|----------------------------|---|---|----|----|----|----|
| | | _ | M | | _ | _ |
| Electron Capacity $(2n^2)$ | 2 | 8 | 18 | 32 | 50 | 72 |

$$I_D = I_0 \left(e^{V_D/\eta V_T} - 1 \right) pprox I_0 e^{V_D/\eta V_T},$$

$$V_D = \eta V_T \ln \left(\frac{I_D}{I_0} + 1\right) \approx \eta V_T \ln(I_D/I_0)$$

$$V_T = kT/e$$

 $k = 1.38 \times 10^{-23}$

$$V_T = kT/e = 26 \ mV$$

$$I_D \approx -I_0$$

$$V_D = 0$$

$$I_D \approx I_0 e^{V_D/V_T}$$

| I_D | 1 mA | 5 mA | 10 mA | 20 mA | 100 mA |
|---|-------|------|-------|-------|--------|
| V_D for Si $(I_0 = 10^{-10}, \eta = 1.4)$ | | | | | |
| V_D for Ge $(I_0 = 10^{-4}, \eta = 1.0)$ | 0.06V | 0.10 | 0.12V | 0.14 | 0.18V |

$$R = \Delta V / \Delta I$$

$$V_D(I_D)$$

$$R_D = dV_D/dI_D$$

$$R_D = \frac{d V_D}{d I_D} = \frac{d}{d I_D} \left[\eta V_T \ln \left(\frac{I_D + I_0}{I_0} \right) \right] = \eta V_T \frac{I_0}{I_D + I_0} \frac{1}{I_0} = \eta \frac{V_T}{I_D + I_0} \approx \eta \frac{V_T}{I_D}$$

$$I_D + I_0 \approx I_D$$

 $V_T = 26 \ mV$

| I_D | 0.05 mA | 0.1 mA | 0.2 mA | 0.5 mA | 1 mA | 2 mA | 5 mA |
|-----------------------------|-------------|-------------|-------------|------------|------------|------------|-----------|
| R_D for Si $(\eta = 1.4)$ | 728Ω | 364Ω | 182Ω | 73Ω | 36Ω | 18Ω | 7Ω |

$$R_D = \infty$$

$$R_D = 0$$

$$I_D = V/R$$

$$I_D = (V - 0.7)/R$$

$$I_D = (V - 0.7)/(R + R_D)$$

$$I_D = V/R = 3 mA$$

$$I_D = (V - 0.7)/R = 2.3/1000 = 2.3 \text{ mA}$$

$$I_D = (3 - 0.7)/(1000 + 20) = 2.255 \, mA$$

$$V_D = 0.7 + I_D R_D = 0.745 V$$

$$\begin{cases} I_D = I_0(e^{V_D/V_T} - 1) \\ V_D = V - RI_D \end{cases}$$

$$V_D = V - RI_0(e^{V_D/V_T} - 1)$$

$$I_D = I_0 (e^{V_D/V_T} - 1)$$

$$V = V_D + I_D R$$

$$(V_D = 0, I_D = V/R)$$

$$(I_D = V, I_D = 0)$$

$$(V_D = 0.75 \ V, I_D = 2.4 \ mA)$$

$$14.7/\sqrt{2} = 10.4V$$

$$I \approx V/R_L = 14/10 = 1.4 \ mA$$

$$T = 1/f = 1/60 = 16.7 \ ms$$

$$\Delta Q \approx IT = 1.4 \ mA \times 16.7 \ ms = 23.4 \ \mu C$$

$$\Delta V = \Delta Q/C < 14 \times 5/\% = 0.7V$$

$$C = \Delta Q/\Delta V = 23.4 \ \mu C/0.7V = 33.4 \ \mu F$$

$$i(t) = \frac{V}{R_L} e^{-t}$$

$$I_C = I_E - I_B$$

$$=\frac{I_C}{I_E}<1,$$

 $\alpha = 99\% \approx 1$

$$I_E - I_C = I_E - \alpha I_E = (1 - \alpha)I_E$$

$$\frac{I_C}{\alpha} = \frac{I_B}{1 - \alpha}$$

 $I_E = f(V_{BE}, V_{CB}) \approx f(V_{BE}) = \frac{I_B}{1 - \alpha} = \frac{1}{1 - \alpha} I_0(e^{V_{BE}/V_T} - 1)$

$$I_B = I_0(e^{V_{BE}/V_T} - 1)$$

 $V_{BE} = 0.7 V$

$$I_C = f(I_E, V_{CB}) \approx f(I_E) = \alpha I_E$$

$$I_C = I_{CB0}$$

$$I_C = \alpha I_E + I_{CB0} \approx \alpha I_E$$

$$V_{CB} = 0$$

$$V_{CE} = V_{CB} + V_{BE},$$

$$V_{CB} = V_{CE} - V_{BE}$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha I_E}{(1 - \alpha)I_E} = \frac{\alpha}{1 - \alpha}$$

$$\beta = 0.99/(1 - 0.99) = 99$$

$$\beta = \frac{\alpha}{1-\alpha}, \quad \alpha = \frac{\beta}{1+\beta}, \quad 1+\beta = \frac{1}{1-\alpha}, \quad 1-\alpha = \frac{1}{1+\beta}$$

$$I_B = f(V_{BE}, V_{CE}) \approx f(V_{BE}) = I_0(e^{V_{BE}/V_T} - 1)$$

$$I_C = f(I_B, V_{CE}) \approx f(I_B) = \beta I_B$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B, \qquad V_{CE} = V_{CB} + V_{BE}$$

$$\frac{I_{out}}{I_{in}} = \frac{I_C}{I_E},$$

 $= \alpha I$ F

$$I_C + I_B = \alpha I_E + (1 - \alpha)I_E$$

$$\frac{I_{out}}{I_{in}} = \frac{I_C}{I_B},$$

$$I_C = \beta I_B$$

$$I_C + I_B = \beta I_B + I_B$$

$$I_C = \alpha I_E$$

$$V_{CB} = -V_{BE}$$

$$\beta = \alpha/(1-\alpha)$$

$$V_{CC} = 12V$$

$$R_B = 6K\Omega$$

$$R_C = 2K\Omega$$

$$(V_{CE} = 0, I_C = V_{CC}/R_C = 6 mA)$$

$$(I_C = 0, V_{CE} = V_{CC} = 12 V)$$

$$V_{out} = V_{CE}$$

$$V_{BE} = V_{in} = 0 < 0.7V$$

$$I_C = \beta I_B = 0$$

$$V_C = V_{CC} = 12 V$$

$$V_{in} = 1V$$

$$V_{BE} \approx 0.7 \ V$$

$$(V_{in} - V_{BE})/R_B = (1 - 0.7)/6 = 0.05 \ mA$$

$$\beta I_B = 60 \times 0.05 \ mA = 3 \ mA$$

$$V_{CC} - I_C R_C = 12 V - 3 mA \times 2 K\Omega = 6 V$$

$$V_{in} = 2V$$

$$I_B = (2 - 0.7)/6 = 0.22 \ mA$$

$$I_C = \beta I_B = 13 \ mA$$

$$V_{CE} = 12 V - 13 mA \times 2 K\Omega = -14 V$$

$$V_{CE} = 0.2V$$

$$(V_{CC} - V_{CE})/R_C = (12 - 0.2)/2 = 5.9 \text{ mA}$$

$$I_C = \beta I_B$$

$$I_C = I_{CE0} \approx 0$$

$$V_C = V_{CC}$$

$$V_{BE} \approx 0.7V$$

$$I_C = \beta I_B < V_{CC}/R_C$$

$$V_C = V_{CC} - R_C I_C$$

$$\beta I_B > V_{CC}/R_C$$

$$V_{CE} \approx 0.2V$$

$$I_E = I_B + I_C$$

$$V_{in} = V_{BE} = V_B$$

$$V_{out} = V_{CE} = V_C$$

 $R_C = 1.5K \Omega$

$$v_{in}(t) = v_{be}(t)$$

$$v_{be}(t) = 0.02 \cos(\omega t) V$$

$$V_{BE} + v_{be}(t) = 0.7 + 0.02 \cos(\omega t)$$

V

$$r_{be} = \frac{\triangle v_{be}}{\triangle i_b} = \frac{40 \, mV}{0.1 \, mA} = 400 \, \Omega$$

$$I_B + i_b(t) \approx 0.1 + \frac{\triangle v_{be}}{r_{be}} = 0.1 + \frac{20 \cos(\omega t)}{400} = (0.1 + 0.05 \cos(\omega t)) \ mA$$

$$I_B + i_b(t) = \frac{V_{BE} + v_{be}(t)}{r_{be}} = \frac{0.7 + 0.02 \cos(\omega t)}{400} = (1.75 + 0.05 \cos(\omega t)) \ mA$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$\begin{cases} I_C = 0 \\ V_{CE} = V_{CC} = 15V \end{cases}$$

$$\begin{cases} V_{CE} = 0 \\ I_C = V_{CC}/R_C = 15V/1.5 \, k\Omega = 10 \, mA \end{cases}$$

$$I_C + i_c(t) = \beta(I_B + i_b(t)) = 40 \times (0.1 + 0.05\cos(\omega t)) = (4 + 2\cos(\omega t)) mA$$

$$V_C + v_c(t) = V_{CC} - R_C(I_C + i_c(t)) = 15 - 1.5(4 + 2\cos(\omega t)) = (9 - 3\cos(\omega t)) V$$

 $-\cos \omega t$

 ωt COS

$$R_C = 1.5 \ k\Omega$$

$$V_1 = V_{BE} = 0.2V, \ 0.7V$$

$$V_2 = V_{CE} = V_C$$

 $V_{BE} = 0.2V < 0.7V$

$$V_2 = V_{CC} - I_C R_C = V_{CC} = 15V$$

 $V_{BE} = 0.7V$

$$I_C = \beta I_B = 5 \ mA$$

$$V_C = V_{CC} - I_C R_C = 15 - 5 \times 10^{-3} \times 1.5 \times 10^3 = 7.5 V$$

$$V_{BE} = 0.8V > 0.7V$$

$$I_C = \beta I_B = 20 \ mA$$

$$V_C = V_{CC} - I_C R_C = 15 - 20 \times 10^{-3} \times 1.5 \times 10^3 = -15V$$

$$I_C = V_{CC}/R_C = 15 \ V/1.5 \ k\Omega = 10 \ mA$$

$$I_C = (15 - 0.2)/1.5 \approx 10 \ mA$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B = \beta \frac{V_{CC} - V_{BE}}{R_B}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$R_B = 200 \, k\Omega$$

$$V_{CC} = 12 V$$

$$V_{CE} = V_{CC}/2 = 6 V$$

 $V_{BE} = 0.6 \ V$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.6}{200} = 0.057 \, mA, \quad I_C = \beta I_B = 5.7 \, mA$$

$$V_{CE} = V_{CC} - I_C R_C = 12 - 5.7 R_C = 6 V,$$

$$R_C = \frac{6V}{5.6 \, mA} \approx 1.05 \, k\Omega$$

$$\frac{V_{CC}}{R_C} = \frac{12 \, V}{R_C} = 2 \times I_C = 11.4 \, mA,$$

$$R_C = \frac{12 V}{11.4 \, mA} \approx 1.05 \, k\Omega$$

$$V_{CE} = V_{CC} - R_C I_C = 12 V - 1.05 k\Omega \times 5.7 mA \approx 6 V$$

$$R_C = 1 k\Omega$$

$$(V_{CE}, I_C)$$

 $\beta = 50, 100, 200$

$$V_C = V_{CC} - I_C R_C$$

$$I_C = 0, \ V_C = V_{CC} = 12 V$$

$$V_C = 0, I_C = V_C/R_C = 12 V/1 k\Omega = 12 mA$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.6}{200 \times 10^3} = 0.057 \ mA$$

| | $\beta = 50$ | $\beta = 100$ | $\beta = 200$ |
|------------------------------|--------------|---------------|---------------|
| $I_C = \beta I_B \ (mA)$ | 2.85 | 5.70 | 11.4 |
| $V_C = V_{CC} - R_C I_C (V)$ | 9.15 | 6.3 | 0.6 |

=

$$(V_C = 12/2 = 6 V, I_C = 12/2 = 6 mA)$$

$$I_C \uparrow \Longrightarrow I_e = I_C + I_B \uparrow \Longrightarrow V_E \uparrow \Longrightarrow V_{BE} \downarrow \Longrightarrow I_B \downarrow \Longrightarrow I_C = \beta I_B \downarrow$$

 I_2

 I_{R}

$$V_B = V_{CC} \; \frac{R_2}{R_1 + R_2}$$

$$V_B - V_{BE} - I_E R_E = V_B - V_{BE} - (I_C + I_B)R_E = V_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{V_B - V_{BE}}{(\beta + 1)R_E},$$
 $I_C = \beta I_B = \frac{\beta (V_B - V_{BE})}{(\beta + 1)R_E} \approx \frac{V_B - V_{BE}}{R_E} = \frac{V_E}{R_E}$

$$V_{Th} = V_B$$

$$R_{Th} = R_B = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_B - I_B R_B - V_{BE} - (I_C + I_B)R_E = V_B - V_{BE} - I_B R_B - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{V_B - V_{BE}}{(\beta + 1)R_E + R_B},$$

$$I_C = \beta I_B = \frac{\beta (V_B - V_{BE})}{(\beta + 1)R_E + R_B}$$

$$R_B = R_1 || R_2$$

$$\beta R_E \gg R_B = R_1 || R_2$$

 $\beta R_E \geq 10 R_B$

$$I_C \approx \frac{\beta(V_B - V_{BE})}{(\beta + 1)R_E} \approx \frac{V_B - V_{BE}}{R_E} = \frac{V_E}{R_E}$$

$$I_C \approx \beta (V_{CC} - V_{BE})/R_B$$

$$R_1 = 100 \, k\Omega$$

$$R_E = 1 k\Omega$$

$$R_C = 2 k\Omega$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E \approx V_{CC} - I_C (R_C + R_E)$$

$$I_C = V_{CC}/(R_C + R_E) = 12/(2+1) = 4 \, mA$$

$$I_C = 0 \, mA$$

$$V_{CE} = 12 V/2 = 6V$$

$$I_C = 4 \, mA/2 = 2 \, mA$$

$$R_1||R_2 = \frac{R_1 R_2}{R_1 + R_2} = 26.5 \,k\Omega$$

$$V_{CC} \frac{R_2}{R_1 + R_2} = 3.18 \ V$$

$$V_B - V_{BE} = 3.18 - 0.7 = 2.48 V$$

$$I_E = \frac{V_E}{R_E} = 2.48 \ mA$$

$$V_{CC} - R_C I_C = 12 - 2 \times 2.48 = 7.04 V$$

$$V_C - V_E = 7.04 - 2.48 = 4.56 V$$

$$\frac{V_B - V_{BE}}{(\beta + 1)R_E + R_B}$$

$$I_E R_E = (I_C + I_B) R_E$$

$$V_{CC} - I_C R_C$$

| | $\beta = 50$ | $\beta = 100$ | $\beta = 200$ |
|-------------|--------------|---------------|---------------|
| $I_C (mA)$ | 1.60 | 1.94 | 2.18 |
| $V_E(V)$ | 1.63 | 1.96 | 2.19 |
| $V_C(V)$ | 8.80 | 8.11 | 7.65 |
| $V_B(V)$ | 2.33 | 2.66 | 2.89 |
| $V_{CE}(V)$ | 7.17 | 6.15 | 5.46 |

$$V_{CE} \approx 6 V$$

$$R_1 = R_2 = 100 \, k\Omega$$

$$R_E = 2 k\Omega$$

$$R_{Th} = R_B = R_1 || R_2 = 50 \ k\Omega, \qquad V_{Th} = V_B = V_{CC} \frac{R_2}{R_1 + R_2} = 6 \ V$$

$$I_C = \beta I_B = \frac{\beta(V_B - V_{BE})}{(\beta + 1)R_E + R_B} = \frac{100 \times (6 - 0.7)}{101 \times 2 + 50} = \frac{530}{250} = 2.12$$

$$V_{CE} = V_{CC} - (I_C + I_B)R_E - I_CR_C \approx V_{CC} - I_C(R_E + R_C) = 12 - 2.12 \times (2 + R_C)$$

$$V_{CE} = 12 \, V/2 = 6 \, V$$

$$I_C \uparrow \Longrightarrow V_C = V_{CC} - R_C I_C \downarrow \Longrightarrow I_B \downarrow \Longrightarrow I_C = \beta I_B \downarrow$$

$$V_{CC} = R_C(I_B + I_C) + R_B I_B + V_{BE} = (R_C(\beta + 1) + R_B)I_B + 0.7$$

$$I_B = \frac{V_{CC} - 0.7}{(\beta + 1)R_C + R_B}, \quad I_C = \beta I_B = \frac{\beta(V_{CC} - 0.7)}{(\beta + 1)R_C + R_B}$$

$$V_C = V_{CC} - (I_C + I_B)R_C = V_{CC} - (\beta + 1)I_BR_C$$

$$R_B \ll (\beta + 1)R_C$$

$$I_C \approx (V_{CC} - 0.7)/R_C$$

$$V_{CC} = 10V$$

$$I_C = 2 \, mA$$

$$R_C = (V_{CC} - V_C)/I_C = 5V/2mA = 2.5K\Omega$$

$$I_B = I_C/\beta = 0.02mA$$
, $R_B = (5 - 0.7)/0.02 = 4.3/0.02 = 215K\Omega$

$$I_C = \beta I_B,$$
 $V_C = V_{CC} - I_E R_C = V_{CC} - (\beta + 1) I_B R_C$

| | $\beta = 50$ | $\beta = 100$ | $\beta = 200$ |
|------------|--------------|---------------|---------------|
| $I_B (mA)$ | 0.027 | 0.02 | 0.013 |
| $I_C(mA)$ | 1.36 | 2 | 2.6 |
| $V_C(V)$ | 6.6 | 5 | 3.5 |

$$v_1 = b_{be}, i_1 = i_b, v_2 = v_{ce}, i_2 = i_c$$

$$C_4^2 = 4!/[2!(4-2)!] = 6$$

$$\begin{cases} v_1 = f_1(i_1, i_2) \\ v_2 = f_2(i_1, i_2) \end{cases}, \qquad \begin{cases} i_1 = f_3(v_1, v_2) \\ i_2 = f_4(v_1, v_2) \end{cases}, \qquad \begin{cases} v_1 = f_5(i_1, v_2) \\ i_2 = f_6(i_1, v_2) \end{cases}$$

$$\begin{cases} v_{be} = v_{be}(i_b, v_{ce}) \\ i_c = i_c(i_b, v_{ce}) \end{cases}$$

$$dv_{be} = \frac{\partial v_{be}}{\partial i_b} di_b + \frac{\partial v_{be}}{\partial v_{ce}} dv_{ce} = h_i di_b + h_r dv_{ce} \qquad di_c = \frac{\partial i_c}{\partial i_b} di_b + \frac{\partial i_c}{\partial v_{ce}} dv_{ce} = h_f di_b + h_o dv_{ce}$$

$$h_i, h_f, h_r, h_o$$

$$h_i = \partial v_{be} / \partial i_b = r_{be}$$

$$h_r = \partial v_{be} / \partial v_{ce}$$

$$h_f = \partial i_c / \partial i_b = \beta$$

$$h_f = \beta$$

$$h_o = \partial i_c / \partial v_{ce} = 1/r_{ce}$$

$$v_{be} = \frac{\partial v_{be}}{\partial i_b} i_b + \frac{\partial v_{be}}{\partial v_{ce}} v_{ce} = h_i i_b + h_r v_{ce} \approx h_i i_b \qquad i_c = \frac{\partial i_c}{\partial i_b} i_b + \frac{\partial i_c}{\partial v_{ce}} v_{ce} = h_f i_b + h_o v_{ce} \approx h_f i_b$$

$$h_f I_B = \beta I_B$$

$$h_i = r_{be} \approx \eta \, \frac{V_T}{I_B}$$

$$(V_T = 26 \, mV)$$

$$r_{in} = R_1 ||R_2|| r_{be} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_{be}}\right)^{-1} = \frac{R_1 R_2 r_{be}}{R_1 R_2 + R_1 r_{be} + R_2 r_{be}} \approx r_{be}$$

$$R_1, R_2 \gg r_{be}$$

$$r_{out} = R_C$$

$$v_b \approx v_{in} \frac{r_{be}}{r_{be} + R_s}, \qquad i_b = \frac{v_b}{r_{be}} \approx \frac{v_{in}}{r_{be} + R_s}$$

$$i_c = \beta i_b$$

$$v_{out} = v_c \approx -i_c (R_C || R_L) = -\beta i_b (R_C || R_L) = -\beta \frac{v_{in}}{r_{be} + R_s} (R_C || R_L)$$

$$A = \frac{v_{out}}{v_{in}} = \frac{v_c}{v_{in}} \approx -\beta \frac{R_C || R_L}{r_{be} + R_s}$$

$$R_s \ll r_{in} = R_1 ||R_2|| r_{be} \approx r_{be}, \quad R_L \gg r_{out} = R_C$$

$$A = \frac{v_{out}}{v_{in}} \approx -\beta \frac{R_C}{r_{be}}$$

 $r_{in} \approx r_{be}$

$$r_{out} \approx R_C$$

$$r_{be} \approx \eta \ V_T / I_B$$

$$R_B = 300 \, k\Omega$$

$$R_C = R_L = 4 \, k\Omega$$

$$R_s = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \approx \frac{V_{CC}}{R_B} = \frac{12}{300 \times 10^3} = 40 \times 10^{-6} A = 40 \ \mu A$$

$$V_{CE}=0,$$

$$I_C = \frac{V_{CC}}{R_C} = \frac{12 V}{4 \times 10^3 \Omega} = 3 \times 10^{-3} A = 3 mA$$

$$I_C = \beta I_B = 40 \times 40 \ \mu A = 1.6 \ mA, \qquad V_{CE} = V_{CC} - R_C I_C = 12 - 4 \times 1.6 = 5.6 \ V$$

$$R_L' = R_C || R_L = 2 k\Omega$$

$$1/R_L' = 1/2$$

$$\frac{1.5}{V_{AC0} - 6} = \frac{1}{2} \implies V_{AC0} = 8.8 V$$

$$\frac{I_{AC0} - 1.5}{6} = \frac{1}{2} \implies I_{AC0} = 4.4 \ mA$$

$$v_{in} = 20 \sin \omega t \, mV$$

$$V_{BE} = 0.6V$$

$$v_{be}(t) = V_{BE} + v_{in} = (0.6 + 0.02 \sin \omega t) V$$

$$i_b(t) = I_B + i_{in} = (40 + 20 \sin \omega t) \,\mu A$$

$$r_{be} = \frac{\Delta v_{be}}{\Delta i_b} = \frac{20 \, mV}{20 \, \mu A} = 1 \, k\Omega$$

$$i_c(t) = \beta \ i_b(t) = 40 \times (40 + 20 \sin \omega t) \ \mu A = (1.6 + 0.8 \sin \omega t) \ mA$$

$$v_c(t) = V_{AC0} - R'_L i_c(t) = 8.8 - 2 \times (1.6 + 0.8 \sin \omega t) = (5.6 - 1.6 \sin \omega t) V = v_{out}(t)$$

$$A_v = \frac{|v_{out}|}{|v_{in}|} = \frac{1.6}{0.02} = 80$$

$$r_{be} = 1 k\Omega$$

$$(V_{CC} - V_{BE})/R_B \approx V_{CC}/R_B = 40 \ \mu A$$

$$\beta I_B = 40 \times 40 \ \mu A = 1.6 \ mA$$

$$V_{CC} - R_C I_C = 12 - 1.6 \times 4 = 5.6 V$$

$$i_b = v_{in}/r_{be}, \quad v_c = -i_c \left(R_C || R_L \right)$$

$$A_v = \frac{v_c}{v_{in}} = -\frac{\beta i_b (R_C || R_L)}{r_{be} i_b} = -\frac{\beta (R_C || R_L)}{r_{be}} = -\frac{(40 \times 2) k\Omega}{1 k\Omega} = -80$$

$$r_{in} = R_B || r_{be} \approx r_{be} = 1 \, k\Omega$$

$$r_{out} = R_C = 4 k\Omega$$

$$v_{in} = v_b, \ v_{out} = v_c$$

$$\frac{v_c-v_s}{R_B}+\beta i_b+\frac{v_c}{R_C}=\frac{v_c-v_s}{R_B}+\beta\,\frac{v_s}{r_{be}}+\frac{v_c}{R_C}=0$$

$$v_C \left(\frac{1}{R_B} + \frac{1}{R_C} \right) = v_s \left(\frac{1}{R_B} - \beta \frac{1}{r_{be}} \right)$$

$$\frac{v_{out}}{v_{in}} = \frac{v_c}{v_s} = \frac{1/R_B - \beta/r_{be}}{1/R_B + 1/R_C} = \frac{R_C(r_{be} - \beta R_B)}{(R_B + R_C)r_{be}} \approx -\beta \frac{R_C R_B}{(R_B + R_C)r_{be}}$$

$$-\beta \frac{R_B||R_C}{r_{be}} = -\beta \frac{R_C}{r_{be}} \frac{R_B}{R_B + R_C} \stackrel{R_B \to \infty}{\Longrightarrow} -\beta \frac{R_C}{r_{be}}$$

$$i_b = v_b/r_{be} = v_s/r_{be}$$

$$\dot{a} = \frac{v_b - (-R_C \beta i_b)}{R_B + R_C} = \frac{v_b + R_C \beta v_b / r_{be}}{R_B + R_C} = v_b \frac{1 + R_C \beta / r_{be}}{R_B + R_C} \approx v_b \frac{\beta R_C / r_{be}}{R_B + R_C}$$

$$r'_{in} = \frac{v_b}{i} = \frac{R_B + R_C}{\beta R_C / r_{be}} = \frac{R_B + R_C}{\beta R_C} r_{be}$$

$$r_{in} = r_{be} ||r'_{in} = r_{be} \frac{1}{1 + \beta R_C / (R_B + R_C)} = r_{be} \frac{R_B + R_C}{R_B + (\beta + 1)R_C} = \begin{cases} r_{be} & R_B \to \infty \\ r_{be} / \beta & R_B \to 0 \end{cases}$$

$$v_{oc} = Av_b = -\beta \frac{R_C}{r_{be}} \frac{1}{1 + R_C/R_B} v_b$$

$$i' = v_b/R_B$$

$$i'' = -\beta i_b = -\beta v_b / r_{be}$$

$$i_{sc} = i' + i'' = v_b \left(\frac{1}{R_B} - \frac{\beta}{r_{be}}\right)$$

$$\frac{v_{oc}}{i_{sc}} = \frac{-\beta \frac{R_C}{r_{be}} \frac{1}{1 + R_C/R_B}}{1/R_B - \beta/r_{be}} = \frac{-\beta \frac{R_C}{r_{be}} \frac{1}{1 + R_C/R_B}}{\frac{r_{be} - \beta R_B}{R_B r_{be}}}$$

$$\frac{-\beta \frac{R_C}{r_{be}} \frac{R_B}{R_B + R_C}}{\frac{-\beta R_B}{R_B r_{be}}} = \frac{R_C R_B}{R_C + R_B} = R_C ||R_B \stackrel{R_B \to \infty}{\Longrightarrow} R_C$$

$$V_{CC} - V_{BE} = I_B R_B + (\beta + 1) I_B R_E, \quad I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \beta \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}, \quad V_{CE} \approx V_{CC} - I_C(R_C + R_E)$$

$$V_{CC} = 12V, \ R_E = 0.1 \, k\Omega, \ \beta = 100$$

$$R_C = 1.9 \, k\Omega$$

$$I_E = \frac{V_{CC} - V_{CE}}{R_C + R_E} = \frac{6}{0.1 + 1.9} = 3 \, mA, \quad I_B = \frac{I_C}{\beta} = 0.03 \, mA$$

$$R_B + (\beta + 1)R_E = \frac{V_{CC} - V_{BE}}{I_B} = \frac{12 - 0.7}{0.03} = 377 \, k\Omega$$

$$R_B = 377 - 100 \times 0.1 = 367 \, k\Omega$$

$$R_B = 250 \, k\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_E} = \frac{12 - 0.7}{250 + 100 \times 0.1} = \frac{11.3}{260} = 0.044$$

$$\frac{V_{CC} - V_{CE}}{R_C + R_E} = \frac{6}{0.1 + R_C} = I_C = \beta I_B = 4.4 \, mA$$

$$R_C = 1.26 \, k\Omega$$

$$i_b + \beta i_b = (\beta + 1)i_b = \frac{v_e}{R_E} = \frac{v_{in} - r_{be}i_b}{R_E}$$

$$i_b = \frac{v_{in}}{r_{be} + (\beta + 1)R_E}$$

$$r_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{i_b} = r_{be} + (\beta + 1)R_E \approx \beta R_E$$

$$A = \frac{v_{out}}{v_{in}} = -\frac{\beta i_b(R_C||R_L)}{v_{in}} = -\frac{\beta (R_C||R_L)}{v_{in}} \frac{v_{in}}{r_{be} + (\beta + 1)R_E} = -\frac{\beta R_C||R_L}{r_{be} + (\beta + 1)R_E} \approx -\frac{R_C||R_L}{R_E}$$

$$v_{oc} = -\beta i_b R_C$$

$$i_{sc} = -\beta i_b$$

$$r_{out} = \frac{v_{oc}}{i_{sc}} = R_C$$

$$v_{out} = v_e \uparrow \Longrightarrow v_{be} \downarrow \Longrightarrow i_b \downarrow \Longrightarrow i_c \downarrow \Longrightarrow v_e \downarrow$$

$$V_{CC} = R_B I_B + V_{BE} + R_E I_E = R_B I_B + V_{BE} + R_E (\beta + 1) I_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)R_E + R_B}$$

$$I_E = (\beta + 1)I_B = \frac{(\beta + 1)(V_{CC} - V_{BE})}{(\beta + 1)R_E + R_B}$$

$$V_{CE} = V_{CC} - V_E = V_{CC} - R_E I_E$$

$$R_B = 100 \, k\Omega$$

$$V_{CC} = 10 V$$

$$V_{CE} = V_{CC} - V_E = 10 - V_E = V_{CC}/2 = 5 V$$

$$V_E = I_E R_E = R_E \frac{(\beta + 1)(V_{CC} - V_{BE})}{(\beta + 1)R_E + R_B} = \frac{101 R_E (10 - 0.7)}{101 R_E + 100} = 5 V$$

$$R_E = 1.15 \, k\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)R_E + R_B} = 0.043 \, mA, \quad I_C = \beta \, I_B = 100 \, I_B = 4.3 \, mA$$

$$I_E = (\beta + 1)I_B = 4.34 \, mA, \quad V_E = I_E R_E = 5 \, V$$

$$\begin{cases} v_{out} = v_e = (R_E || R_L) i_e = (R_E || R_L) (i_c + i_b) = (R_E || R_L) (\beta + 1) i_b \\ v_{in} = (R_s + r_{be}) i_b + v_{out} = (R_s + r_{be}) i_b + (R_E || R_L) (\beta + 1) i_b \end{cases}$$

$$A = \frac{v_{out}}{v_{in}} = \frac{(\beta + 1)(R_E||R_L)}{(R_s + r_{be}) + (\beta + 1)(R_E||R_L)} \approx 1$$

$$R_s + r_{be} \ll (\beta + 1)(R_E||R_L)$$

$$v_b = i_b r_{be} + v_{out} = i_b \left[r_{be} + (\beta + 1)(R_E || R_L) \right]$$

$$r'_{in} = \frac{v_b}{i_b} = r_{be} + (\beta + 1)(R_E||R_L) \approx r_{be} + \beta(R_E||R_L) \approx \beta(R_E||R_L)$$

$$r_{in} = R_B || r'_{in} \approx r'_{in} \approx \beta(R_E || R_L)$$

$$r_{in} = R_1 ||R_2|| r_{be} \approx r_{be}$$

 $v_{oc} \approx v_{in}$

$$i_{sc} = i_e = (\beta + 1)i_b = (\beta + 1)\frac{v_{in}}{r_{be} + R_s} \approx \beta \frac{v_{in}}{r_{be} + R_s}$$

$$r'_{out} = \frac{v_{oc}}{i_{sc}} \approx \frac{r_{be} + R_s}{\beta}$$

$$r_{out} = R_E ||r'_{out} = R_E || \left(\frac{r_{be} + R_s}{\beta}\right) \approx \frac{r_{be} + R_s}{\beta}$$

 v_{om}

$$r_{in} = \beta \left(R_E || R_L \right)$$

$$r_{out} = (r_{be} + R_s)/\beta$$

$$R_s + r_{be}$$

$$R_{in} = \beta R_E$$

 $R_{out} = r_{be}/beta$

$$\triangle V = V_1 - V_2$$

$$I_E = I_1 + I_2$$

$$V_1 = V_2$$

$$\Delta V = V_1 - V_2 = 0$$

$$I_1 = I_2 = I_E/2$$

$$V_{out} = V_{CC} - I_2 R_C$$

$$V_1 \uparrow \Longrightarrow I_1 \uparrow \Longrightarrow I_2 \downarrow \Longrightarrow V_{out} = V_{CC} - I_2 R_c \uparrow$$

$$V_1 \downarrow \Longrightarrow I_1 \downarrow \Longrightarrow I_2 \uparrow \Longrightarrow V_{out} = V_{CC} - I_2 R_c \downarrow$$

$$\beta_1 = \beta_2 = \beta$$

$$I_{ref} = \frac{V_{CC} - V_B}{R_C}$$

$$I_{ref} = I_C + 2I_B = I_C(1 + 2/\beta) \approx I_C$$

$$V_B = V_C$$

$$I_B = I_C/\beta$$

$$V_B = V_T \ln \left(\frac{I_B}{I_0} + 1 \right) \approx V_T \ln \left(\frac{I_B}{I_0} \right)$$

$$V_B \uparrow \Longrightarrow I_B \uparrow \Longrightarrow (I_C = \beta I_B) \uparrow \Longrightarrow (V_C = V_B = V_{CC} - I_C R_C) \downarrow$$

$$V_B = V_{C1}$$

$$I_{C1} \approx I_{ref} = (V_{CC} - V_B)/R_C$$

$$I_{C2} = \beta I_{B2} = I_L$$

$$V_{B2} = V_{B1} = V_B$$

$$I_{B2} = I_{B1} = I_B$$

$$I_{C2} = \beta I_B = I_{C1} = I_C$$

$$I_L = I_C = I_{ref}/(1 + 2/\beta) \approx I_{ref} = \frac{V_{CC} - V_B}{R_C}$$

$$(I_L = I_{C3}) \uparrow \Longrightarrow I_{C2} \uparrow \Longrightarrow I_{C1} \uparrow \Longrightarrow (V_{C1} = V_{B3}) \downarrow \Longrightarrow I_{B3} \downarrow \Longrightarrow (I_L = I_{C3}) \downarrow$$

$$\omega_0 = 1/\sqrt{LC}$$

$$\omega_0 = 1/\sqrt{C(L_1 + L_2)}$$

$$\omega_0 = 1/\sqrt{LC_1C_2/(C_1 + C_2)}$$

 v_{c} v_{out}

$$v_{feedback} = v_c \frac{Z_{L_1}}{Z_{L_1} + Z_{L_2}} = v_c \frac{L_1}{L_1 + L_2}, \qquad v_{feedback} = v_c \frac{Z_{C_2}}{Z_{C_2} + Z_{C_3}} = v_c \frac{C_3}{C_2 + C_3}$$

$$v_c \uparrow \Longrightarrow v_{feedback} \uparrow \Longrightarrow v_e \uparrow \Longrightarrow v_{be} \downarrow \Longrightarrow i_b \downarrow \Longrightarrow i_c \downarrow \Longrightarrow v_c \uparrow$$

 ω_1 1.カ.カ

$$\omega_{IF} = 10.7$$

$$i_c = \beta i_b = \beta I_o \left(e^{v_{be}/V_T} - 1 \right)$$

$$e^x = \sum_{k=0}^{\infty} \frac{x^k}{k!},$$

$$e^{x} - 1 = x + \frac{1}{2}x^{2} + \frac{1}{3!}x^{3} + \dots \approx x + \frac{1}{2}x^{2}$$

$$v_{be} = \cos(\omega_1 t) + \cos(\omega_2 t)$$

$$(\cos \omega_1 t + \cos \omega_2 t) + \frac{1}{2}(\cos \omega_1 t + \cos \omega_2 t)^2 + \cdots$$

$$\cos \omega_1 t + \cos \omega_2 t + \frac{1}{2} \left(\cos^2 \omega_1 t + 2 \cos \omega_1 t \cos \omega_2 t + \cos^2 \omega_2 t \right)$$

$$\cos \omega_1 t + \cos \omega_2 t + \frac{1}{4} (1 + \cos(2\omega_1 t)) + \frac{1}{2} \cos(\omega_1 + \omega_2) t + \frac{1}{2} \cos(\omega_1 - \omega_2) t + \frac{1}{4} (1 + \cos(2\omega_2 t))$$

$$\cos^2 \alpha = \frac{1 + \cos 2\alpha}{2}, \quad \cos \alpha \cos \beta = \frac{\cos(\alpha + \beta) + \cos(\alpha - \beta)}{2}$$

$$\omega_1 + \omega_2$$

$$\omega_1 - \omega_2$$

$$\Delta\omega = \omega_{OS} - \omega_{RF} = \omega_{IF}$$

$$G(j\omega)$$

$$V_o = G(V_i + FV_o) = GV_i + GFV_o,$$
 $\frac{V_o}{V_i} = H = \frac{G}{1 - GF},$ $V_o = HV_i = \frac{G}{1 - GF}V_i$

$$\angle(GF) = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC_s}},$$

$$C_s = \left(\frac{1}{C_1} + \frac{1}{C_2}\right)^{-1}$$

$$\omega_0 = 1/\sqrt{LC_s}$$

$$v_c \uparrow \Longrightarrow v_e \uparrow \Longrightarrow v_{be} \downarrow \Longrightarrow i_b \downarrow \Longrightarrow i_c = \beta i_b \downarrow \Longrightarrow v_c \uparrow$$

$$v_{C_1} = v_b$$

 v_{C}

$$v_c \uparrow \Longrightarrow v_b \downarrow \Longrightarrow v_{be} \downarrow \Longrightarrow i_b \downarrow \Longrightarrow i_c = \beta i_b \downarrow \Longrightarrow v_c \uparrow$$

$$v_e = v_t \uparrow \Longrightarrow v_b \uparrow \Longrightarrow i_b \uparrow \Longrightarrow i_e = (\beta + 1)i_b \uparrow \Longrightarrow v_e \uparrow$$

$$H = V_o/V_i$$

$$\frac{V_t - V_i}{R} + \frac{V_t}{1/j\omega C_2} + \frac{V_t}{j\omega L + 1/j\omega C_1} = 0$$

$$V_t \left(\frac{1}{R} + j\omega C_2 + \frac{j\omega C_1}{1 - \omega^2 L C_1} \right) = \frac{V_i}{R}$$

$$V_t = \frac{1}{R(\frac{1}{R} + j\omega C_2 + \frac{j\omega C_1}{1 - \omega^2 L C_1})} V_i = \frac{1}{1 + j\omega R(C_2 + C_1/(1 - \omega^2 L C_1))} V_i$$

$$C_2 + \frac{C_1}{1 - \omega_0^2 L C_1} = 0,$$

$$\omega_0 = \frac{1}{\sqrt{LC_1C_2/(C_1 + C_2)}} = \frac{1}{\sqrt{LC_s}}$$

$$V_t = V_i$$

$$Z_{C_2}||(Z_{C_1} + Z_L)| = \frac{Z_{C_2}(Z_{C_2} + Z_L)}{Z_{C_2} + Z_{C_1} + Z_L} = \frac{(1/j\omega C_1 + j\omega L)/j\omega C_2}{1/j\omega C_2 + 1/j\omega C_1 + j\omega L}$$

$$\frac{(1/j\omega C_1 + j\omega L)/C_2}{1/C_1 + 1/C_2 - \omega^2 L} = \frac{(1/j\omega C_1 + j\omega L)/C_2}{1/C_s - \omega^2 L} \stackrel{\omega = \omega_0}{\Longrightarrow}$$

$$Z_{tank} = \infty$$

$$V_t = \frac{Z_{C_2}}{Z_{C_1} + Z_{C_2}} V_o = \frac{C_1}{C_1 + C_2} V_o,$$

$$V_o = \frac{C_1 + C_2}{C_1} \ V_t = \frac{C_1 + C_2}{C_1} \ V_i$$

$$H = \frac{V_o}{V_i} = \frac{C_1 + C_2}{C_1}$$

$$V_{GS} = V_G - V_S > 0$$

$$V_{DS} = V_D - V_S > 0$$

$$\begin{cases} V_{GS} \uparrow \Longrightarrow I_D \uparrow \Longrightarrow \text{conducting} \\ V_{GS} \downarrow \Longrightarrow I_D \downarrow \Longrightarrow \text{cut off} \end{cases}$$

$$I_D = \begin{cases} 0 & \text{if } V_{GS} < V_T \text{ (cutoff)} \\ K(V_{GS} - V_T)^2 & \text{if } V_{GS} \ge V_T \text{ (conducting)} \end{cases}$$

$$I_D(V_{GS}, V_{DS})$$

$$I_C = f(I_B, V_{CE})$$

 $V_{GS} > V_T$

$$V_{GD} = V_{GS} - V_{DS} > V_T$$

$$V_{GD} = V_{GS} - V_{DS} < V_T$$

$$V_{GD} = V_{GS} - V_{DS} = V_T$$

$$V_T = 1V$$

$$V_{GS} < V_T = 1V$$

$$V_{GS} = 2V > V_T = 1V$$

$$V_{DS} < V_{GS} - V_T = 1V$$

$$V_{DS} > V_{GS} - V_T = 1V$$

$$K = 2mA/V^2$$

$$V_{GS} = 2V$$

$$V_{in} = V_{GS} > V_T$$

$$V_{DS} > V_{in} - V_T$$

$$\begin{cases} I_D = K(V_{in} - V_T)^2 \\ V_{out} = V_{DS} = V_{dd} - I_D R = V_{dd} - KR(V_{in} - V_T)^2 \end{cases}$$

$$V_{DS} = V_{out} = V_{dd} - KR(V_{in} - V_T)^2 \ge V_{in} - V_T$$

$$V_{in} - V_T$$

$$V_{in} - V_T < \frac{-1 + \sqrt{1 + 4KRV_{dd}}}{2KR},$$

$$V_{in} < \frac{-1 + \sqrt{1 + 4KRV_{dd}}}{2KR} + V_T$$

$$V_T < V_{in} < \frac{-1 + \sqrt{1 + 4KRV_{dd}}}{2KR} + V_T$$

$$0 < V_{in} - V_T < \frac{-1 + \sqrt{1 + 4KRV_{dd}}}{2KR}$$

$$g = \frac{dV_{out}}{dV_{in}} = \frac{d}{dV_{in}}(V_{dd} - KR(V_{in} - V_T)^2) = -2KR(V_{in} - V_T)$$

$$V_{dd} = 10V$$

$$R = 10k\Omega$$

$$K = 0.5 \ mA/V^2$$

$$V_{in} > V_T = 1 V$$

$$V_{in} < [-1 + \sqrt{1 + 4KRV_{dd}}]/2KR + V_T = 2.32 V$$

$$V_{out} = V_{dd} - K(V_{in} - V_T)^2 R = 10 - 5(V_{in} - 1)^2$$

$$g(V_{in}) = \frac{d}{dV_{in}}V_{out}(V_{in}) = -10(V_{in} - 1)$$

$$g(V_{in}) = g(1.8) = -10(1.8 - 1) = -8$$

$$g(V_{in}) = g(2) = -10(2-1) = -10$$

$$V_T = 1V < V_{in} < 2.32V$$

$$V_{out}(V_{in})$$

$$V_{in} < V_T = 1V$$

 $V_{out} = 1.3 < V_{in} - V_T = 2.32 - 1 = 1.32$

$$K = 1 \ mA/V^2$$

$$V_{dd} = 5V$$

$$v_{in}(t) = V_{bias} + \sin(\omega t)$$

$$V_{bias} = 1.5V$$

$$v_{out} = V_{dd} - RI_D = V_{dd} - RK(V_{in} - V_T)^2 = 5 - 10(V_{in} - 1)^2$$

 $V_{in} = 1.4V, 1.5V, 1.6V$

 $v_{out} = 3.4V, \ 2.5V, \ 1.4V$

 $i_{DS} = 0.16mA, 0.25mA, 0.36mA$

$$V_{bias} = V_{dd} \frac{R_1}{R_1 + R_2}$$

$$K = 0.5mA/V^2$$

$$V_B = V_{bias} = 1.6V$$

$$V_{GS} = V_B - V_{in}$$

$$V_{out} = V_{dd} - R_d K (V_{GS} - V_T)^2 = V_{dd} - R_d K (V_B - V_{in} - V_T)^2 = 10 - 10 \times (0.6 - V_{in})^2$$

 V_{out} = 6.4V

$$V_{GS} - V_T \ge 0$$

$$V_{GS} - V_T = V_B - V_{in} - V_T = 0.6 - V_{in} \ge 0$$

$$V_{DS} \ge V_{GS} - V_T$$

$$V_{DS} = V_{out} - V_{in} = (V_{dd} - R_d I_D) - V_{in} = V_{dd} - R_d K (V_B - V_{in} - V_T)^2 - V_{in} \ge V_B - V_{in} - V_T$$

$$V_{out} = V_{dd} - R_d K (V_B - V_{in} - V_T)^2 \ge V_B - V_T$$

$$V_{out} = 10 - 10 \times (0.6 - V_{in})^2 \ge 0.6$$

$$V_{in} \ge -0.37V$$

$$-0.37V \le V_{in} \le 0.6V$$

$$R_s = 10k\Omega$$

$$K = 10mA/V^2$$

$$I_D = V_{out}/R_s$$

$$I_D = K(V_{GS} - V_T)^2 = K(V_{in} - V_{out} - V_T)^2 = V_{out}/R_s$$

$$(V_{in} - V_{out} - 1)^2 = V_{out}$$

$$(V_{out} - 1)^2 = V_{out}$$

 V_{out} 2.6V V_{out} = 0.4V

$$V_{GS} = V_{in} - V_{out} = 2 - V_{out} > V_T = 1$$

$$V_{in} = 3V$$

$$(V_{out} - 2)^2 = V_{out}$$

$$V_{out} = 1V$$

$$g = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{1 - 0.4}{3 - 2} = 0.6 < 1$$

$$\{V_{GS}, I_D, V_{DS}\}$$

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$V_{gs} > V_{Tn}$$

$$V_{Tn} = 1 V$$

$$V_{gs} \le V_{Tp}$$

$$V_{Tp} = -1 V$$

$$f(a,b,\cdots,x)$$

$$f = FALSE$$

$$f(a,b,c) = (a'+b')c$$

$$f'(a,b,c) = [(a'+b')c]' = (a'+b')' + c' = ab + c'$$

$$f(V_1, V_2) = (V_1 V_2)' = V_1' + V_2'$$

$$(V_1 \ V_2)' = V_1' + V_2'$$

$$V_{out} = f(V_1, V_2) = V_1' + V_2' = (V_1 V_2)'$$

$$f(V_1 + V_2) = (V_1 + V_2)' = V_1' V_2'$$

$$f' = V_1 + V_2$$

$$(V_1 + V_2)' = V_1' \ V_2'$$

$$V_{out} = (V_1 + V_2)'$$

| | | AND | OR | NAND | NOR |
|-------|-------|-----------|-------------|--------------|----------------|
| V_1 | V_2 | $V_1 V_2$ | $V_1 + V_2$ | $(V_1 V_2)'$ | $(V_1 + V_2)'$ |
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 |

$$f'(a, b, c) = ab + c'$$