


# E84 Midterm Exam 1

## Instructions

- Take home, open notes, feel free to use a calculator, but not any software package such as Multisim.
- Mark your start and end times. Don't spend more than 3 hours. Due on Monday in class.
- Compare your print-out of the exam with the online version to make sure your hard copy is complete.
- Mark your name and question number clearly on top of each page. Indicate the total number of pages submitted.
- When solving a problem, list all the steps. In each step, indicate concisely what you are doing in English, then show the calculation and the result of for the step. Box the final answer. A final answer, even if correct, without evidence of the steps leading to it will receive ZERO credit.

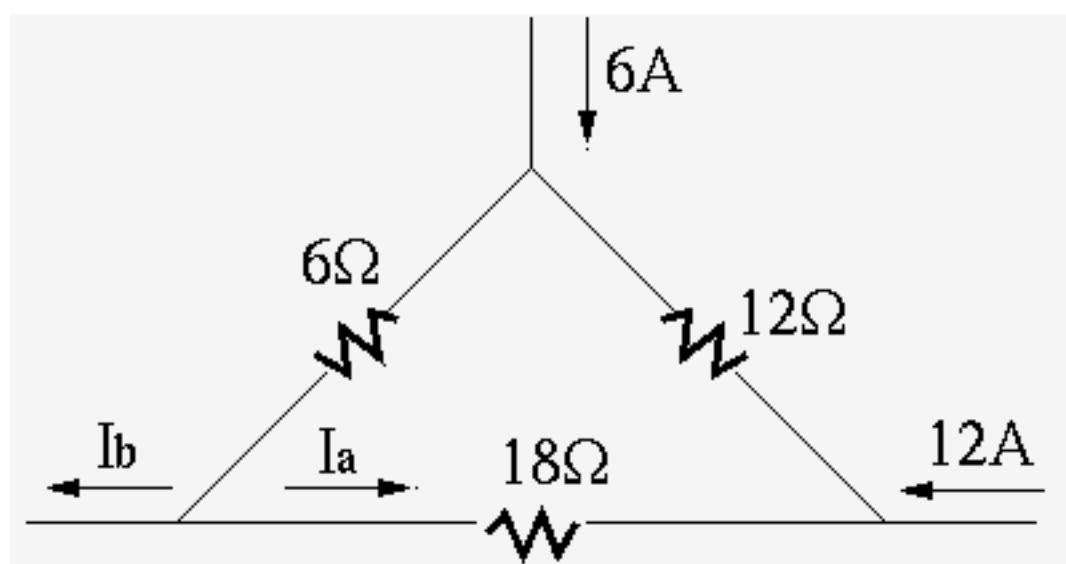
### 1. Problem 1. (30 pts)

Find the two currents labeled as  $I_a$  and  $I_b$  in the figure.


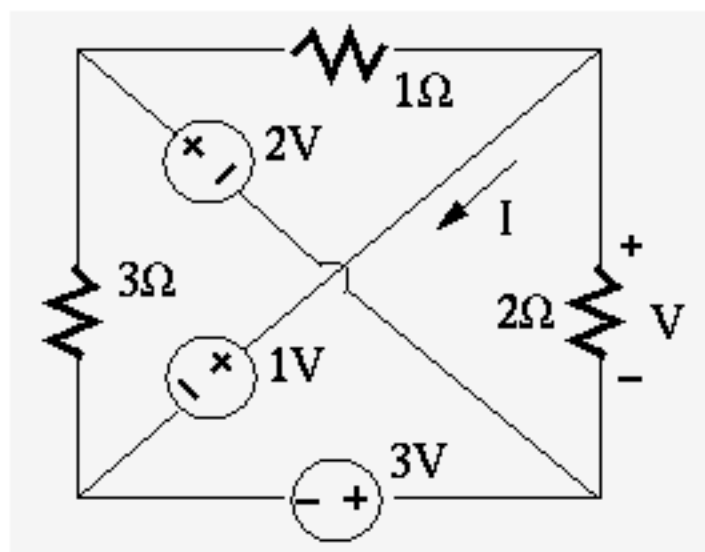
### 2. Problem 2. (30 points)

Find the voltage  $V$  across the  $2\Omega$  resistor (with assumed polarity shown), and the current  $I$  through the  $1V$  voltage source (with assumed direction shown).



### 3. Problem 3. (40 pts)

The following two parts of the problem are independent, each worth 20 pts.

- Find the resistance  $R$  so that the voltage across the resistor is  $1V$ .
- Find the resistance  $R$  so that the current through the resistor is  $0.2A$ .

