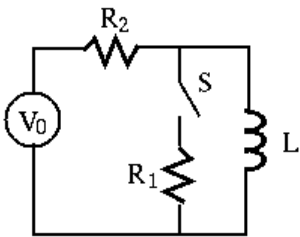


[Next](#) [Up](#) [Previous](#)

**Next:** [About this document ...](#)

## E84 Home Work 7

- Find the current  $\underline{i_1(t)}$  through resistor  $R_1$  after the switch is closed at  $t = 0$ , assuming the input is a DC voltage and the circuit is already in steady state before  $t = 0$ . (Hint: current through an inductor cannot change instantaneously.)




### Solution:

First, as current through  $L$  does not change when the switch is closed at  $t = 0$ , the current through  $R_1$  is zero  $\underline{i_1(0_+) = 0}$ . Second, when the circuit reaches steady state after the switch is closed at  $t = 0$ , the inductor is short-circuit, i.e., no current goes through  $R_1$ . Therefore,  $\underline{v_1(t) = 0}$ .

- In the circuit below,  $V_s = 6V$ ,  $R_1 = 6\Omega$ ,  $R_2 = 3\Omega$ ,  $L = 0.5H$ ,  $I_s = 2A$ .

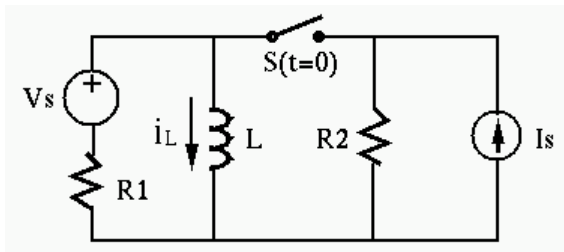Assume before the switch is closed at  $t = 0$ , the system is already stabilized. Find current  $\underline{i_L(t)}$  through  $L$  and voltage  $v_{R_1}$  across  $R_1$ .



### Solution:

$\underline{i(0) = V_s/R_1 = 6/6 = 1A}$ ,  $\underline{i(\infty) = V_s/R_1 + I_s = 1 + 2 = 3A}$  Find equivalent resistance (when both energy sources are turned off


$R = R_1 || R_2 = 3 \times 6 / (3 + 6) = 2$ ,  $\tau = L/R = 0.5/2 = 0.25 \text{ sec}$ . Final solution:

$i_L(t) = 3 + (1 - 3)e^{-t/0.25} = 3 - 2e^{-4t} \text{ (A)}$  Find  $v_{R_1}$ : apply KVL to the loop of  $V_s$ ,  $R_1$  and  $L$ , get

$$L \frac{di_L}{dt} + v_{R_1} = V_s$$

$$v_{R_1} = V_s - L di_L/dt = 6 - 0.5 \frac{d(3 - 2e^{-4t})}{dt} = 6 - 4e^{-4t}$$

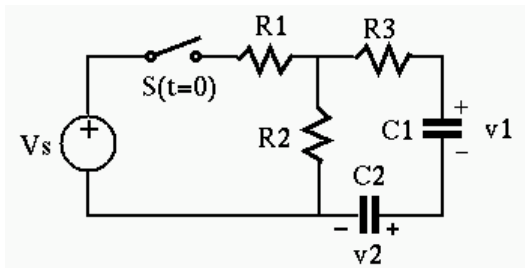3. In the circuit below,  $V_s = 12V$ ,  $R_1 = 5\Omega$ ,  $R_2 = 20\Omega$ ,  $R_3 = 6\Omega$ ,  $C_1 = 10\mu F$ ,  $C_2 = 30\mu F$ . Assume before the switch is closed at  $t = 0$ , the system is already stabilized. Find voltages  $v_1(t)$  and  $v_2(t)$  across capacitors  $C_1$  and  $C_2$ , respectively. (Hint,  $C_1$  and  $C_2$  are two capacitors in series with an equivalent capacitance is  $C = C_1 C_2 / (C_1 + C_2)$ .  $C_1$  and  $C_2$  have share the same time constant  $\tau = RC$ .)



**Solution:**

$$v_1(0) = v_2(0) = 0$$

$$v_1(\infty) + v_2(\infty) = V_s \frac{R_2}{R_1 + R_2} = 12 \frac{20}{5 + 20} = 9.6V$$

As voltage across capacitor is inversely proportional to  $C$ , we have

$$\frac{v_1(\infty)}{v_2(\infty)} = \frac{C_2}{C_1} = 3$$

i.e.,  $v_1(\infty) = 3v_2(\infty)$ , and we get  $v_1(\infty) = 7.2V$ ,  $v_2(\infty) = 2.4V$ . Find equivalent resistance:

$$R = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 6 + \frac{5 \times 20}{5 + 20} = 10\Omega$$


Find equivalent capacitance:  $C_1 C_2 / (C_1 + C_2) = 30 \times 10 / (30 + 10) = 7.5$ .

Find time constant:  $\tau = RC = 10 \times 7.5 \times 10^{-6} = 7.5 \times 10^{-5}$ . Find  $v_1(t)$  and

$$v_2(t): v_1(t) = 7.2(1 - e^{-t/(7.5 \times 10^{-5})}) \quad v_2(t) = 2.4(1 - e^{-t/(7.5 \times 10^{-5})})$$

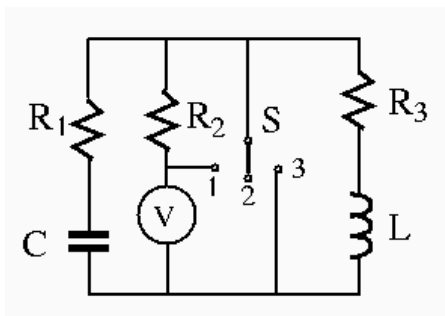4. In the circuit below,  $R_1 = 100\Omega$ ,  $R_2 = 150\Omega$ ,  $R_3 = 100\Omega$ ,  $H = 0.1H$ ,  $C = 20\mu F$ ,  $V = 60V$ . The circuit is in steady state initially when the switch is at position 2 (not connected). Find  $v_C(t)$  and  $i_L(t)$  for the following two independent cases:

- after the switch is changed to position 1 at  $t = 0$ ;
- after the switch is changed to position 3 at  $t = 0$ ;



### Solution

Find initial values:

$$v_C(0) = \frac{100}{150 + 100} \times 60 = 24V, \quad i_L(0) = \frac{6}{150 + 100} = 0.24A$$

- after the switch is put on position 1 at  $t = 0$ ,

$$v_C(\infty) = 60V, \quad i_L(\infty) = 60/100 = 0.6A$$

Find the time constants:

$$\tau_1 = R_1 C = 2 \times 10^{-3} s, \quad \tau_2 = L/R_2 = 10^{-3} s$$

The complete responses:

$$v_C(t) = v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-t/\tau_1} = 60 - 36e^{-500t}, \quad i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau_2} = 0.6 - 0.36e^{-1000t}$$

- after the switch is put on position 3 at  $t = 0$ ,

$$v_C(\infty) = 0, \quad i_L(\infty) = 0$$

The time constants are the same as above. The complete responses:

$$v_C(t) = v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-t/\tau_1} = 24e^{-500t}, \quad i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau_2} = 0.24e^{-1000t}$$

- 
- [About this document ...](#)
- 

[Next](#) [Up](#) [Previous](#)

**Next:** [About this document ...](#)

*Ruye Wang 2008-03-05*