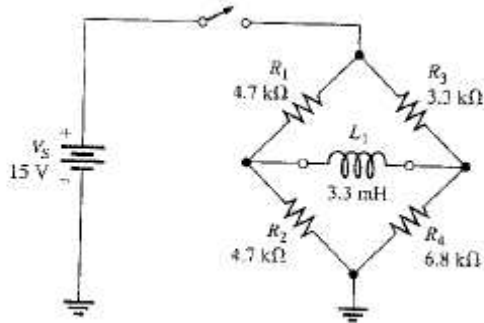


E84: HW4 (Due in class, Wednesday, October 3rd)

1. (5 points) FoEE 3.25
2. (15 points) What is the current through the inductor $1.0\mu\text{s}$ after the switch closes?



3. (10 points) FoEE 3.29
4. (15 points) FoEE 3.37
5. (10 points) FoEE 3.48
6. (15 points) FoEE 3.57

Optional Problems

7. (0 points) FoEE 3.31
8. (0 points) FoEE 3.35