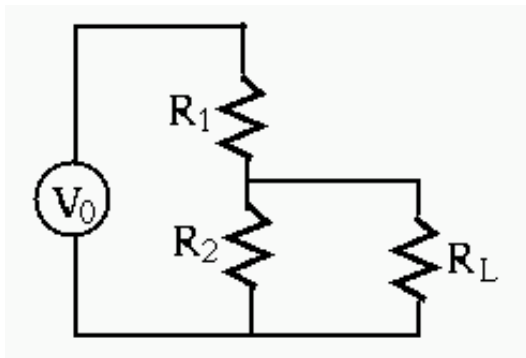


[Next](#)
[Up](#)
[Previous](#)

**Next:** [About this document ...](#)

## E84 Home Work 3


1. In the voltage divider circuit below,  $V_0 = 20V$ ,  $R_1 = R_2 = 500\Omega$ . Use Thevenin's theorem to find the current through and voltage across the load resistor  $R_L$  when it is  $100\Omega$ ,  $200\Omega$ ,  $300\Omega$ , respectively.



### Solution:

- $R_T = 250, V_T = 10V$
- When  $R_L = 100$ ,  $I_L = V_T / (R_T + R_L) = 1/35$ ,  $V_L = I_L R_L = 20/7$
- When  $R_L = 200$ ,  $I_L = V_T / (R_T + R_L) = 1/45$ ,  $V_L = I_L R_L = 40/9$
- When  $R_L = 300$ ,  $I_L = V_T / (R_T + R_L) = 1/55$ ,  $V_L = I_L R_L = 60/11$

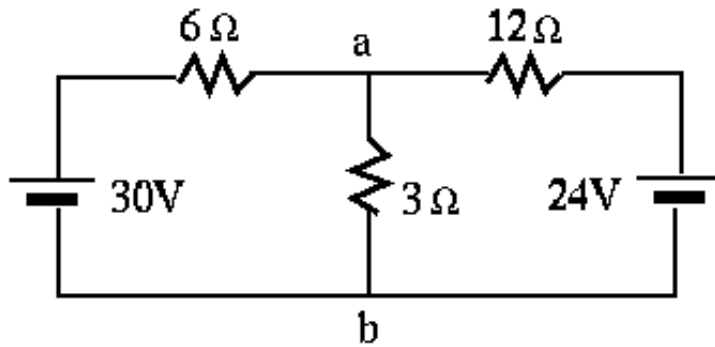2. Use Thevenin's theorem to determine the current in the  $3 - \Omega$  resistor of the following figure.




**Solution:** move two voltage sources to left, and 3- $\Omega$  resistor to the right as load find equivalent voltage  $V_o$  and internal resistance and  $R_o$ :

current going clockwise around the loop (without load):

$(30 - 24)/(6 + 12) = 1/3$  voltages across 6 ohm resistor and 12 ohm resistor are  $-2V$  and  $4V$ ,  $V_o = 30 - 2 = 24 + 4 = 28V$ ,  $R_o = 6//12 = 4\Omega$ ,  
current through load resistor is  $28/(4 + 3) = 4A$ .

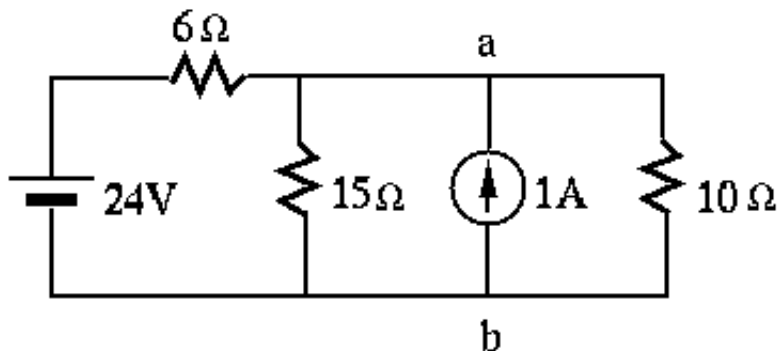3. Find voltage across and the current through the 10- $\Omega$  resistor.




**Solution:**

Use superposition principle. When 24V is acting alone with 1A open, parallel resistors 15 and 10 become  $15//10 = 6$ ,

$V'_{ab} = 24 \times 6/(6 + 6) = 12V$ ,  $I' = 12/10 = 1.2A$ . When 1A is acting alone with 24V closed, parallel resistors 6 and 15 become  $90/21 = 30/7$ ,  $I'' = 10/(10 + 30/7) = 3/10 = 0.3A$ ,  $V''_{ab} = I'' \times 10 = 3V$ ,  
overall  $V = V' + V'' = 12 + 3 = 15$ ,  $I = I' + I'' = 1.2 + 0.3 = 1.5A$ .

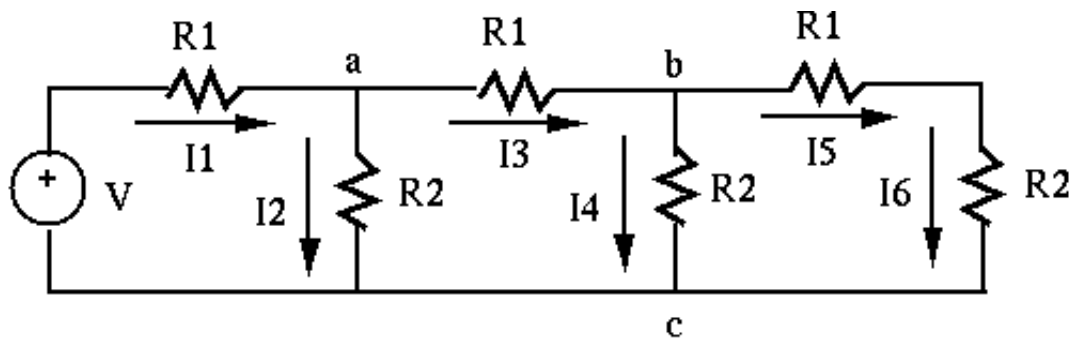4. Find all currents in the diagram in which  $V = 120V$ ,  $R_1 = 2\Omega$ ,  $R_2 = 20\Omega$ .

**Hint:** It is very hard to solve the problem by finding the currents in the order of  $I_1$ ,  $I_3$ ,  $I_5$ , as computing the resistances of the resistor network is tedious. However, it is much more straight forward to find the currents in the order of  $I_5$ ,  $I_3$ ,  $I_1$ , if you assume  $I_5$  is known, e.g.,  $I_5 = 1A$ . However, the voltage for the voltage source obtained based on this assumption is of course not as given (120V). In this case, the linearity property  $F(ax + by) = aF(x) + bF(y)$  can be applied. In particular, given  $y = F(x)$ , then  $ay = F(ax) = aF(x)$ . Use this relationship to find the actual values of the currents.



**Solution:**

- use node c as reference (ground), assume  $I_5 = 1$ , then

$$V_b = (20 + 2) = 22V \quad I_4 = 22/20 = 1.1A, \quad I_3 = I_4 + I_5 = 1.1 + 1 = 2.1A,$$

$$V_a = 2.1 \times 2 + V_b = 4.2 + 22 = 26.2V, \quad I_2 = V_a/20 = 26.2/20 = 1.31A,$$

$$I_1 = I_2 + I_3 = 1.31 + 2.1 = 3.41A,$$

$$V_0 = I_1 \times 2 + V_a = 2 \times 3.41 + 26.2 = 33.02.$$

- But the given voltage source is 120V, all currents should be scaled up by a factor  $120/33.02 = 3.634$ ,  $I_1 = 12.39$ ,  $I_2 = 4.76$ ,


$$I_3 = 7.63, \quad I_4 = 4.00, \quad I_5 = 3.63$$

5. In the circuit below,  $R_1 = 1\Omega$ ,  $V_2 = 2V$ ,  $R_3 = 1\Omega$ ,  $R_4 = 3\Omega$ ,  $I_5 = 5A$ ,

$V_6 = 2V$ , and  $R_6 = 1\Omega$ . Find

1. current through voltage source  $V_2$ .
2. current through resistor  $R_3$

(Hint: consider superposition theorem.)

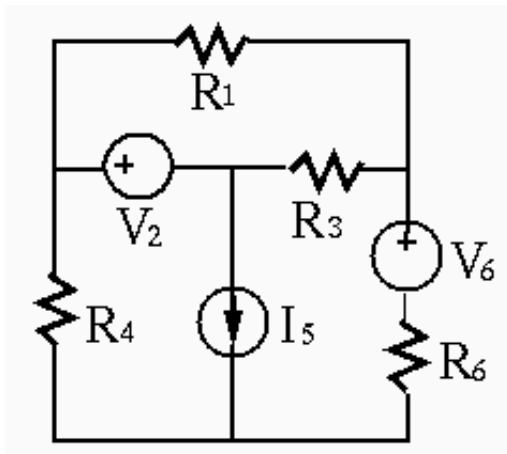

**Solution:** Consider each of the three sources alone:

- V2 alone (I5 open, V6 short):

$$I' = V2/[R1 + R3/(R3 + R6)] = 2/(1 + 1/4) = 2/(1 + 4/5) = 10/9$$

(left).

- V6 alone (I5 open, V2 short):

$$I'' = 0.5xV6/(R6 + R4 + R1//R3) = 1/(1 + 3 + 0.5) = 1/4.5 = 2/9 \text{ (left)}$$

- I5 alone (V2, V6 both short):

$$\text{current thru R6: } I5 \times R4/[R4 + (R6 + R1//R3)] = 5 \times 3/4.5 = 10/3$$


---

current thru R4:

$$I5 \times (R6 + R1//R3)/[R4 + (R6 + R1//R3)] = 5 \times 1.5/4.5 = 5/3$$


---

current thru R1 is (half of that thru R6): 5/3

- $I'''$  is the sum of current thru R4, current thru R1 = 5/3 + 5/3 = 10/3 (right) and current thru V2:

$$I' + I'' + I''' = 10/9 + 2/9 - 10/3 = -2 \text{ (left) or } 2 \text{ (right)}$$


---

- currents thru R3 due to V2 and V6 respectively are the same as that thru V2 currents thru R3 due to I5 is (half of current thru R6 above): 5/3 (left)
- total current thru R3:  $10/9 + 2/9 + 5/3 = 3$  (left)
- The sum of two currents is equal to  $I5 = 2 + 3 = 5$


6. In the circuit below,  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 3\Omega$ ,  $R_4 = 4\Omega$ ,  $R_5 = 5\Omega$ ,

$V_1 = 4V$ ,  $V_2 = 5V$ . Find voltage  $V$  across and current  $I$  through the

load resistor  $R_3$  by converting the rest of the circuit into a

- Thevenin's voltage source  $V_T$  with  $R_T$
- Norton's current source  $I_N$  with  $R_N$

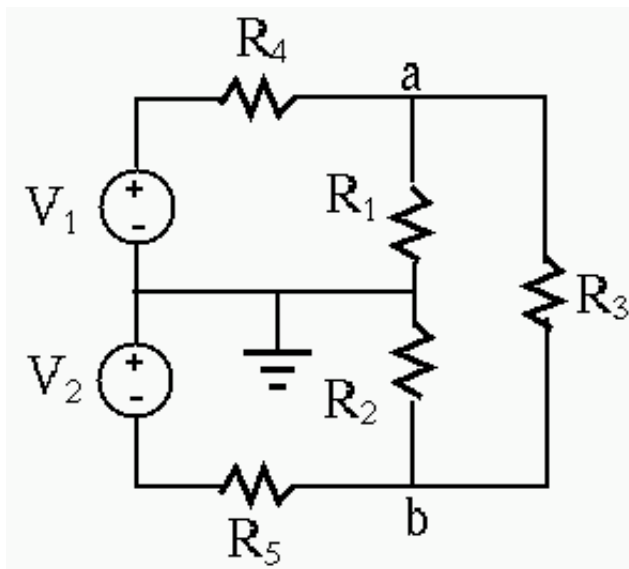Verify your results by converting the current source into a voltage source (or vice versa). Then find voltage  $V$  and current  $I$  associated with load  $R_3$ .



### Solution:

- Find Thevenin's voltage source  $V_T$  with  $R_T$ . First turn voltage sources off and find  $R_T$  between nodes  $a$  and  $b$ :

$$R_T = R_1 || R_4 + R_2 || R_5 = \frac{R_1 R_4}{R_1 + R_4} + \frac{R_2 R_5}{R_2 + R_5} = 78/35$$

Find  $V_{oc}$ :

$$V_a = V_1 \frac{R_1}{R_1 + R_4} = 4/5, \quad V_b = -V_2 \frac{R_2}{R_2 + R_5} = -10/7$$

$$V_{oc} = V_a - V_b = 78/35$$

- Norton's current source  $I_N$  with  $R_N$ . First  $R_N = R_T = 78/35$ .  
Then use loop current method to find  $I_N = I_{sc}$ . Assume loop currents  $I_a$  (top-left loop),  $I_b$  (bottom left loop) and  $I_c = I_{sc} = I_N$  (right loop), and we have these loop current equations:

$$\begin{cases} 5I_a & & -I_c = 4 \\ & 7I_b & -2I_c = 5 \\ -I_a & -2I_b & +3I_c = 0 \end{cases}$$

Solving this to get  $I_N = I_{sc} = I_c = 1$ .

- Verify your results by converting the current source into a voltage source (or vise versa).

$$I_N R_N = 78/35 = V_T$$

Finally,

$$I = \frac{V_T}{R_T + R_3} = \frac{78/35}{78/35 + 3} = \frac{78}{183} = 0.426$$

$$V = IR_3 = 1.28V$$

- 
- [About this document ...](#)
- 

[Next](#) [Up](#) [Previous](#)

**Next:** [About this document ...](#)

*Ruye Wang 2008-02-12*